

AY-2025-2026
ODD SEM

Department of ECE

ANALOG ELECTRONIC CIRCUIT DESIGN
23EC2104

Topic:

HYBRID MODEL FOR BJT
CONFIGURATIONS-CE, CB,CC

Session - 09

SESSION CONTENT

- Hybrid Model for BJT Configurations-CE, CB, CC

AIM OF THE SESSION



To analyze and understand the Hybrid- π model for the Common Emitter (CE), CB, CC configuration of a BJT and apply it in small-signal amplifier circuit analysis.

INSTRUCTIONAL OBJECTIVES

The Session is designed to:

1. Explain the concept of the Hybrid- π model for BJTs.
2. Identify the key elements of the Hybrid- π equivalent circuit.
3. Describe the role of each parameter (r_{π} , g_m , r_o) in CE, CB, CC configuration.
4. Apply the model to analyze small-signal behavior of CE, CB, CC amplifiers.


LEARNING OUTCOMES

At the end of this session, learners will be able to:


1. Construct the Hybrid- π equivalent circuit for a given BJT CE, CB, CC configuration.
2. Use the model to calculate small-signal parameters and performance metrics.
3. Understand how the base-emitter resistance (r_{π}) and transconductance (g_m) influence signal gain.



CE Amplifier With Emitter Resistance

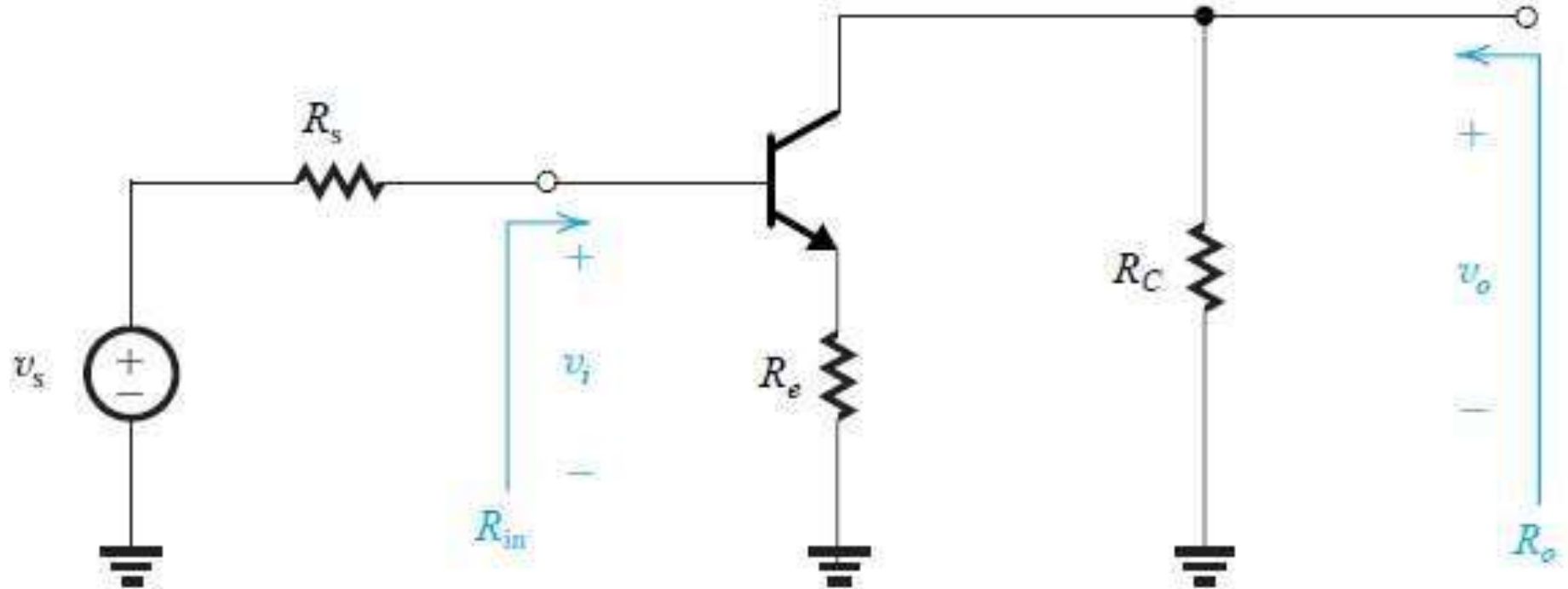

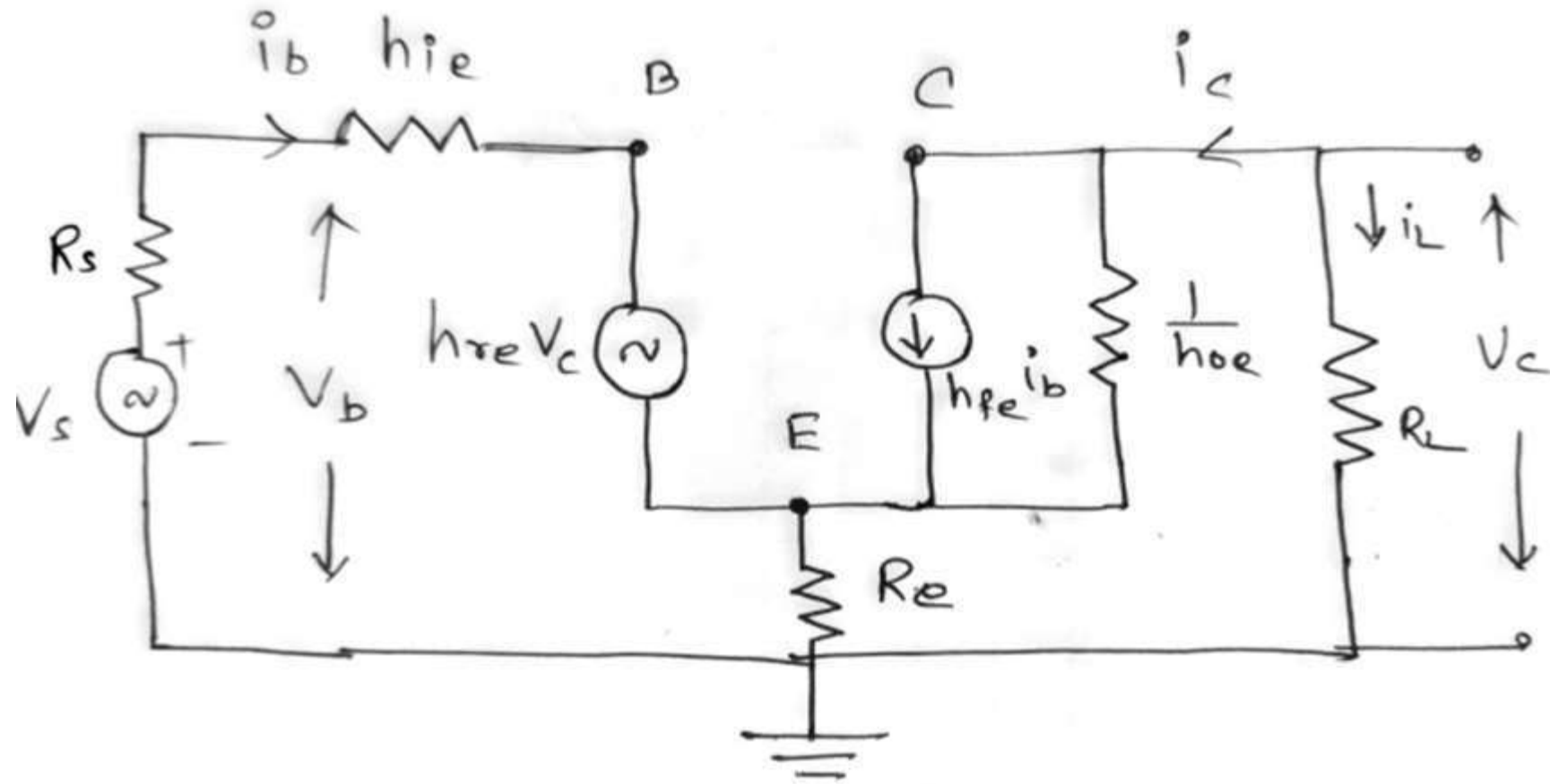CE Amplifier With Emitter Resistance (Using Hybrid Model)



CE Amplifier With Emitter Resistance (Using Hybrid Model)

$$A_i = -\frac{h_{fe}}{1+h_{oe}R_L}$$

$$R_i = \frac{v_b}{i_b} = h_{ie} + h_{re} A_i R_L$$

$$A_v = \frac{A_i R_L}{R_i}$$

$$Y_o = h_{oe} - \frac{h_{fe} h_{re}}{R_s + h_{ie}} \text{ and } R_o = \frac{1}{Y_o}$$

$$A_i = \frac{h_{oe} R_e - h_{fe}}{1 + h_{oe} (R_L + R_e)}$$

$$R_i = h_{ie} + h_{re} A_i (R_L + R_e) + R_e (1 - A_i) - R_e h_{re}$$

$$A_v = \frac{A_i R_L}{R_i}$$

$$R_o = \frac{1 + h_{fe}}{h_{oe}} + \frac{(R_s + h_{ie})(1 + h_{oe} R_e)}{h_{oe} R_e} \text{ and } Y_o = \frac{1}{R_o}$$

Hybrid model

$$A_i = -\frac{h_{fe}}{1 + h_{oe}R_L}$$

$$R_i = \frac{v_b}{i_b} = h_{ie} + h_{re} A_i R_L$$

$$A_v = \frac{A_i R_L}{R_i}$$

$$Y_0 = h_{oe} - \frac{h_{fe} h_{re}}{R_s + h_{ie}} \text{ and } R_0 = \frac{1}{Y_0}$$

Approximate Hybrid model


$$A_i = -h_{fe}$$

$$R_i = h_{ie} + (1 + h_{fe})R_e$$

$$A_v = \frac{A_i R_L}{R_i} = \frac{-h_{fe} R_L}{h_{ie} + (1 + h_{fe})R_e}$$

$$Y_0 = 0, \text{ and } R_0 = \infty$$

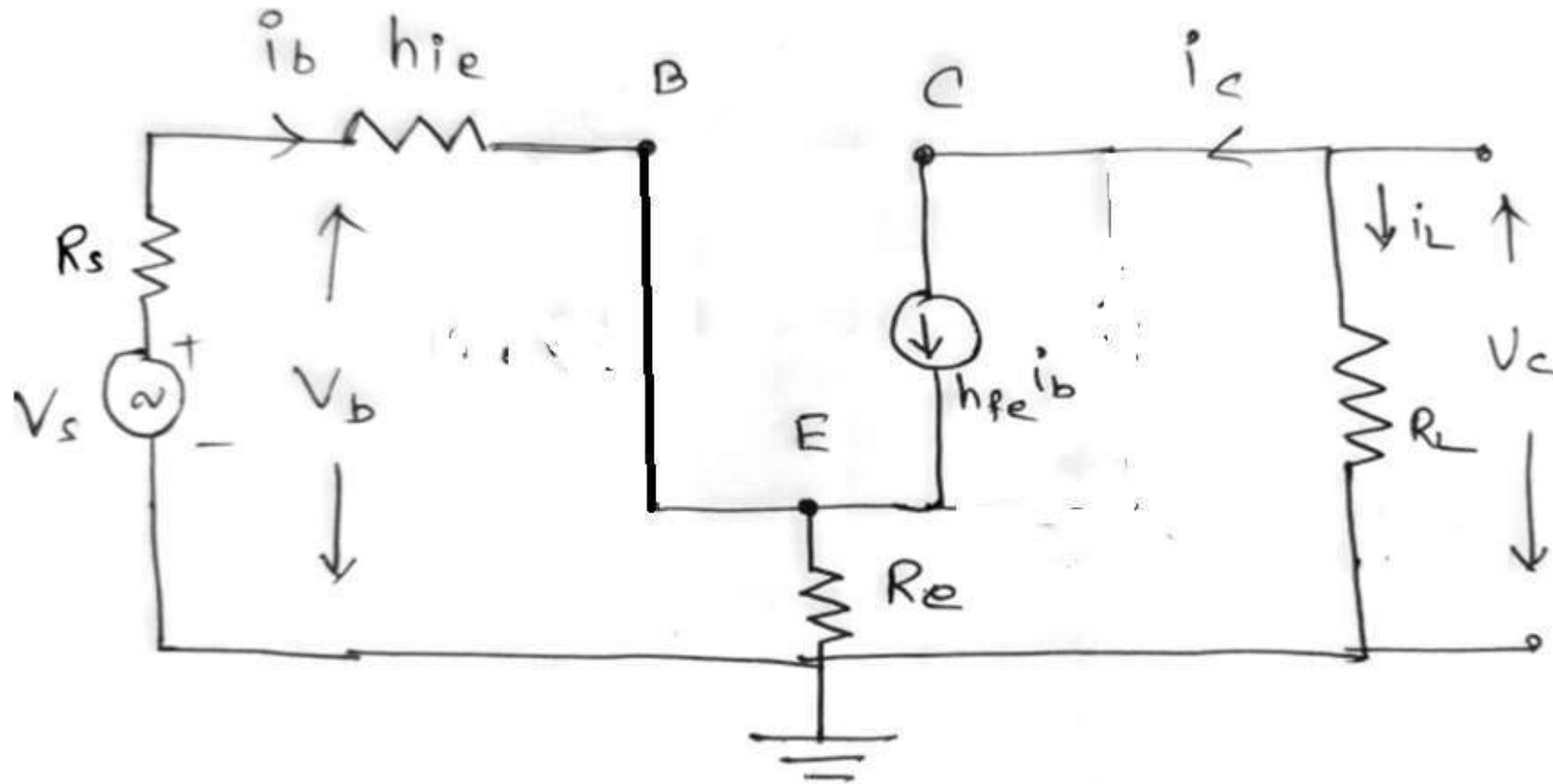CE Amplifier With Emitter Resistance (Using Approximate Hybrid Model)



CE Amplifier With Emitter Resistance (Using Approximate Hybrid Model)

$$A_i = \frac{h_{oe}R_e - h_{fe}}{1 + h_{oe}(R_L + R_e)}$$

$$R_i = h_{ie} + h_{re}A_i(R_L + R_e) + R_e(1 - A_i) - R_e h_{re}$$

$$A_v = \frac{A_i R_L}{R_i}$$

$$R_0 = \frac{1 + h_{fe}}{h_{oe}} + \frac{(R_s + h_{ie})(1 + h_{oe}R_e)}{h_{oe}R_e} \text{ and } Y_0 = \frac{1}{R_0}$$




$$A_i = -h_{fe}$$

$$R_i = h_{ie} + (1 + h_{fe})R_e$$


$$A_v = \frac{A_i R_L}{R_i} = \frac{-h_{fe} R_L}{h_{ie} + (1 + h_{fe})R_e}$$

$$Y_0 = 0, \text{ and } R_0 = \infty$$


CB Amplifier(Using Hybrid Model)

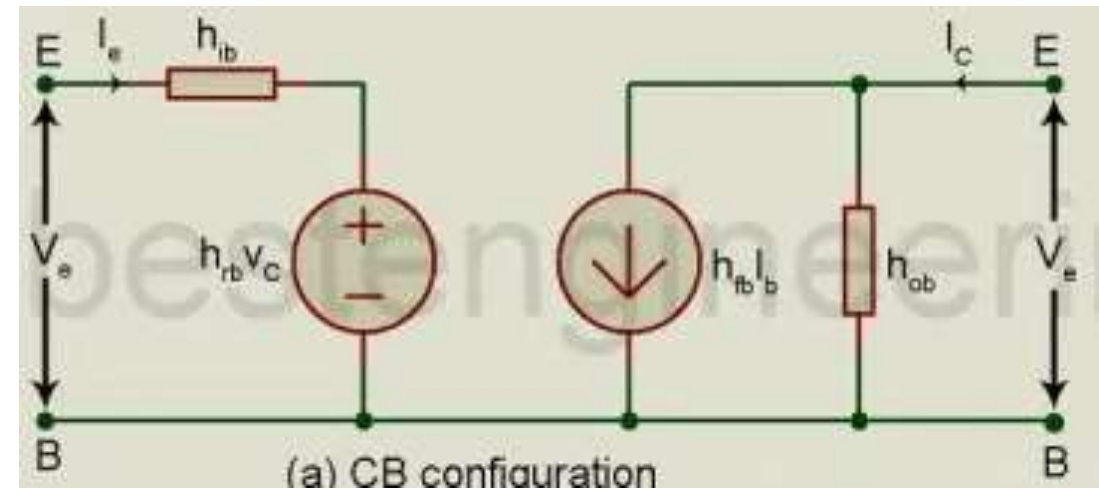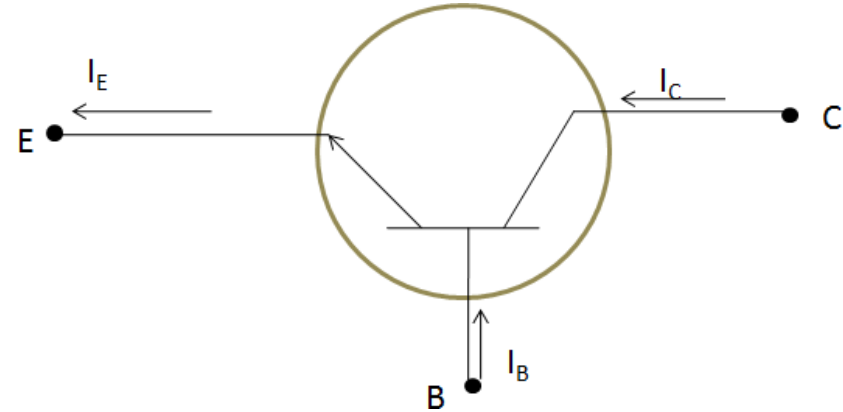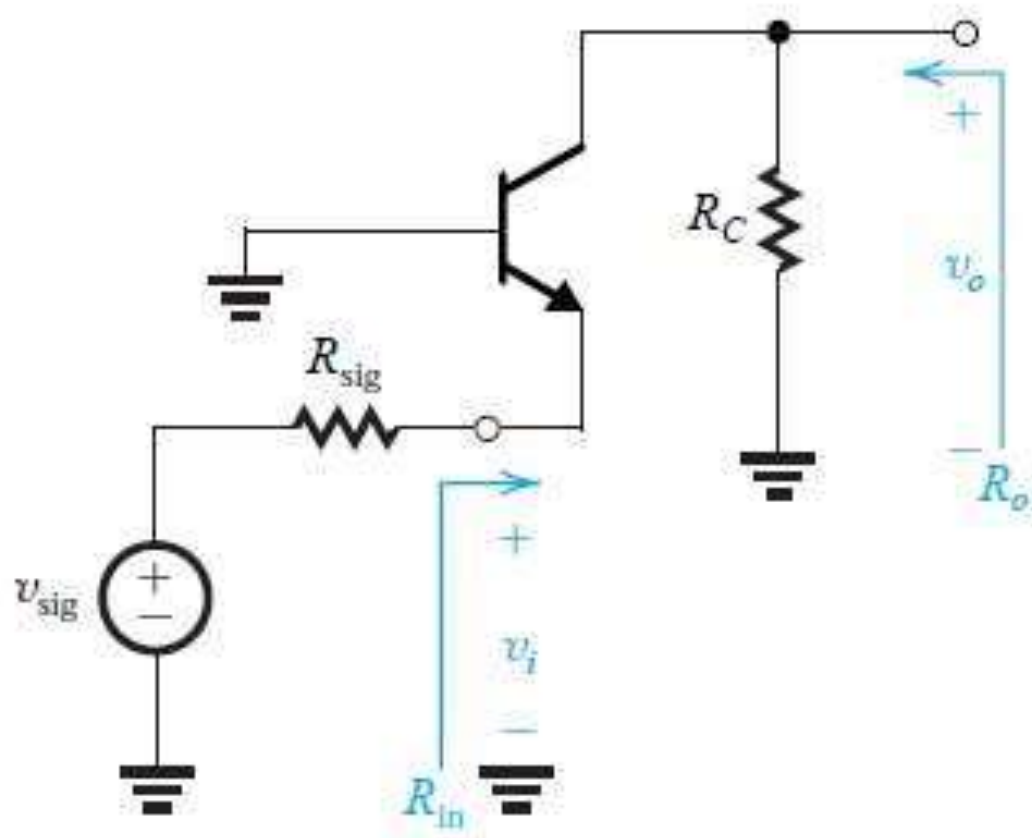

CB Amplifier(Using Hybrid Model)

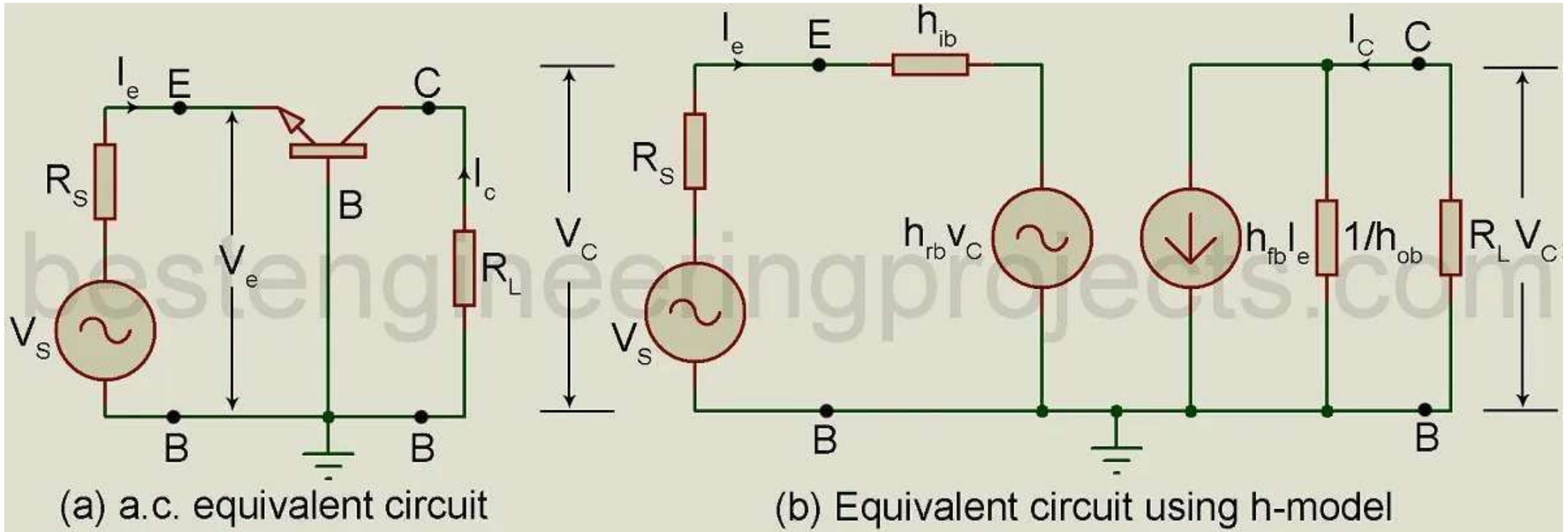

CB Amplifier (Using Hybrid Model)

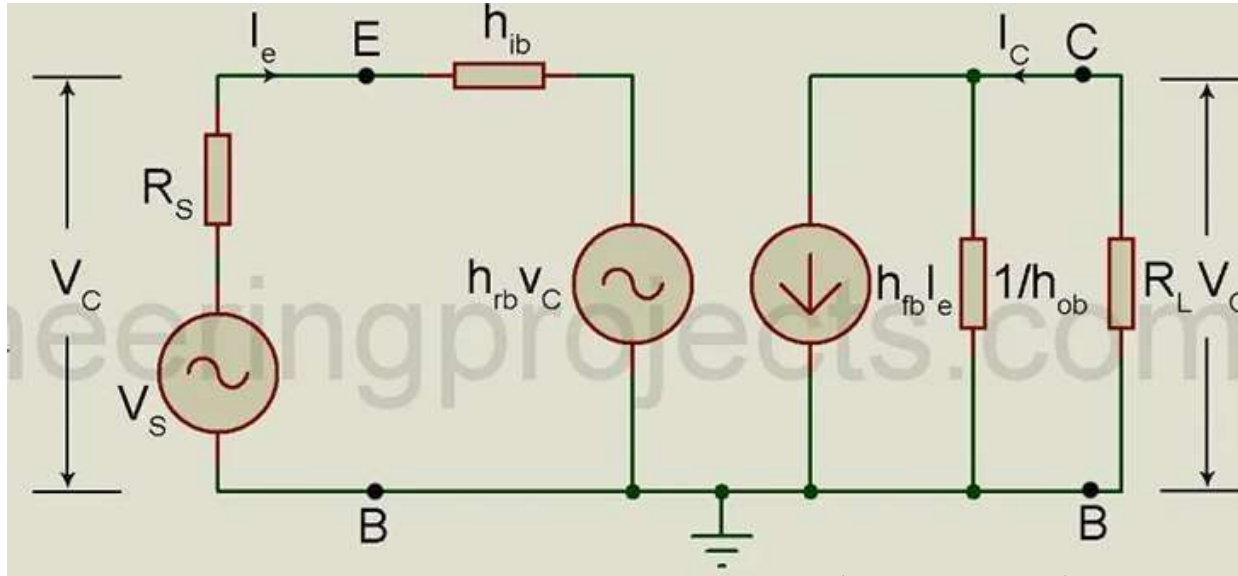

$$i_c = h_{fb} i_e + h_{ob} (-i_c R_L)$$

$$i_c (1 + h_{ob} R_L) = h_{fb} i_e$$


$$A_i = \frac{i_c}{i_e} = -\frac{i_c}{i_e}$$

$$i_c = h_{fb} i_e + h_{ob} v_c$$

$$v_c = i_c R_L = -i_c R_L$$

$$A_i = \frac{i_c}{i_e} = -\frac{h_{fb}}{1 + h_{ob} R_L}$$

CB Amplifier (Using Hybrid Model)

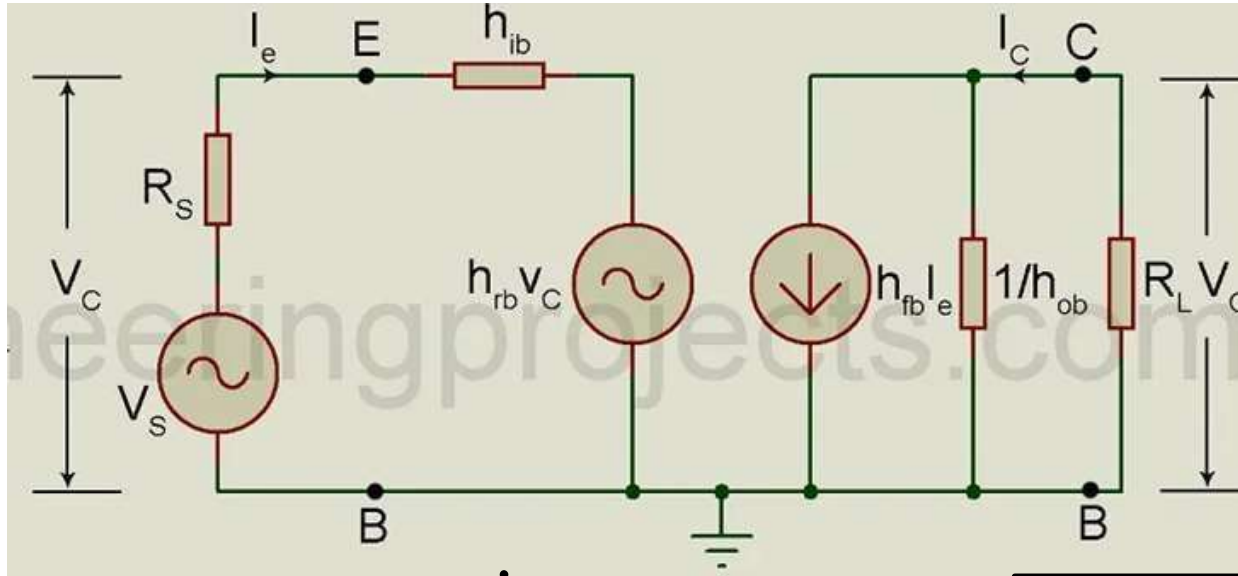

$$R_i = \frac{v_e}{i_e}$$

$$v_e = h_{ib} i_e + h_{rb} v_c$$

$$\text{But, } A_i = -\frac{i_c}{i_e} \Rightarrow i_c = -A_i i_e$$


$$v_c = i_L R_L = -i_c R_L = A_i i_e R_L$$

$$v_e = h_{ib} i_e + h_{rb} (A_i i_e R_L)$$

$$v_e = i_e (h_{ib} + h_{rb} A_i R_L)$$

$$\Rightarrow R_i = \frac{v_e}{i_e} = h_{ib} + h_{rb} A_i R_L$$

CB Amplifier (Using Hybrid Model)

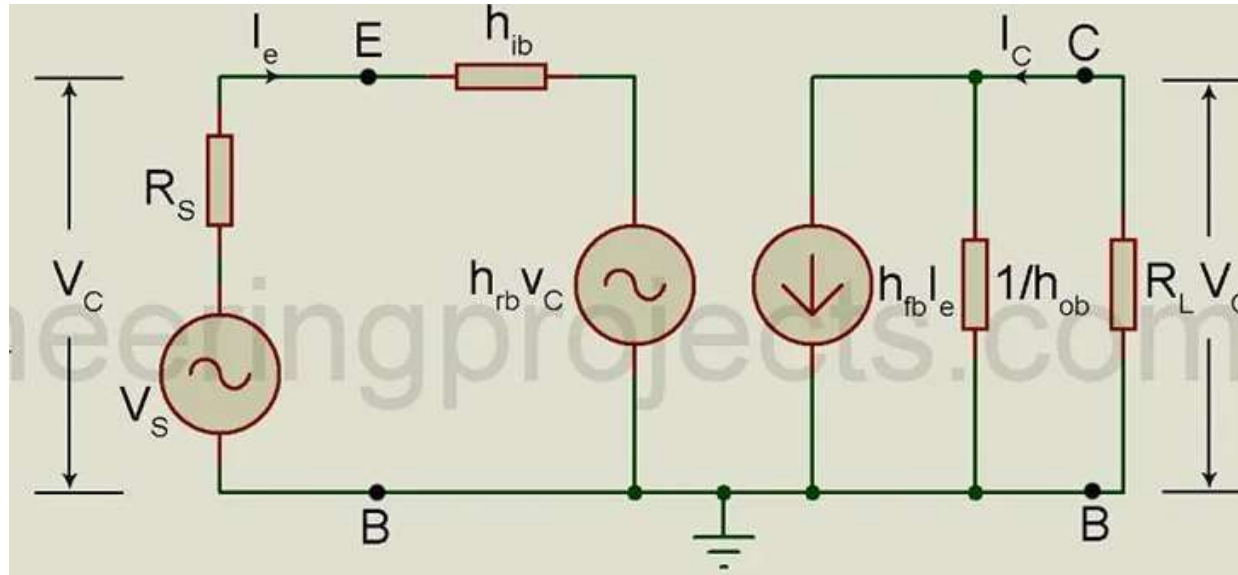

$$A_v = \frac{v_c}{v_e}$$


But, $A_i = -\frac{i_c}{i_e} \Rightarrow i_c = -A_i i_e$

$$v_c = i_L R_L = -i_c R_L = A_i i_e R_L$$

$$\frac{1}{R_i} = \frac{i_e}{v_e}$$

$$\Rightarrow A_v = \frac{v_c}{v_e} = \frac{A_i i_e R_L}{v_e} = \frac{A_i R_L}{R_i}$$

CB Amplifier (Using Hybrid Model)

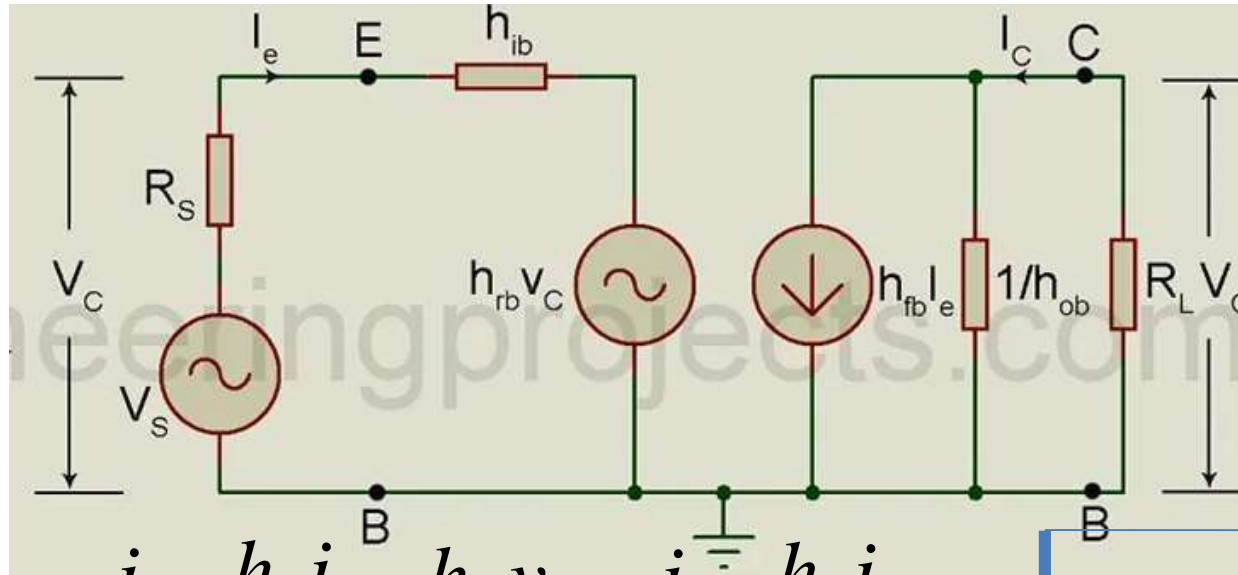

Output Admittance Y_o

$$Y_o = \frac{i_c}{v_c}$$

$$i_c = h_{fb} i_e + h_{ob} v_c$$

Dividing By V_c

$$\Rightarrow \frac{i_e}{v_c} = -\frac{h_{rb}}{R_s + h_{ib}}$$


$$\frac{i_c}{v_c} = \frac{h_{fb} i_e}{v_c} + \frac{h_{ob} v_c}{v_c} \Rightarrow \frac{i_c}{v_c} = \frac{h_{fb} i_e}{v_c} + h_{ob}$$

$$v_s = 0, R_s i_e + h_{ib} i_e + h_{rb} v_c = 0$$


$$(R_s + h_{ib}) i_e = -h_{rb} v_c$$

$$\Rightarrow Y_o = h_{ob} - \frac{h_{fb} h_{rb}}{R_s + h_{ib}} \text{ and } R_o = \frac{1}{Y_o}$$


CC Amplifier(Using Hybrid Model)

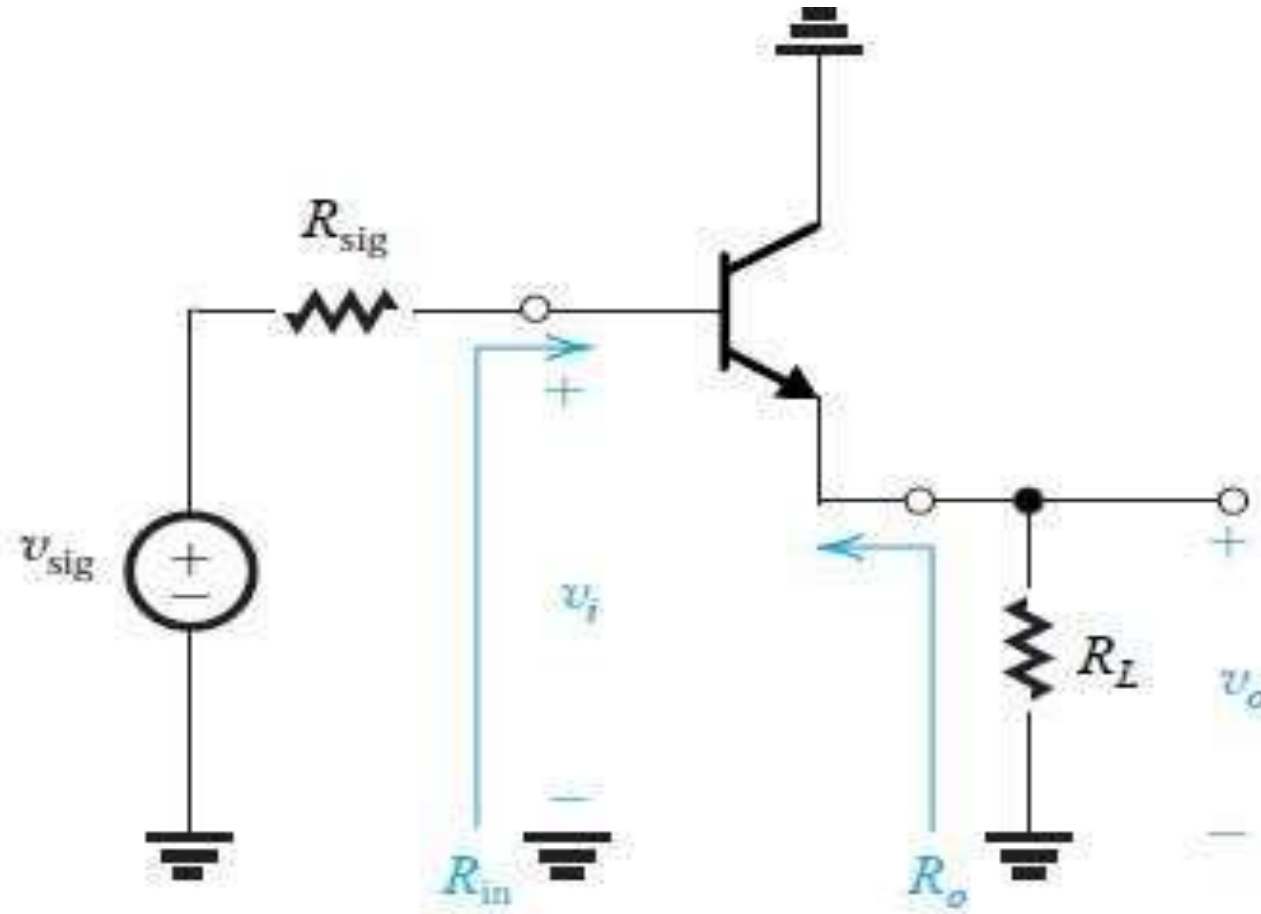

CB Amplifier(Using Hybrid Model)

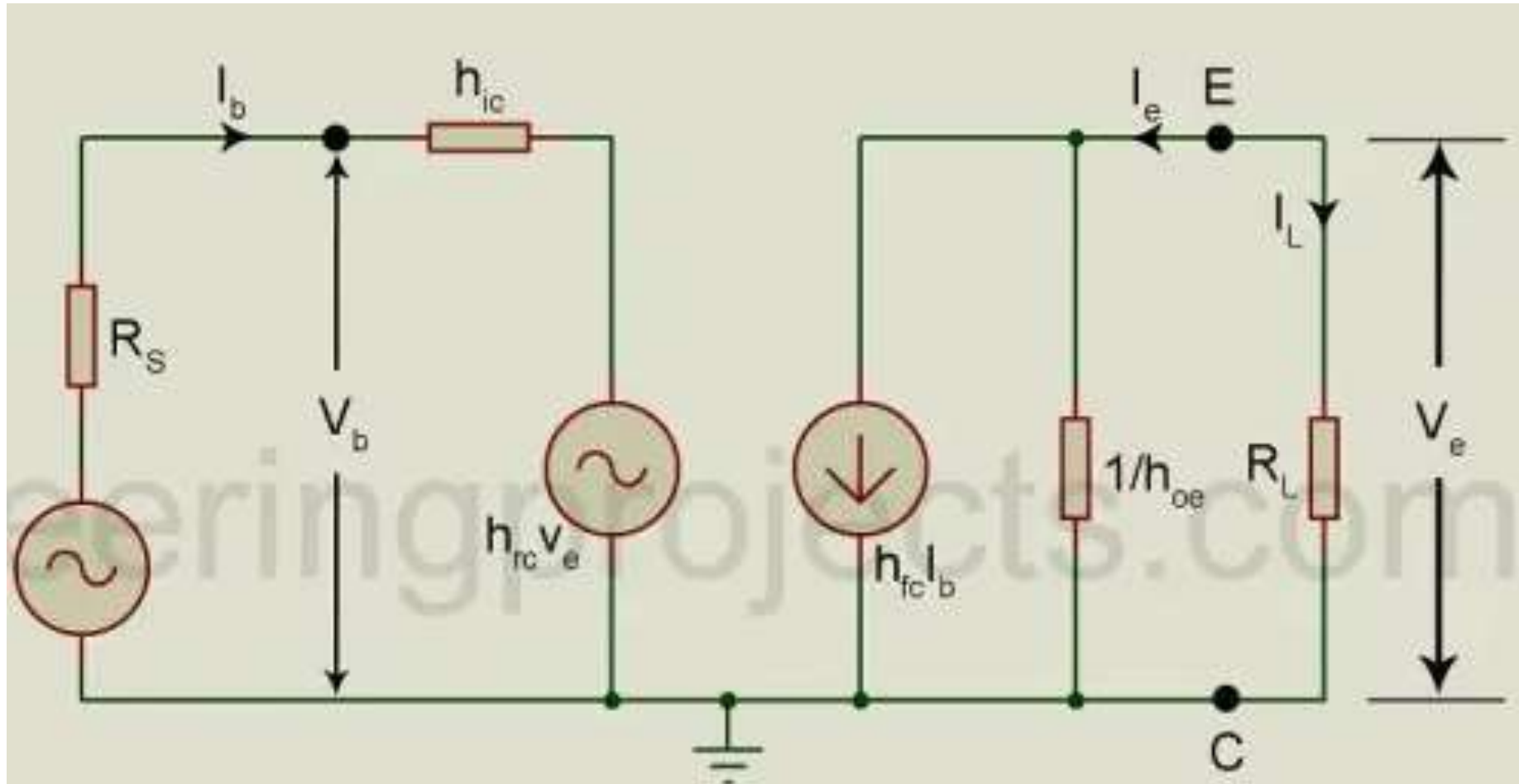

CB Amplifier (Using Hybrid Model)

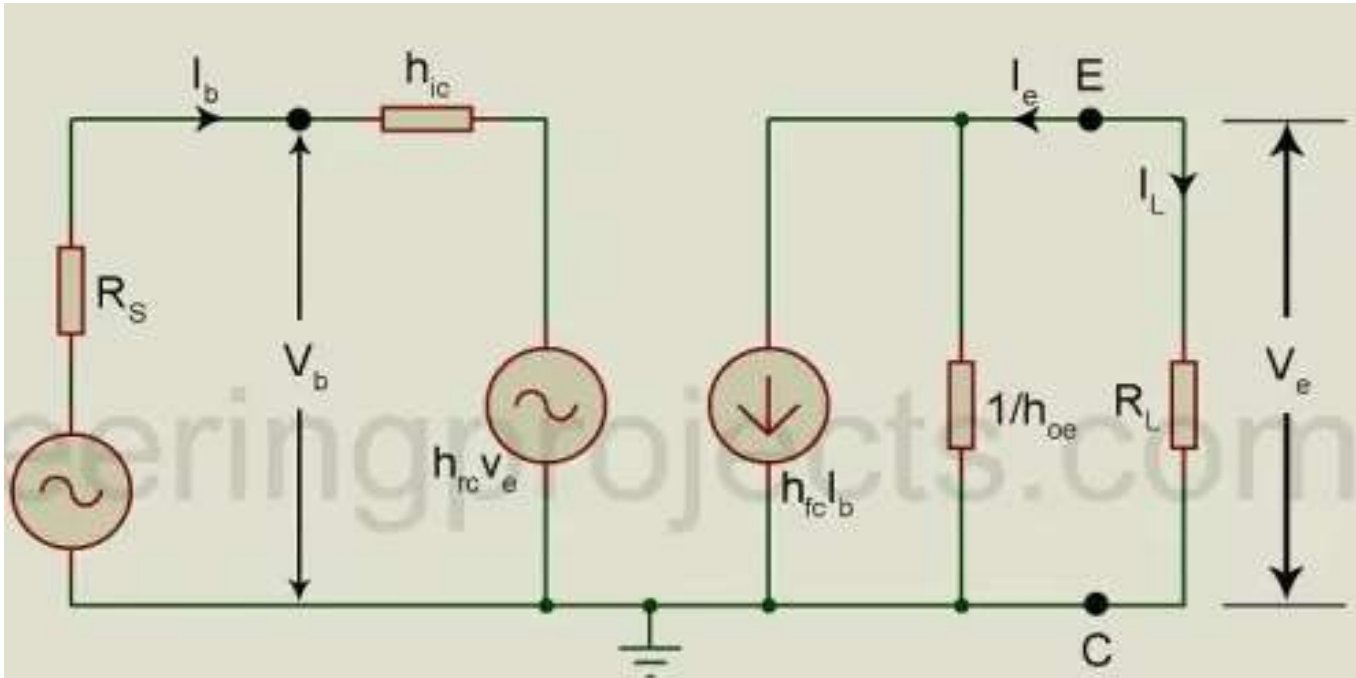

$$A_i = \frac{i_L}{i_b} = -\frac{i_e}{i_b}$$

$$i_e = h_{fc} i_b + h_{oc} v_e$$


$$v_c = i_L R_L = -i_e R_L$$

$$i_e = h_{fc} i_b + h_{oc} (-i_e R_L)$$

$$i_e (1 + h_{oc} R_L) = h_{fc} i_b$$

$$A_i = \frac{i_e}{i_b} = -\frac{h_{fc}}{1 + h_{oc} R_L}$$

CB Amplifier (Using Hybrid Model)

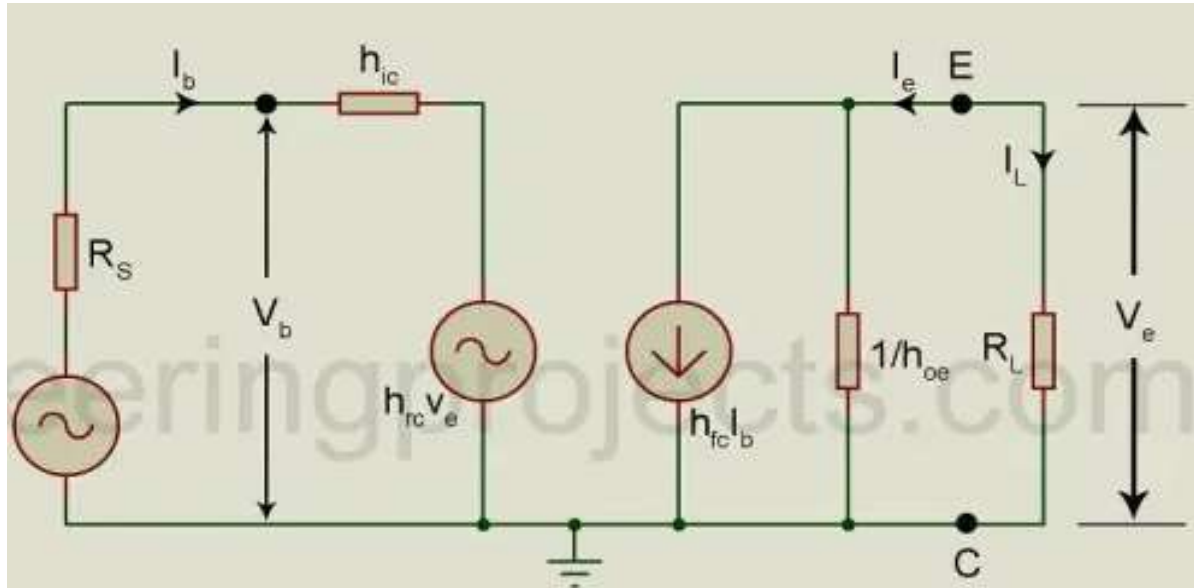

$$R_i = \frac{v_b}{i_b}$$

$$v_b = h_{ic} i_b + h_{rc} v_e$$

$$\text{But, } A_i = -\frac{i_e}{i_b} \Rightarrow i_e = -A_i i_b$$


$$v_e = i_L R_L = -i_e R_L = A_i i_b R_L$$

$$v_b = h_{ic} i_b + h_{rc} (A_i i_b R_L)$$

$$v_b = i_b (h_{ic} + h_{rc} A_i R_L)$$

$$\Rightarrow R_i = \frac{v_b}{i_b} = h_{ic} + h_{rc} A_i R_L$$

CB Amplifier (Using Hybrid Model)

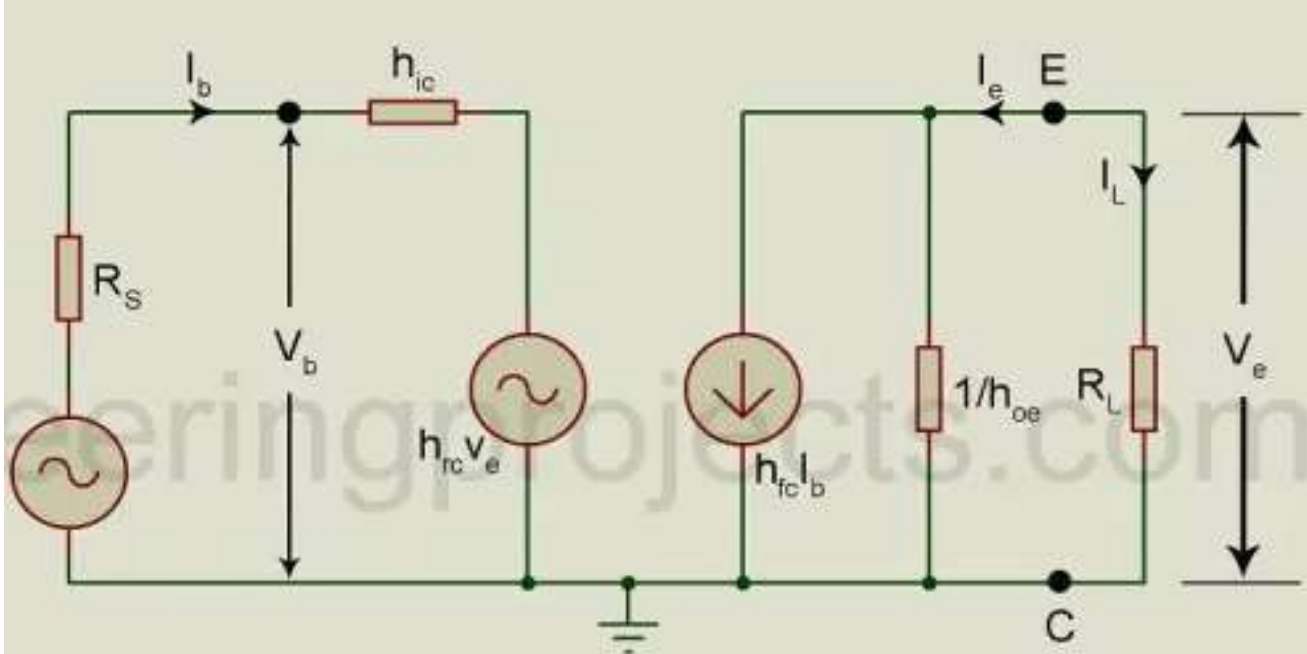

$$A_v = \frac{V_e}{V_b}$$


$$\text{But, } A_i = -\frac{i_e}{i_b} \Rightarrow i_e = -A_i i_b$$

$$V_e = i_L R_L = -i_e R_L = A_i i_b R_L$$

$$\frac{1}{R_i} = \frac{i_b}{V_b}$$

$$\Rightarrow A_v = \frac{V_e}{V_b} = \frac{A_i i_b R_L}{V_b} = \frac{A_i R_L}{R_i}$$

CB Amplifier (Using Hybrid Model)

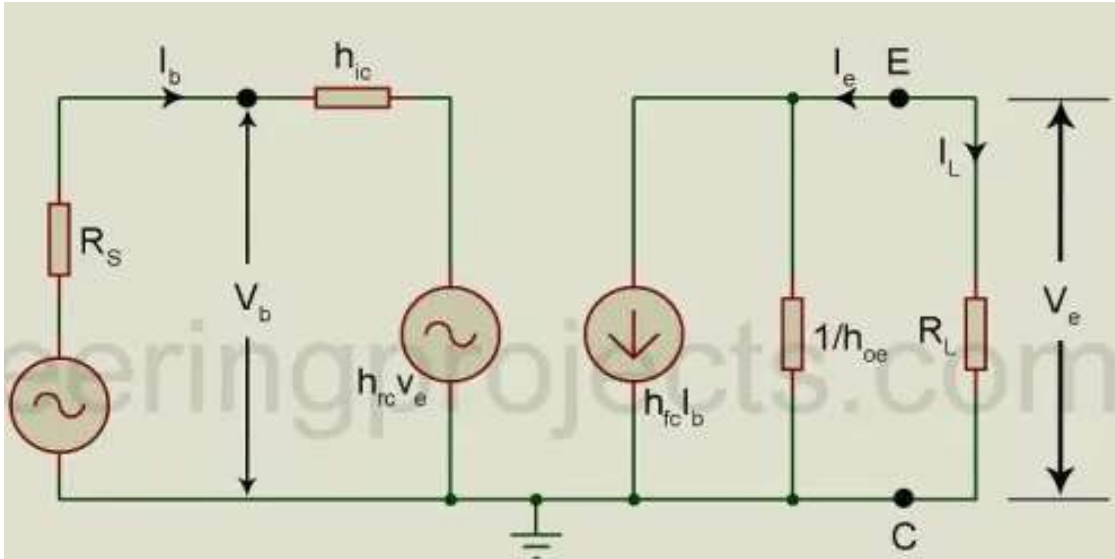

Output Admittance Y_o

$$Y_o = \frac{i_e}{v_e}$$

$$i_e = h_{fc} i_b + h_{oc} v_e$$

Dividing By V_e

$$\Rightarrow \frac{i_b}{v_e} = -\frac{h_{rc}}{R_s + h_{ic}}$$



$$\frac{i_e}{v_e} = \frac{h_{fc} i_b}{v_e} + \frac{h_{oc} v_e}{v_e} \Rightarrow \frac{i_e}{v_e} = \frac{h_{fc} i_b}{v_e} + h_{oc}$$

$$v_s = 0, R_s i_b + h_{ic} i_b + h_{rc} v_e = 0$$



$$(R_s + h_{ic}) i_b = -h_{rc} v_e$$

$$\Rightarrow Y_o = h_{oc} - \frac{h_{fc} h_{rc}}{R_s + h_{ic}} \text{ and } R_o = \frac{1}{Y_o}$$

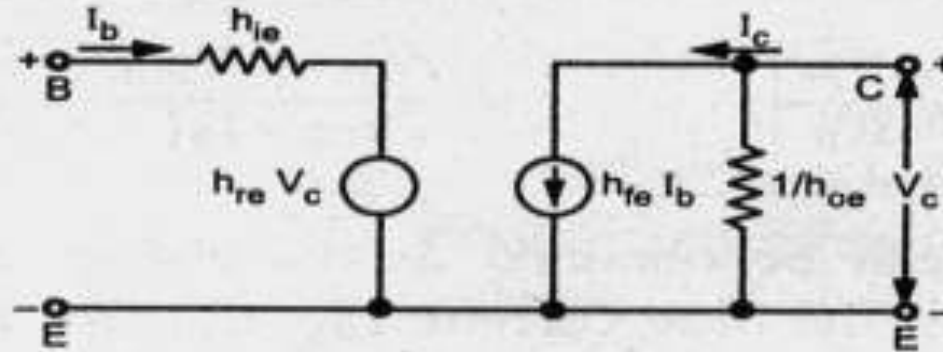
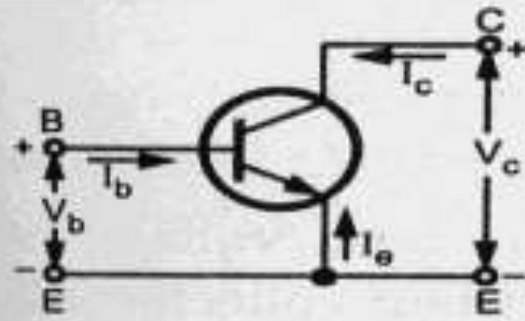
Hybrid Model and Equations for the transistor in three different configurations are given below.


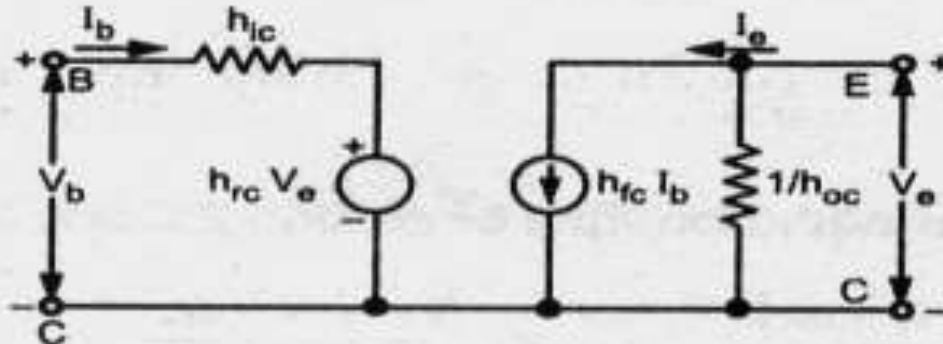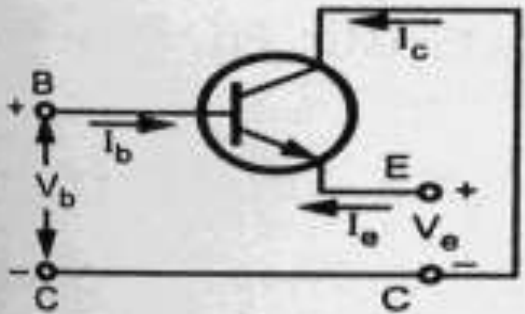
$$\begin{aligned} V_b &= h_{ie} I_b + h_{re} V_c \\ I_c &= h_{fe} I_b + h_{oe} V_c \end{aligned}$$


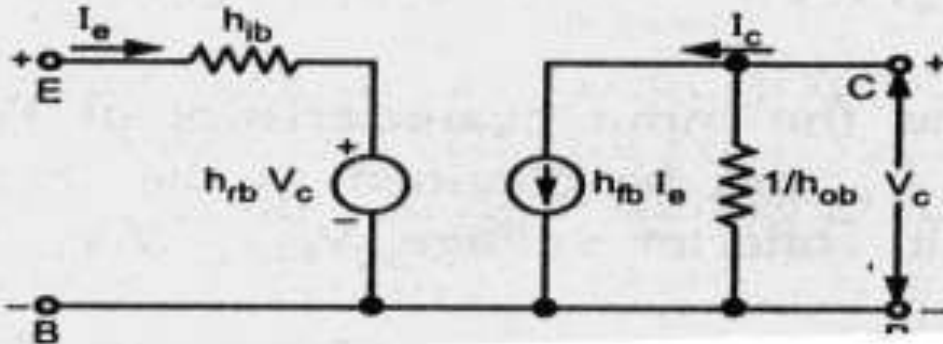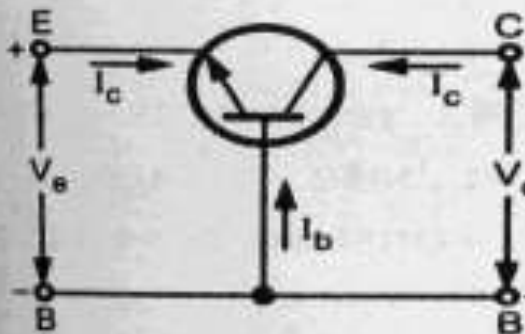
$$\begin{aligned} V_b &= h_{ic} I_b + h_{rc} V_e \\ I_e &= h_{fc} I_b + h_{oc} V_e \end{aligned}$$



$$\begin{aligned} V_e &= h_{ib} I_e + h_{rb} V_c \\ I_c &= h_{fb} I_e + h_{ob} V_c \end{aligned}$$

Conversion Formulae for Hybrid Parameters

CE to CB h-parameters	CE to CC h-parameters	CE h-parameters to r-parameters
$h_{ib} \approx \frac{h_{ie}}{1 + h_{fe}}$	$h_{ic} = h_{ie}$	$\alpha \approx \frac{h_{fe}}{1 + h_{fe}}$
$h_{rb} \approx \frac{h_{ie} h_{oe}}{1 + h_{fe}} - h_{re}$	$h_{rc} = 1 - h_{re}$	$r_c = \frac{1 + h_{fe}}{h_{oe}}$
$h_{fb} \approx \frac{h_{fe}}{1 + h_{fe}}$	$h_{fc} = 1 + h_{fe}$	$r_e = \frac{h_{ie}}{1 + h_{fe}} \approx r'_e$
$h_{ob} \approx \frac{h_{oe}}{1 + h_{fe}}$	$h_{oc} = h_{oe}$	$r_b = h_{ie} - \frac{h_{re}(1 + h_{fe})}{h_{oe}}$
		$r_{\pi} = h_{ie}$
		$\beta = h_{fe}$

TABLE 11.4

Configuration Parameter	Common Emitter, CE	Common Base, CB	Common Collector, CC	Equivalent T-Circuit
h_{ie}	1.1 k Ω	$\frac{h_{ib}}{1 + h_{fb}}$	h_{ic}^*	$r_b + \frac{r_e}{1 - a}$
h_{re}	2.5×10^{-4}	$\frac{h_{ib} h_{ob}}{1 + h_{fb}} - h_{rb}$	$1 - h_{rc}^*$	$\frac{r_e}{r_c (1 - a)}$
h_{fe}	50	$-\frac{h_{fb}}{1 + h_{fb}}$	$-(1 + h_{fc})^*$	$\frac{a}{1 - a}$
h_{oe}	25 μ S (μ A/V)	$\frac{h_{ob}}{1 + h_{fb}}$	h_{oc}^*	$\frac{1}{r_c (1 - a)}$
h_{ib}	$\frac{h_{ie}}{1 + h_{fe}}$	21.6 Ω	$-h_{ic}/h_{fc}$	$r_e + (1 - a) r_b$
h_{rb}	$\frac{h_{ie} h_{oe}}{1 + h_{fe}} - h_{re}$	2.9×10^{-4}	$h_{rc} - \frac{h_{ic} h_{oc}}{h_{fc}} - 1$	r_b/r_c
h_{fb}	$-\frac{h_{fe}}{1 + h_{fe}}$	-0.98	$-\frac{1 + h_{fc}}{h_{fc}}$	$-a$
h_{ob}	$\frac{h_{oe}}{1 + h_{fe}}$	0.49 μ S (μ A/V)	$-\frac{h_{oc}}{h_{fc}}$	$1/r_c$
h_{ic}	h_{ie}^*	$\frac{h_{ib}}{1 + h_{fb}}$	1.1 k Ω	$r_b + \frac{r_e}{1 - a}$
h_{rc}	$1 - h_{re} = 1^*$	1	1	$1 - \frac{r_e}{r_c (1 - a)}$
h_{fc}	$-(1 + h_{fe})^*$	$-\frac{1}{1 + h_{fb}}$	-51	$-\frac{1}{1 - a}$
h_{oc}	h_{oe}^*	$\frac{h_{ob}}{1 + h_{fb}}$	25 μ S (μ A/V)	$\frac{1}{r_c (1 - a)}$
a	$\frac{h_{fe}}{1 + h_{fe}}$	$-h_{fb}$	$\frac{1 + h_{fc}}{h_{fc}}$	0.98
r_c	$\frac{1 + h_{fe}^*}{h_{oe}}$	$\frac{1}{h_{ob}}$	$-\frac{h_{fc}^*}{h_{oc}}$	2.04 M Ω
r_e	$\frac{h_{re}^*}{h_{oe}}$	$h_{ib} - \frac{h_{rb}}{h_{ob}} (1 + h_{fb})^*$	$\frac{1 - h_{rc}^*}{h_{oc}}$	10 Ω
r_b	$h_{ie} - \frac{h_{re}}{h_{oe}} (1 + h_{fe})^*$	$\frac{h_{rb}^*}{h_{ob}}$	$h_{ic} + \frac{h_{fc}}{h_{oc}} (1 - h_{rc})^*$	590 Ω

* Stands for exact.