

The current in a circuit is given by $i = 42.42 \sin(628)t$ Calculate

- i) Frequency
- ii) RMS Value
- iii) Average Value
- iv) Form Factor

$$i = I_m \sin \omega t$$

$$i = 42.42 \sin(628t)$$

$$I_m = 42.42 \text{ A}$$

$$\omega = 628$$

$$2\pi f = 628$$

$$f = \frac{628}{2\pi} = 99.95 \text{ Hz}$$
$$\approx 100 \text{ Hz}$$


$$\text{RMS} \Rightarrow I_{\text{rms}} = \frac{I_m}{\sqrt{2}} = \frac{42.42}{\sqrt{2}} = 30 \text{ A}$$

$$\text{Average} \Rightarrow I_{\text{ave}} = \frac{2I_m}{\pi} = \frac{2 \times 42.42}{\pi} = 27 \text{ A}$$

$$\text{Form factor} = \frac{I_{\text{rms}}}{I_{\text{ave}}} = \frac{I_m / \sqrt{2}}{2I_m / \pi} = \frac{30}{27} = 1.11$$

$$\text{Peak factor} = \frac{I_m}{I_{\text{rms}}} = \frac{I_m}{I_m / \sqrt{2}} = \sqrt{2} = 1.414$$

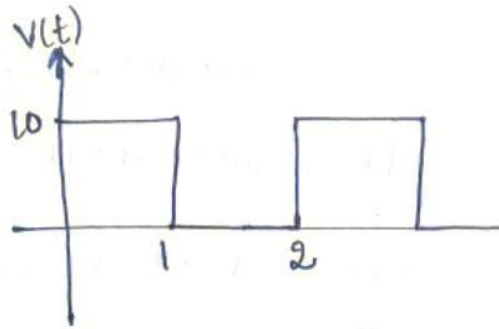2. Calculate the average and RMS value of the square wave.




$$V_{rms} = \sqrt{\frac{\int_0^2 v^2(t) dt}{2}} = \sqrt{\frac{\int_0^1 10^2 dt + \int_1^2 0^2 dt}{2}}$$

$$= \sqrt{\frac{100(t)_0^1 + 0}{2}} = \sqrt{\frac{50}{2}} = 7.071V.$$

$$V_{ave} = \frac{\int_0^2 v(t) dt}{2} = \frac{\int_0^1 10 dt + \int_1^2 0 dt}{2}$$

$$= \frac{10(t)_0^1}{2} = \frac{10[1]}{2} = 5V.$$

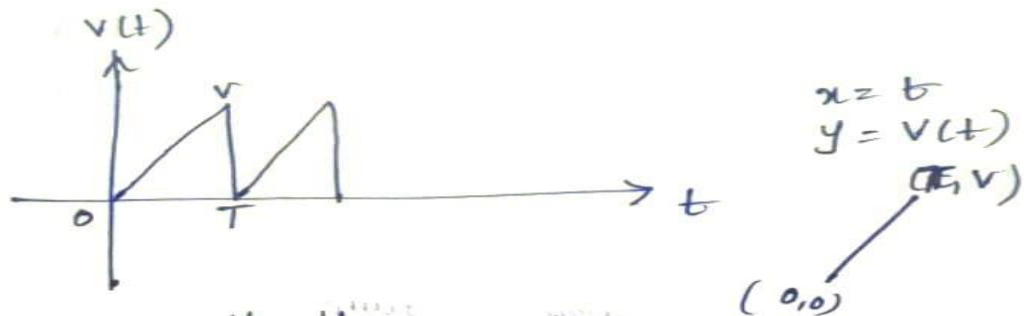3. Calculate the form factor and peak factor of a triangular wave in which the voltage rises uniformly from 0 to V volts in time T seconds and completes the cycle by instant fall back to zero ?



$$y - y_1 = \frac{y_2 - y_1}{x_2 - x_1} (x - x_1)$$

$$y - 0 = \frac{V - 0}{T - 0} (t - 0)$$

$$V(t) = \frac{V}{T} \cdot t$$

$$V_{rms} = \sqrt{\frac{\int_0^T \left(\frac{V}{T}\right)^2 t^2 dt}{T}} = \sqrt{\frac{\frac{V^2}{T^2} \left[\frac{t^3}{3}\right]_0^T}{T}}$$

$$= \sqrt{\frac{V^2 \cdot T}{T^2 \cdot 3}} = \frac{V}{\sqrt{3}}$$

$$V_{ave} = \frac{\int_0^T V(t) dt}{T} = \int_0^T \frac{V}{T} \cdot t dt$$

$$= \frac{V}{T^2} \int_0^T t dt = \frac{V}{T^2} \cdot \frac{t^2}{2} = \frac{V}{2}$$

$$\text{Form factor} = \frac{V_{rms}}{V_{ave}} = \frac{V/\sqrt{3}}{V/2} = 1.154$$

$$\text{Peak factor} = \frac{V_m}{V_{rms}} = \frac{V}{V/\sqrt{3}} = \sqrt{3} = 1.732$$

The current drawn by a pure capacitance of $20\mu\text{F}$ is 1.382 A from 220V ac supply, find the supply frequency?

$$C = 20\mu\text{F}$$

$$I = 1.382\text{ A}$$

$$V = 220\text{V}$$

$$Z = X_C = \frac{V}{I} = \frac{220}{1.382} = 159\Omega$$

$$X_C = \frac{1}{2\pi fL}$$

$$f = \frac{1}{2\pi X_C L} = 49.99\text{ Hz}$$

A 300 μF capacitor is connected across a 240V, 50Hz system. Determine i) the capacitance reactance ii) R.M.S value of current iii) Equations for voltages and currents

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(50)(300 \times 10^{-6})} = 10 \Omega$$

$$Z = R + j(X_L - X_C) = 0 + j(0 - 10) = -10j \\ = 10 \angle -90^\circ$$

$$I = \frac{V}{Z} = \frac{240}{10} = 24 \text{ A} \cdot (24 \angle +90^\circ)$$


$$V_m = \sqrt{2}V = \sqrt{2} \times 240 = 325 \text{ V}$$

$$I_m = \sqrt{2}I = \sqrt{2} \times 24 = 32.5 \text{ A}$$

$$V = V_m \sin \omega t = 325 \sin(100\pi t \pm \theta) \text{ V}$$

$$I = I_m \sin \omega t = 32 \sin(100\pi t + 90^\circ) \text{ A}$$

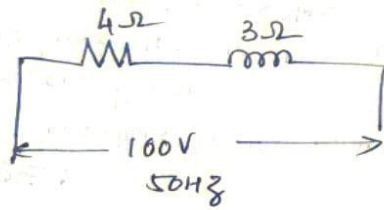A Series RL circuit connected with $R=4 \Omega$ and inductive reactance $X_L=3 \Omega$ is connected to 100 V, 50 Hz. Find the amount of current, power drawn by the circuit and power factor?



$$V = 100 \angle 0^\circ$$

$$Z = R + jX_L$$

$$Z = 4 + j3 = 5 \angle 36.86^\circ \Omega$$

$$I = \frac{V}{Z} = \frac{100 \angle 0^\circ}{5 \angle 36.86^\circ} = 20 \angle -36.86^\circ \text{ A}$$

$$P = I^2 R = (20)^2 \times 4 = 1600 \text{ W}$$

$$\cos \phi = \cos(-36.86^\circ) = 0.8 \text{ Lagging}$$

$$\text{power} \Rightarrow P = V \cdot I \cdot \cos \phi$$

$$= 100 \times 20 \times 0.8$$

$$= 1600 \text{ watts.}$$

- ③ Write the polar form of the voltage $v(t) = \sin(10\pi t + \frac{\pi}{3})$. obtain its rectangular form.

Sol:- $v(t) = \sin(10\pi t + \frac{\pi}{3})$
 $v(t) = V_m \sin(\omega t + \theta)$

By comparison,

$$V_m = 1 \quad \omega = 10\pi \quad \theta = \frac{\pi}{3} = 60^\circ$$

$$\text{voltage in polar form} = V_{ms} \angle \theta = \frac{V_m}{\sqrt{2}} \angle \theta$$

$$\boxed{V = \frac{1}{\sqrt{2}} \angle 60^\circ \text{ V}} \quad \text{polar form}$$

$= 0.707 \angle 60^\circ \text{ V}$

$$\text{voltage in rectangular form} = \frac{1}{\sqrt{2}} \cos 60^\circ + j \frac{1}{\sqrt{2}} \sin 60^\circ$$

$$= 0.707 \cos 60^\circ + j 0.707 \sin 60^\circ$$


$$\boxed{V = 0.354 + j 0.612 \text{ V}} \quad \text{Rectangular form.}$$

A series circuit of $R=10\Omega$, $X_c=15\Omega$ has an applied phase voltage $V=50 \angle -90^\circ$ Vrms. Find the real power, reactance power, and power factor?

Resistance (R) = 10Ω

Capacitive reactance (X_c) = 15Ω

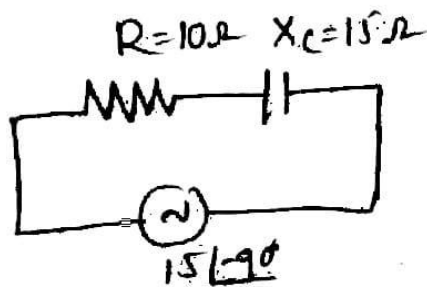Applied phase voltage (V) = $50 \angle -90^\circ$ Vrms



$$\begin{aligned} Z &= R + jX_c \\ &= 10 + j(-15) \\ Z &= \sqrt{10^2 + 15^2} \tan^{-1}\left(\frac{-15}{10}\right) \\ &= 18.02 \tan^{-1}(15/10) \\ Z &= 18.02 \angle 56.3^\circ \end{aligned}$$

$$I_{rms} = \frac{V_{rms}}{Z} = \frac{50}{18} = 2.7 \text{ A}$$

$$\begin{aligned} \text{Real power} &= V_{rms} \times I_{rms} \times \cos\phi = 50 \times 2.7 \times \cos(56.3^\circ) \\ &= 99 \text{ W} \end{aligned}$$

$$\text{Reactive power} = V_{rms} \times I_{rms} \times \sin\phi = 109 \text{ VAR}$$

$$\text{Power factor} = \cos(\phi) = \cos(56.3^\circ) = 0.547$$