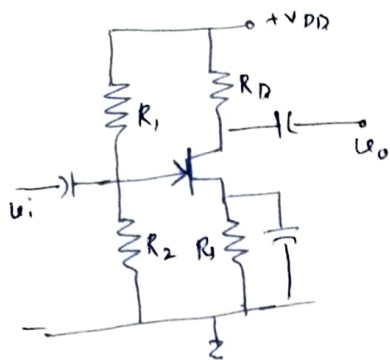


Voltage-Divider Bias



$$V_G = \frac{R_2}{R_1 + R_2} V_{DD}$$

$$V_{GS} = V_G - V_S$$

$$= V_G - I_D R_S$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$V_D = V_{DD} - I_D R_D$$

Given $V_{DD} = 22V$, $R_1 = 80k\Omega$, $R_2 = 330k\Omega$, $R_D = 2.2k\Omega$, $R_S = 1.8k\Omega$

$I_{D1} = 8mA$, $V_P = -4V$

$$V_G = V_{DD} \cdot \frac{R_2}{R_1 + R_2} = 6V; \quad V_{GS} = V_G - V_S = 6 - I_D \times 1.8k$$

$$I_D = I_{D1} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 8 \left(1 - \frac{6 - 1.8 I_D}{-4}\right)^2$$

$$I_{D1} = 3.98mA \rightarrow V_{GS1} = -1.6V \quad \checkmark$$



$$I_{D2} = 7.7mA \rightarrow V_{GS2} = -7.86V \quad \times$$

$$V_S = I_D R_S = 3.98 \times 1.8 = 7.16V$$

$$V_D = V_{DD} - I_D R_D = 22 - (3.98mA)(2.2k) \\ = 13.24V$$

$$V_{DS} = V_D - V_S = 13.24 - 7.16 = 6V$$


Small signal model

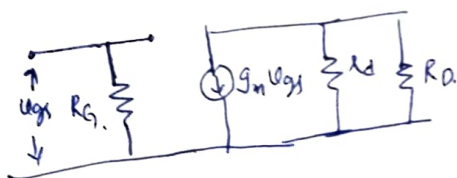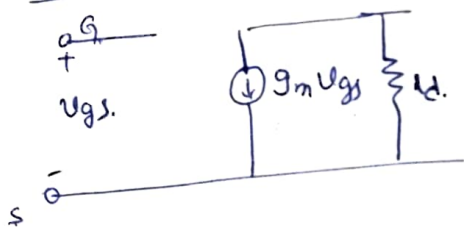

$$R_i = R_G$$

$$R_o = R_D \parallel R_L$$

Common Source Amp

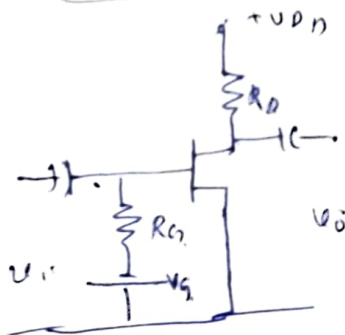

$$A_v = \frac{V_o}{V_i} = - \frac{g_m V_{gs} (R_D \parallel R_L)}{V_{gs}} \\ = -g_m (R_D \parallel R_L)$$