



AY-2025-2026
ODD SEM

Department of ECE

ANALOG ELECTRONIC CIRCUIT DESIGN
23EC2104

Topic:

**HYBRID MODEL FOR BJT
CONFIGURATIONS-CE**

Session - 08

SESSION CONTENT

- Hybrid Model for BJT Configurations-CE

AIM OF THE SESSION



To analyze and understand the Hybrid- π model for the Common Emitter (CE) configuration of a BJT and apply it in small-signal amplifier circuit analysis.

INSTRUCTIONAL OBJECTIVES

The Session is designed to:

1. Explain the concept of the Hybrid- π model for BJTs.
2. Identify the key elements of the Hybrid- π equivalent circuit.
3. Describe the role of each parameter (r_{π} , g_m , r_o) in CE configuration.
4. Apply the model to analyze small-signal behavior of CE amplifiers.

LEARNING OUTCOMES

At the end of this session, learners will be able to:


1. Construct the Hybrid- π equivalent circuit for a given BJT CE configuration.
2. Use the model to calculate small-signal parameters and performance metrics.
3. Understand how the base-emitter resistance (r_{π}) and transconductance (g_m) influence signal gain.





Basic BJT Amplifier Configurations

- Common-Emitter (CE) amplifier without and with emitter resistance
- Common-Base (CB) amplifier
- Common-Collector (CC) amplifier or Emitter Follower

Hybrid Equivalent Model

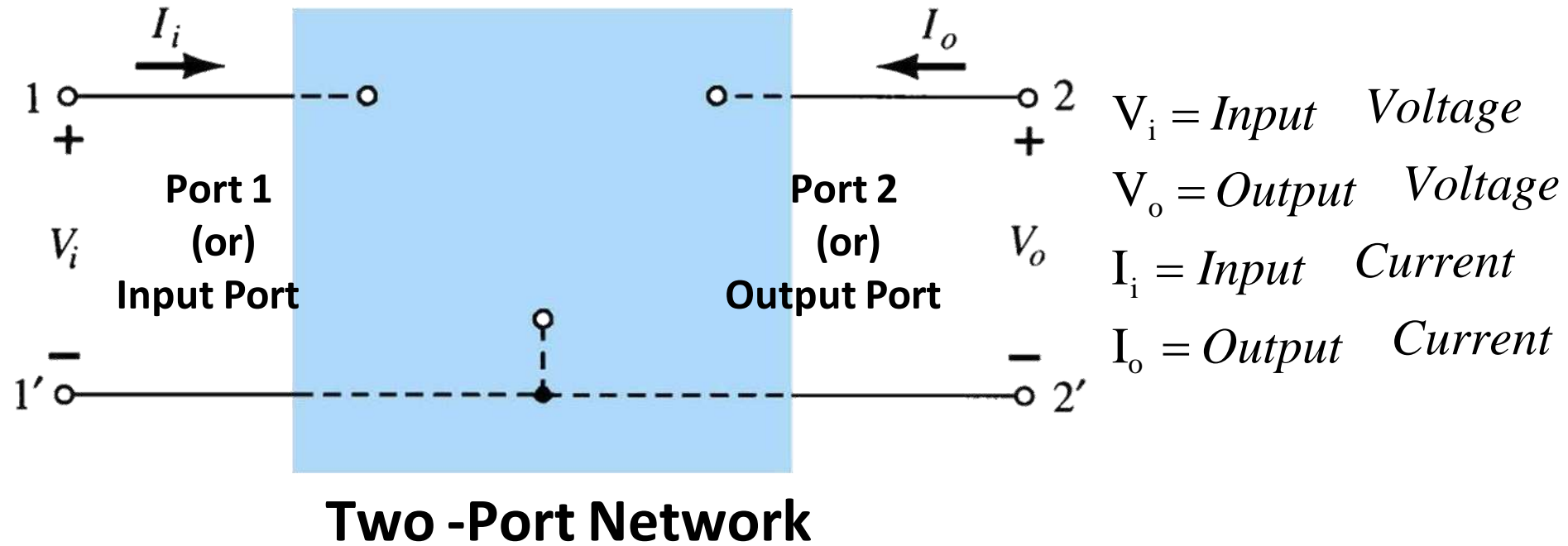


Determination of Hybrid Parameters

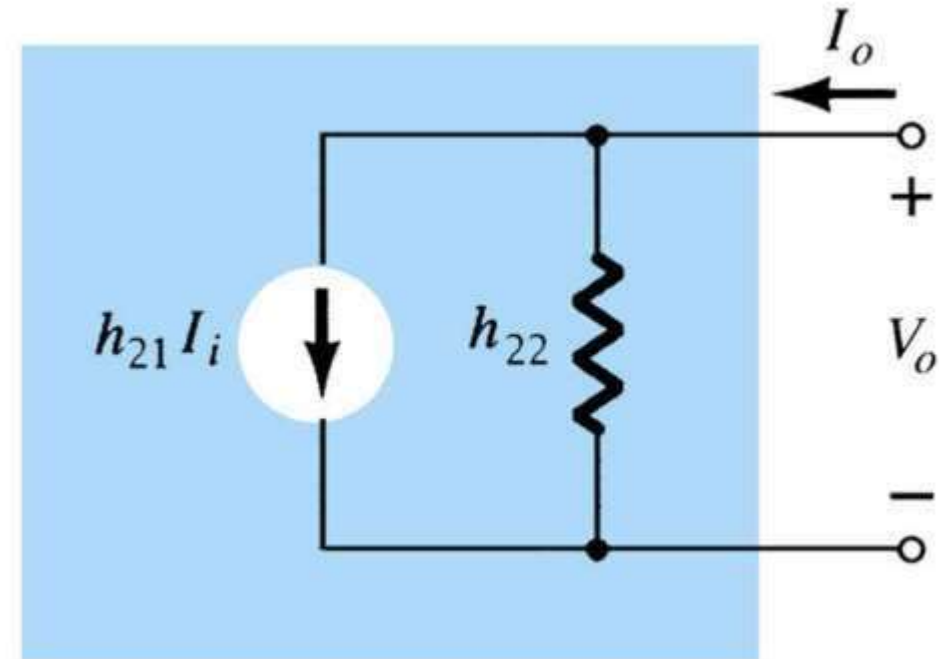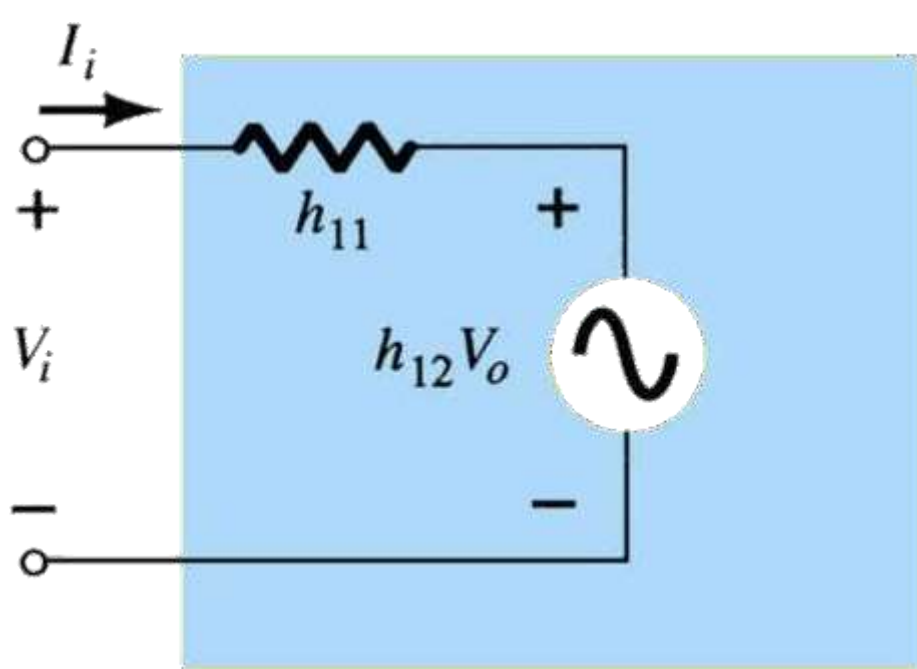

$$V_i = h_{11}I_i + h_{12}V_o \quad I_o = h_{21}I_i + h_{22}V_o$$

Determination of Hybrid Parameters

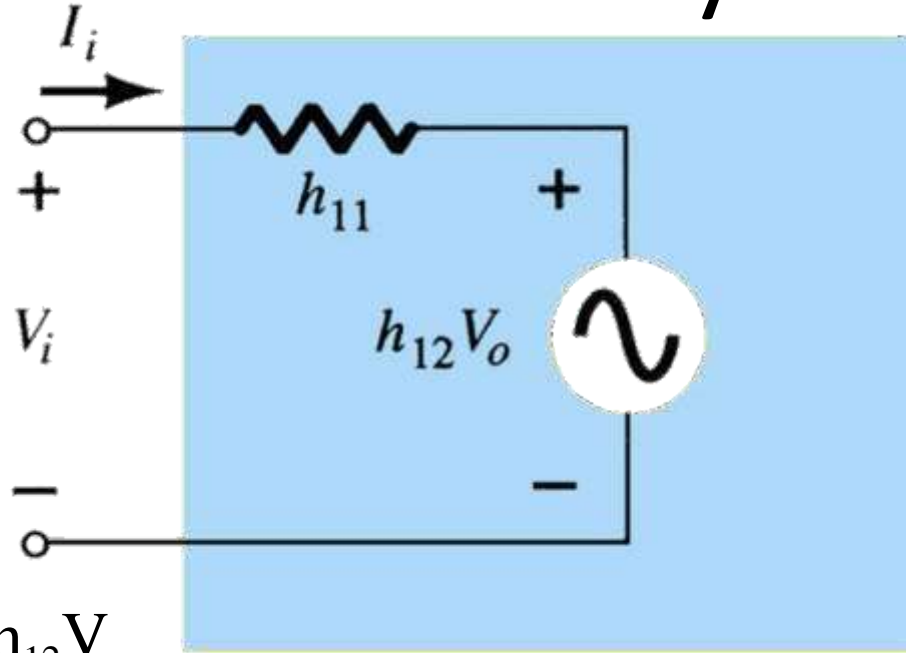


$h_{11} - \Omega$ and $h_{22} - \text{mhos}$
 $h_{12}, h_{21} - \text{Dimension Less.}$

$$V_i = h_{11} I_i + h_{12} V_o$$

$$h_{11} = \left. \frac{V_i}{I_i} \right|_{V_o=0V} = \textbf{Input Impedance} \text{ with output part short circuited} (\Omega)$$

$$h_{12} = \left. \frac{V_i}{V_o} \right|_{I_i=0V} = \textbf{Reverse Voltage Transfer Ratio} \text{ with input part open circuited}$$

Determination of Hybrid Parameters

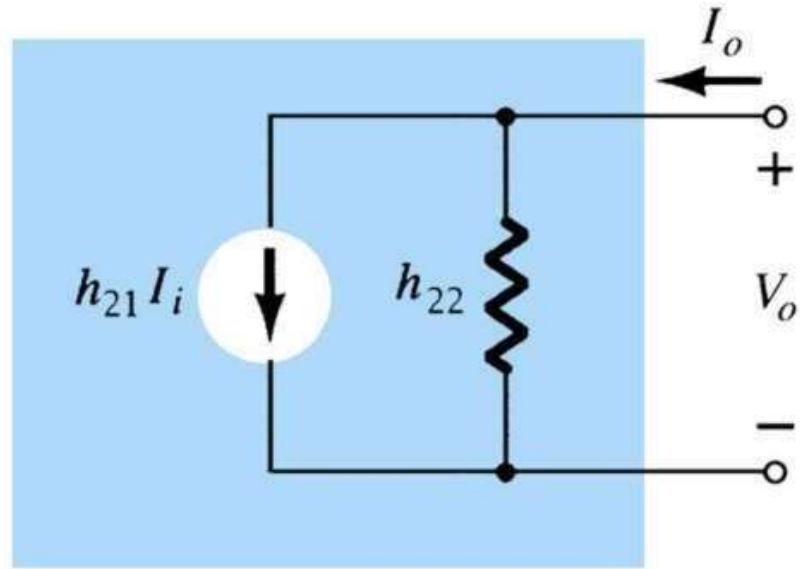


$$I_o = h_{21} I_i + h_{22} V_o$$

$h_{11} - \Omega$ and $h_{22} - \text{mhos}$
 $h_{12}, h_{21} - \text{Dimension Less.}$

$$h_{21} = \left. \frac{I_o}{I_i} \right|_{V_o=0V} = \text{Forward Current Gain with output part short circuited}$$

$$h_{22} = \left. \frac{I_o}{V_o} \right|_{I_i=0A} = \text{Output Admittance with input part open circuited (mhos)}$$

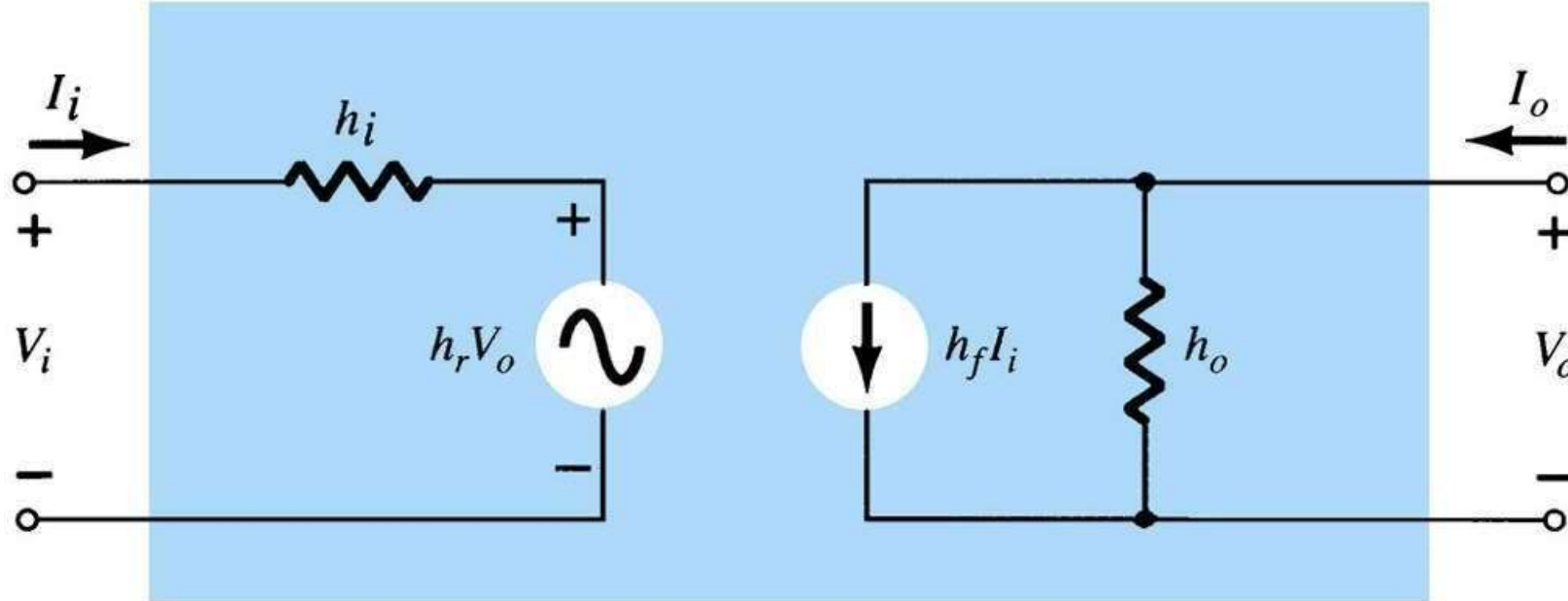General h-Parameters for any Transistor Configuration



$$\begin{aligned} V_i &= h_i I_i + h_r V_o \\ I_o &= h_f I_i + h_o V_o \end{aligned}$$


h_i = Input Resistance (V_i/I_i)

h_r = Reverse Transfer Voltage Ratio (V_i/V_o)

h_f = Forward Transfer Current Ratio (I_o/I_i)

h_o = Output Conductance (I_o/V_o)

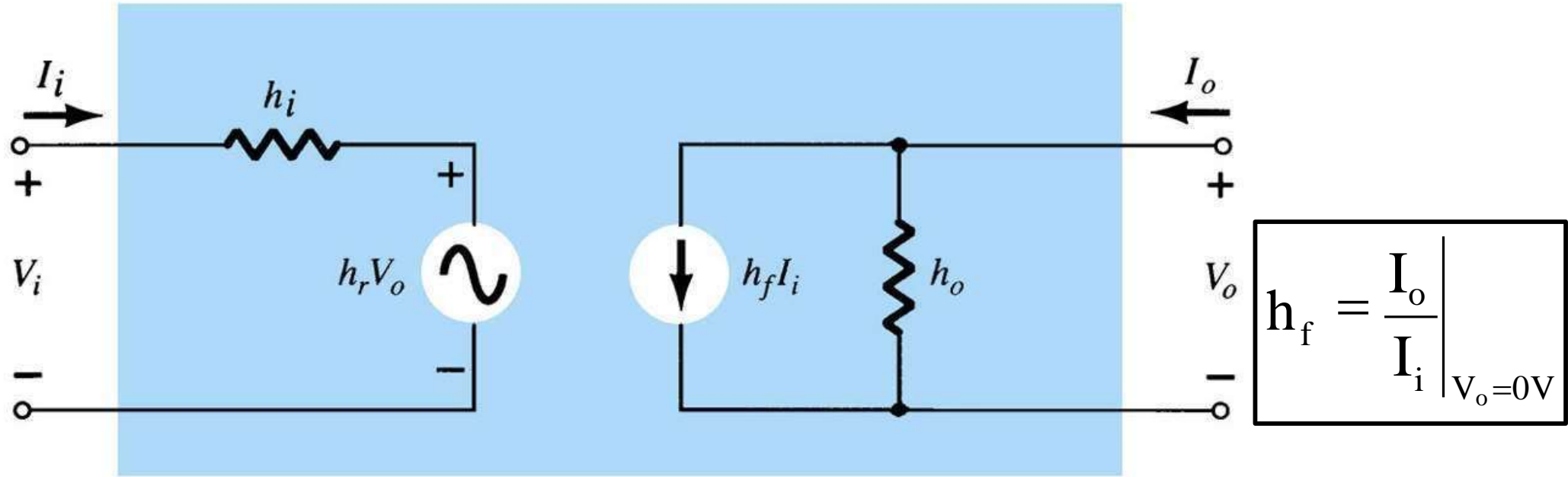General h-Parameters for any Transistor Configuration




$$\begin{aligned} V_i &= h_i I_i + h_r V_o \\ I_o &= h_f I_i + h_o V_o \end{aligned}$$

$$h_i = \left. \frac{V_i}{I_i} \right|_{V_o=0V}$$


$$h_r = \left. \frac{V_i}{V_o} \right|_{I_i=0A}$$

$$h_o = \left. \frac{I_o}{V_o} \right|_{I_i=0A}$$

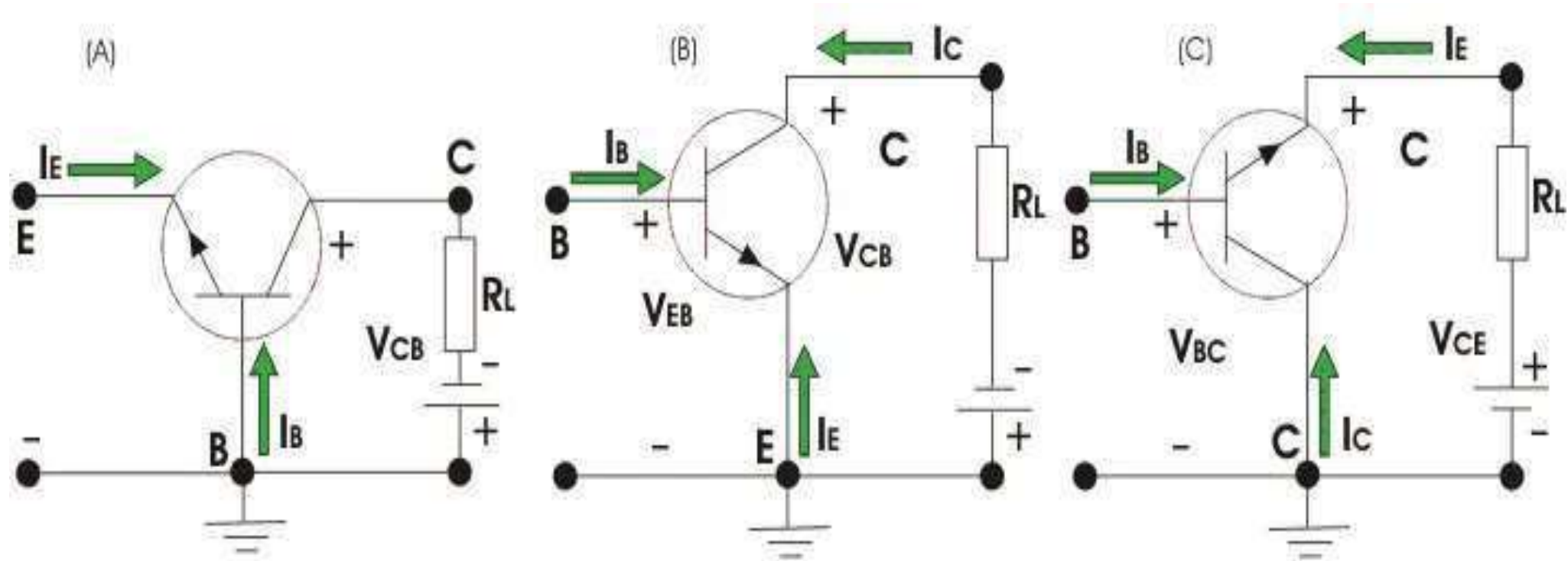
Three Basic Configurations of BJT Amplifier



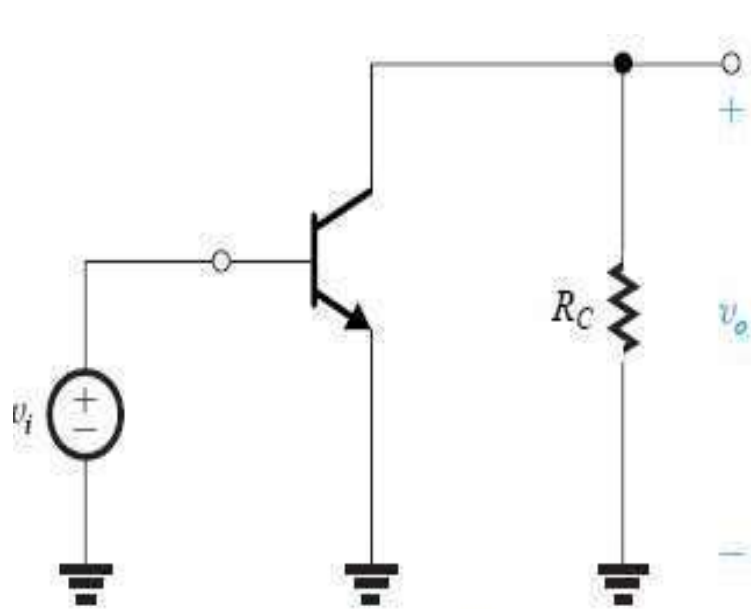
Three Basic Configurations of BJT Amplifier



(a) Common-Emitter (CE)


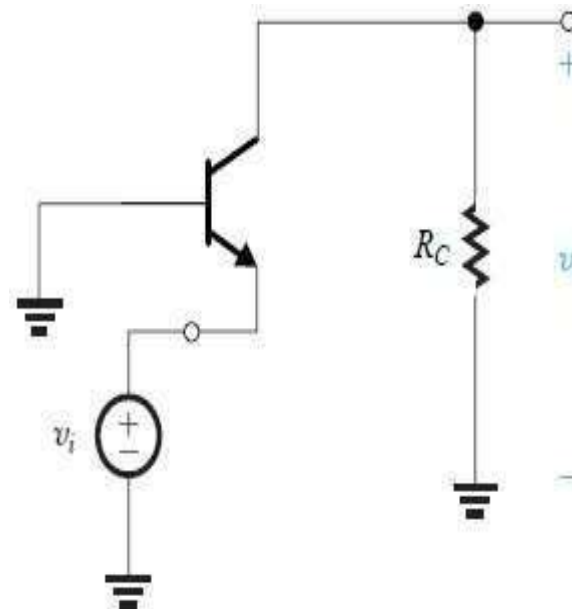


(b) Common-Base (CB)

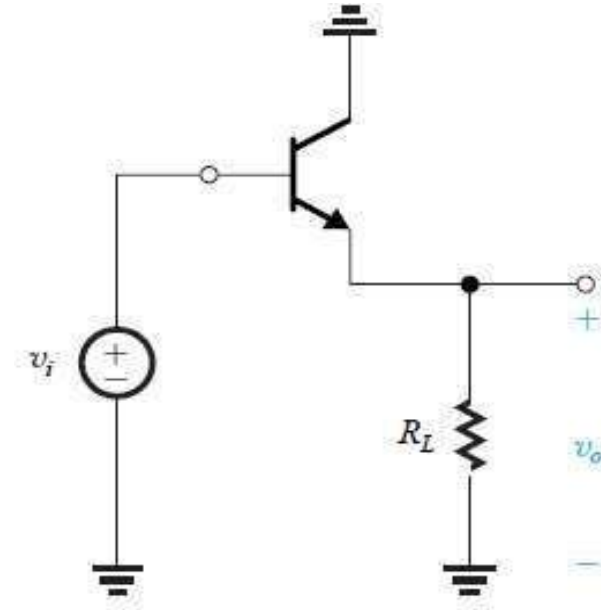

(c) Common-Collector (CC)
or Emitter Follower

Hybrid Model for BJT Configurations-CE

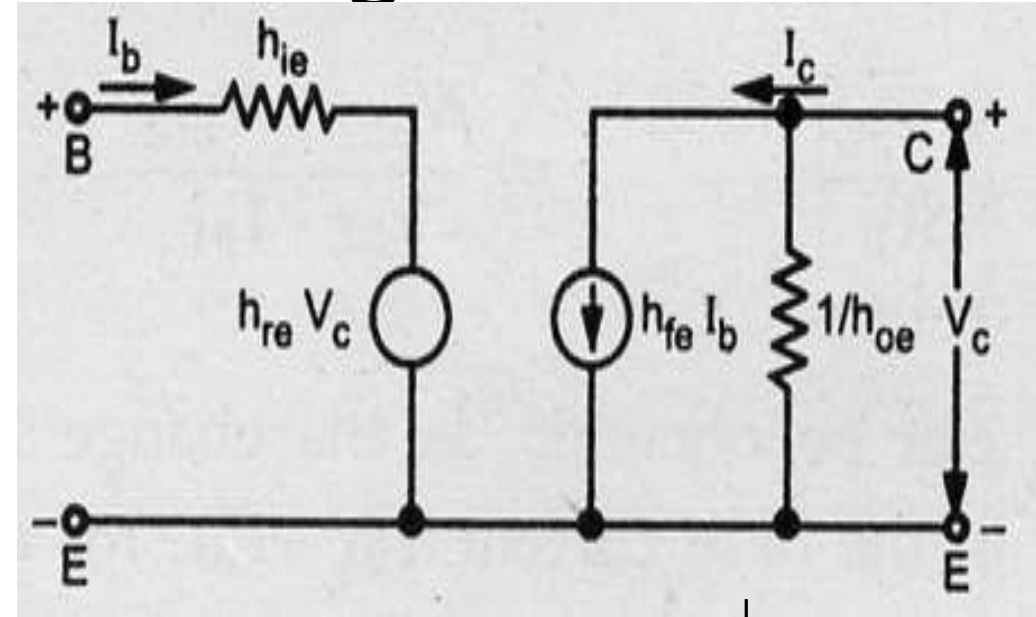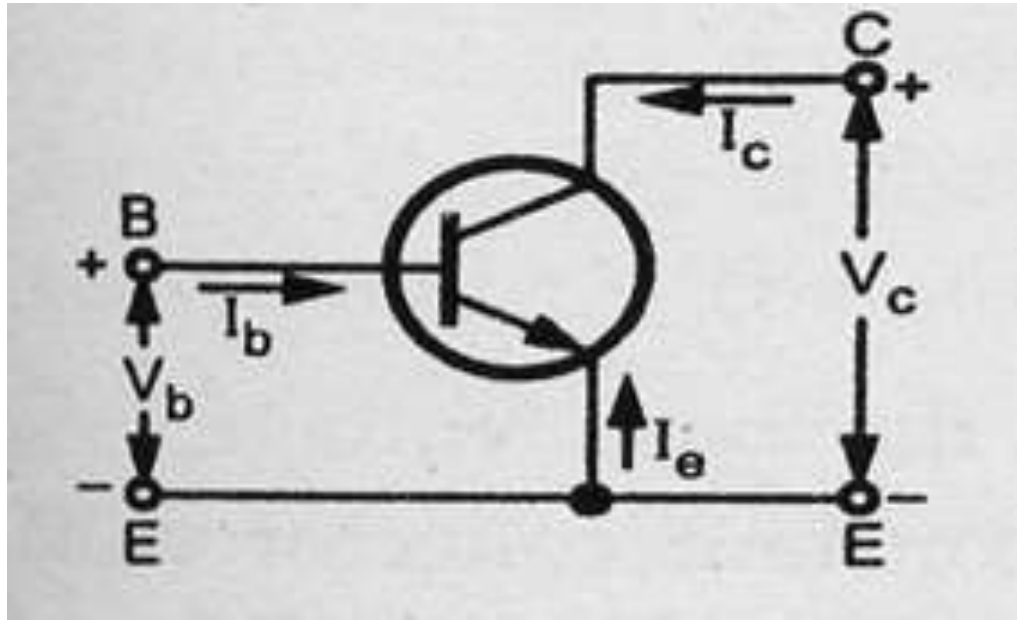

$$v_b = h_{ie} i_b + h_{re} v_c$$

$$i_c = h_{fe} i_b + h_{oe} v_c$$



$$h_{ie} = \left. \frac{v_b}{i_b} \right|_{v_c=0V}$$

$$h_{fe} = \left. \frac{i_c}{i_b} \right|_{v_c=0V}$$

$$h_{re} = \left. \frac{v_b}{v_c} \right|_{i_b=0A}$$

$$h_{oe} = \left. \frac{i_c}{v_c} \right|_{i_b=0A}$$

Hybrid Model for BJT Configurations-CC

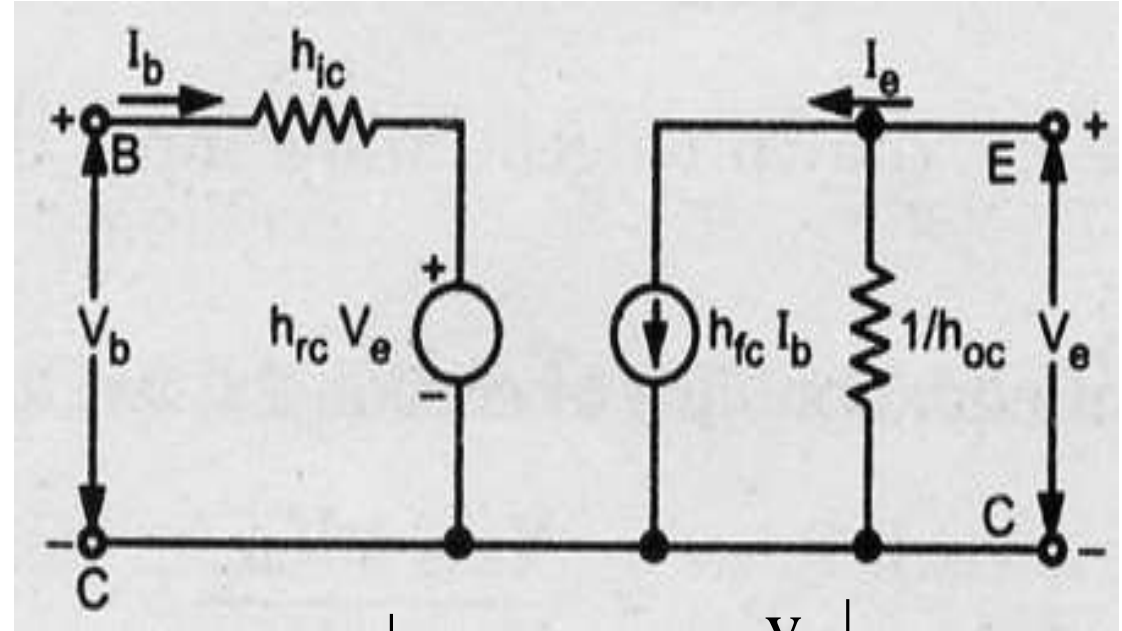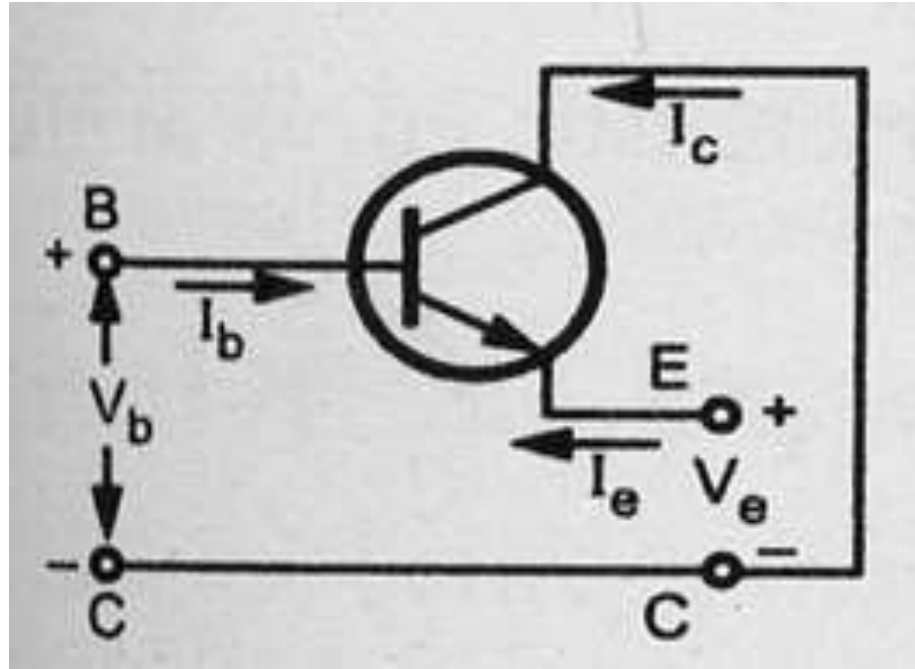

$$v_b = h_{ic} i_b + h_{rc} v_e$$

$$i_e = h_{fc} i_b + h_{oc} v_e$$



$$h_{ic} = \left. \frac{v_b}{i_b} \right|_{v_e=0V}$$

$$h_{fc} = \left. \frac{i_e}{i_b} \right|_{v_e=0V}$$

$$h_{rc} = \left. \frac{v_b}{v_e} \right|_{i_b=0A}$$

$$h_{oe} = \left. \frac{i_e}{v_e} \right|_{i_b=0A}$$



Hybrid Model for BJT Configurations-CB

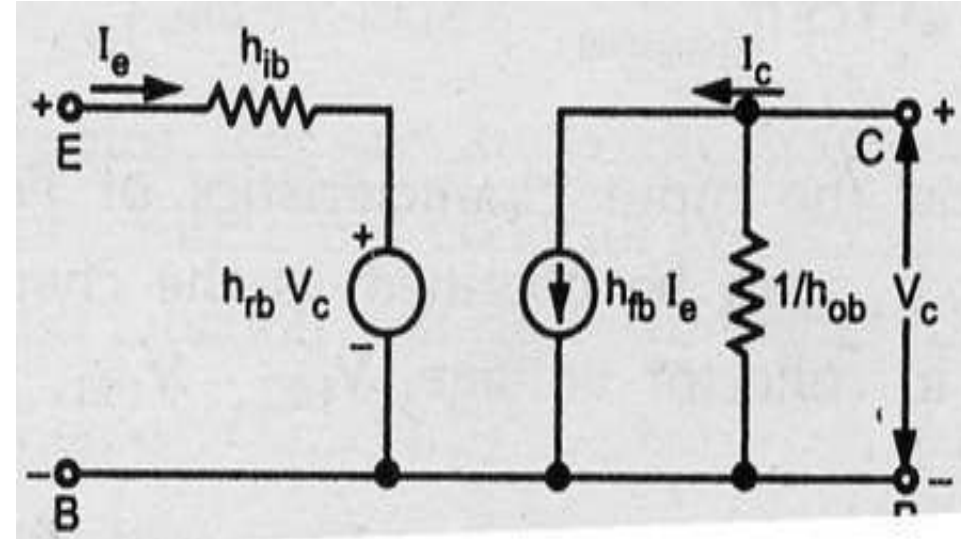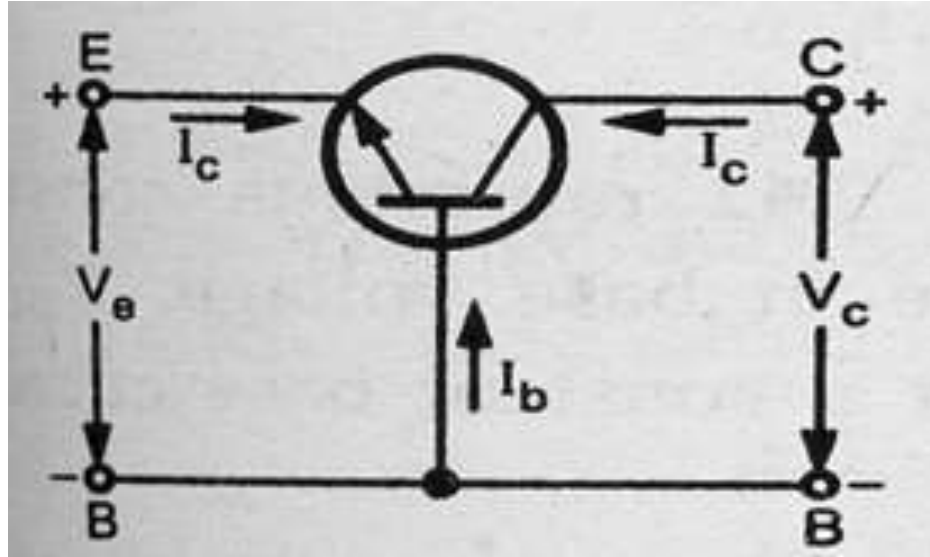


$$\begin{aligned} v_e &= h_{ib} i_e + h_{rb} v_c \\ i_c &= h_{fb} i_e + h_{ob} v_c \end{aligned}$$

$$\begin{aligned} h_{ib} &= \left. \frac{v_e}{i_c} \right|_{v_c=0V} & h_{rb} &= \left. \frac{v_e}{v_c} \right|_{i_e=0A} \\ h_{fb} &= \left. \frac{i_c}{i_e} \right|_{v_c=0V} & h_{ob} &= \left. \frac{i_c}{v_c} \right|_{i_e=0A} \end{aligned}$$

Hybrid Model for BJT Configurations-CE

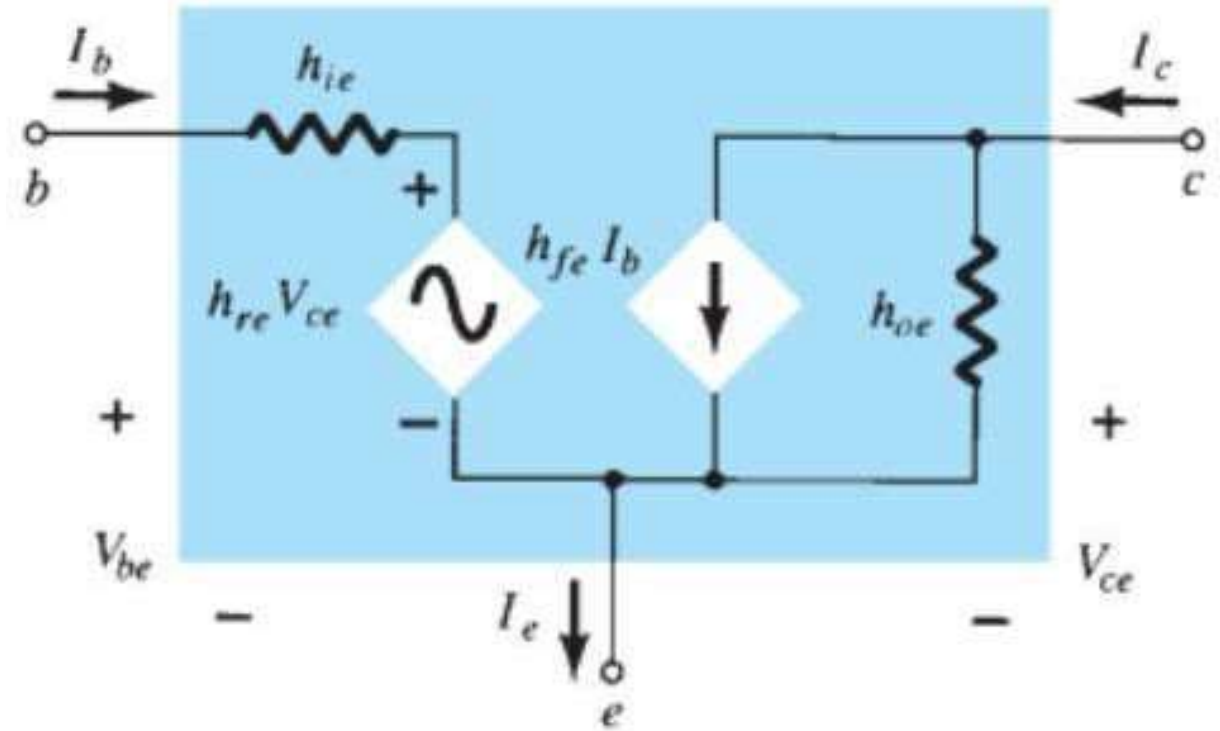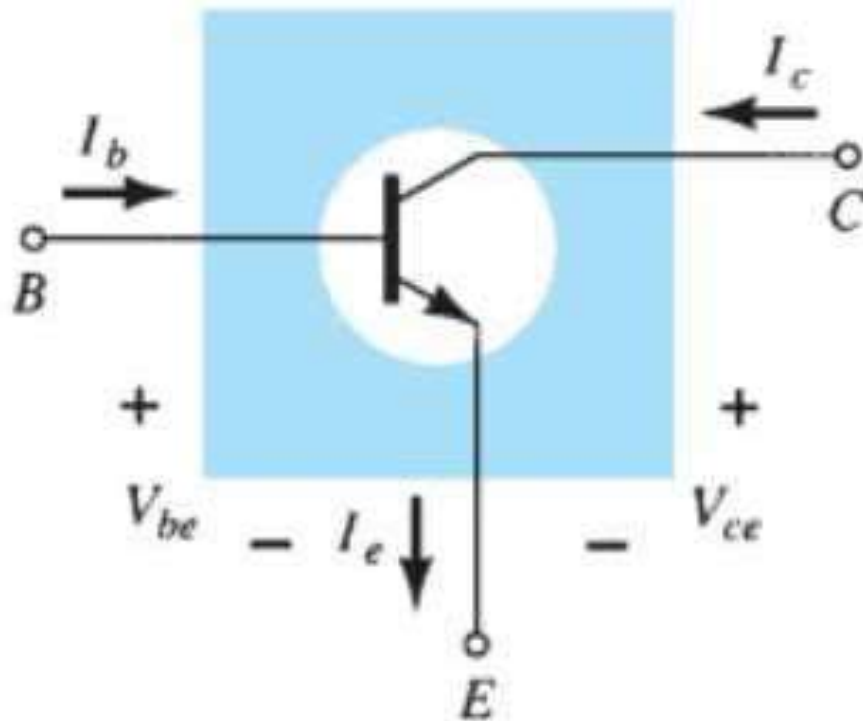


Hybrid Model for BJT Configurations-CE

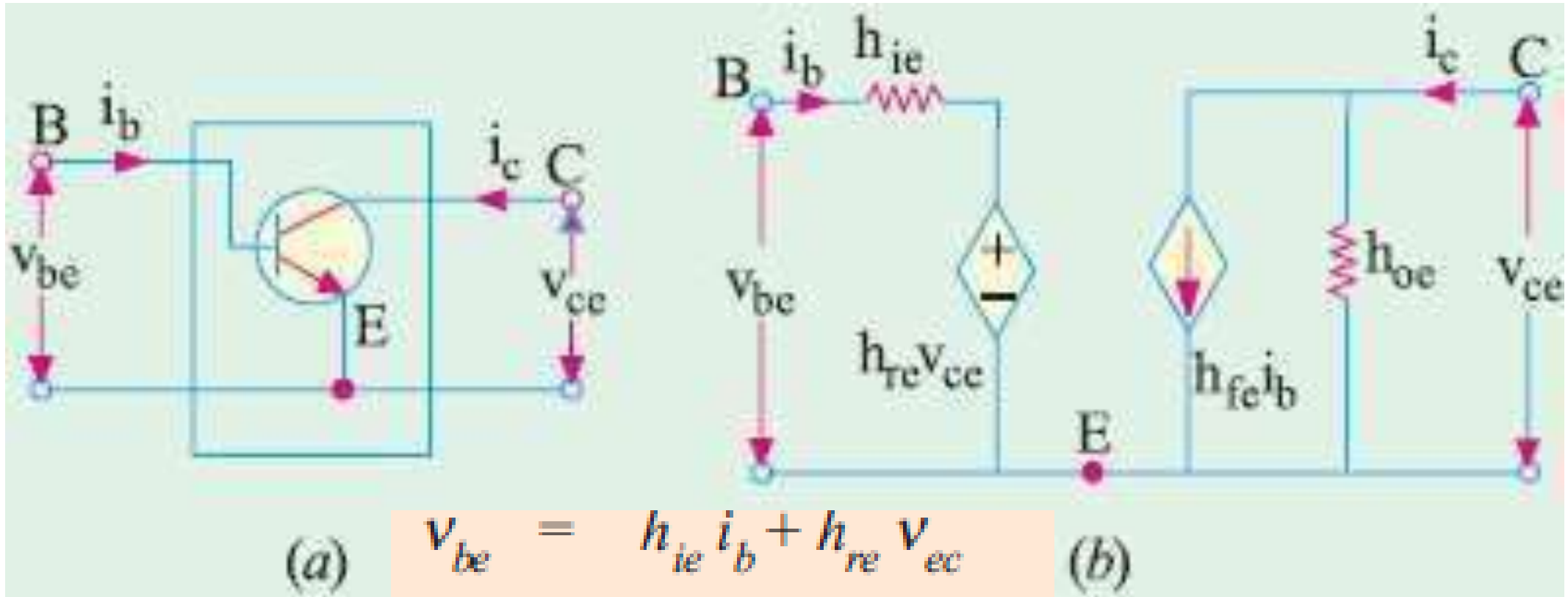


$$v_{be} = h_{ie} i_b + h_{re} v_{ce}$$

$$i_c = h_{fe} i_b + h_{oe} v_{ce}$$


Hybrid Model for BJT Configurations-CB

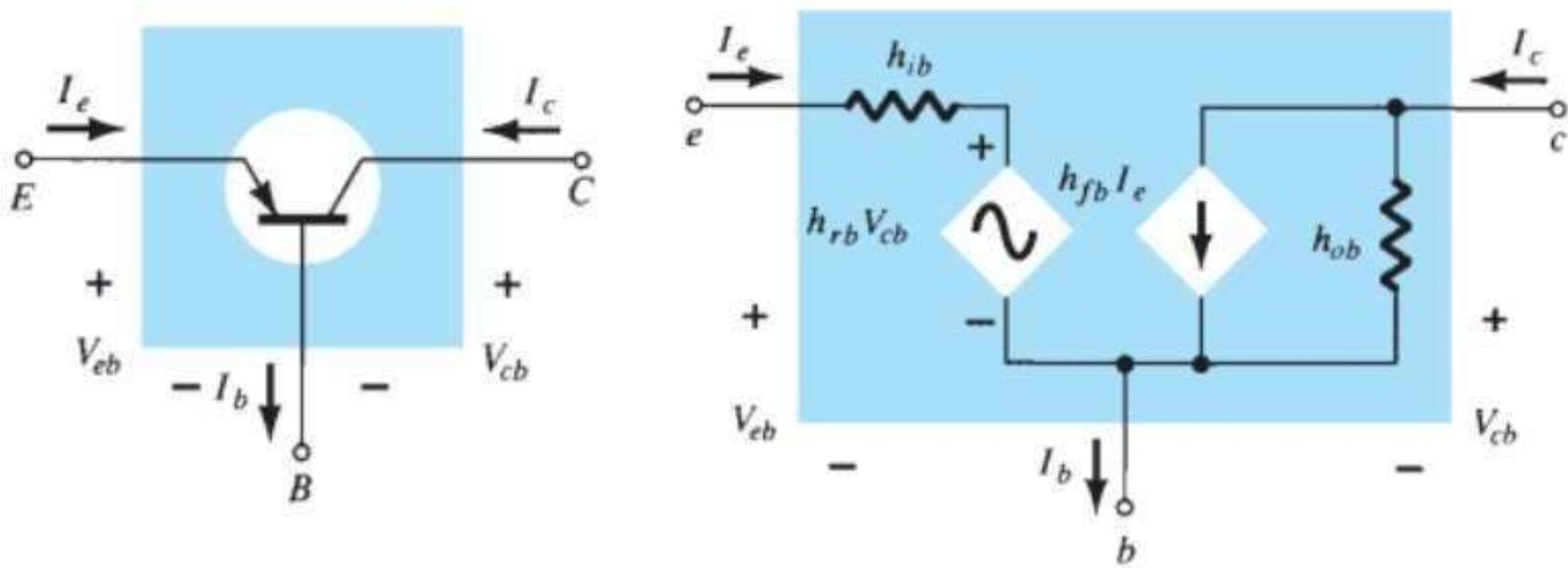

Hybrid Model for BJT Configurations-CB

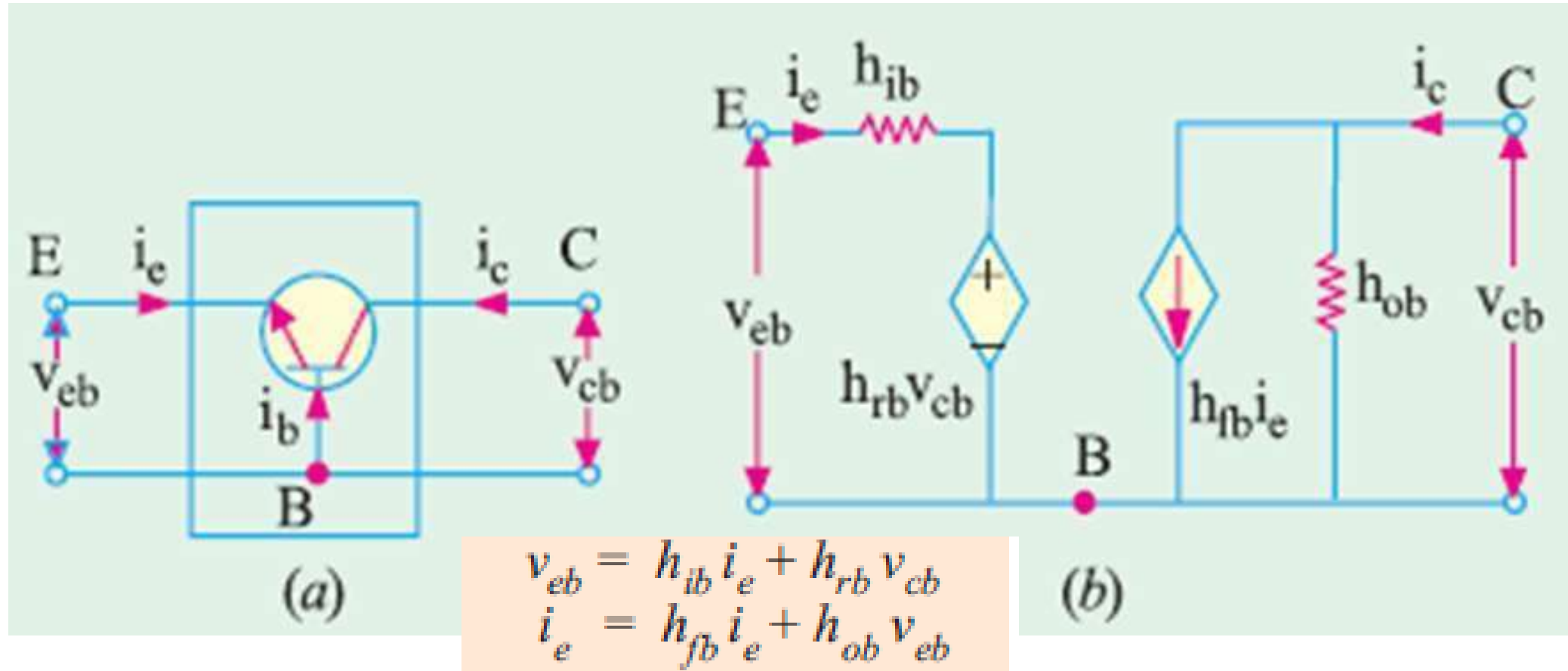


Hybrid Model for BJT Configurations-CC

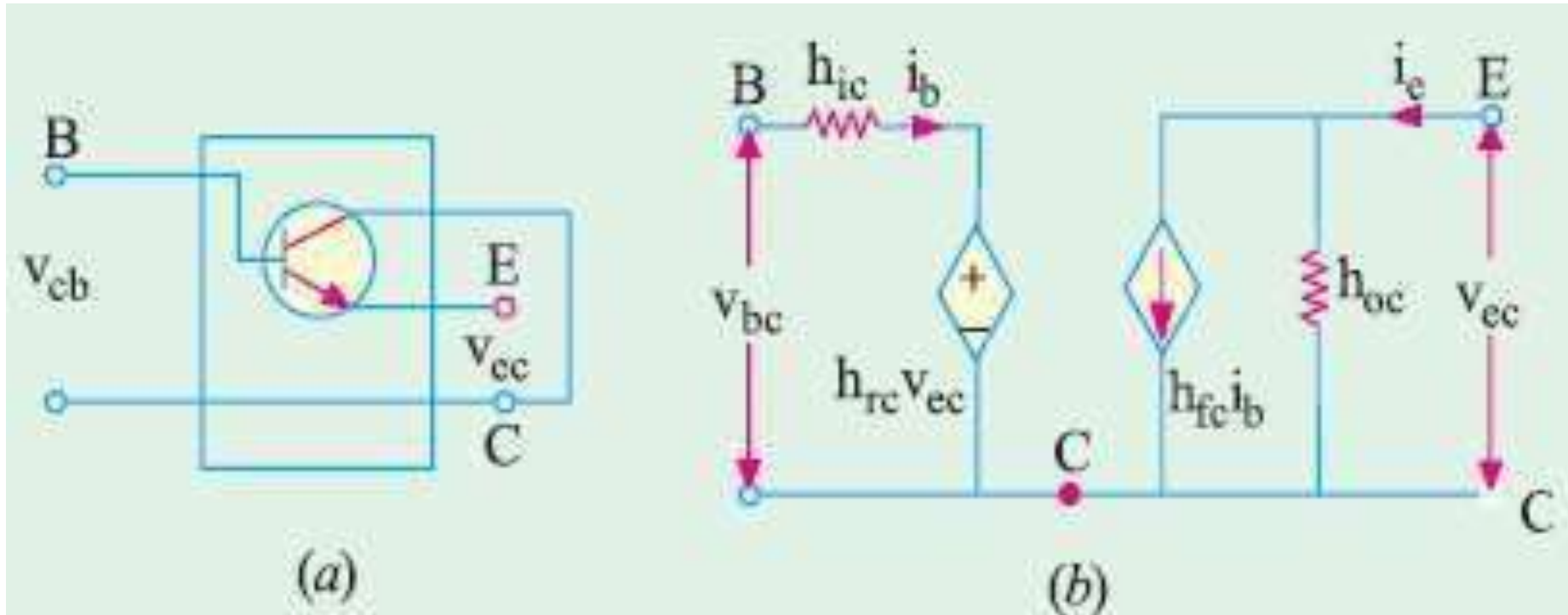

$$\begin{aligned} v_{be} &= h_{ie} i_b + h_{re} v_{ec} \\ i_e &= h_{fe} i_b + h_{oe} v_{ce} \end{aligned}$$


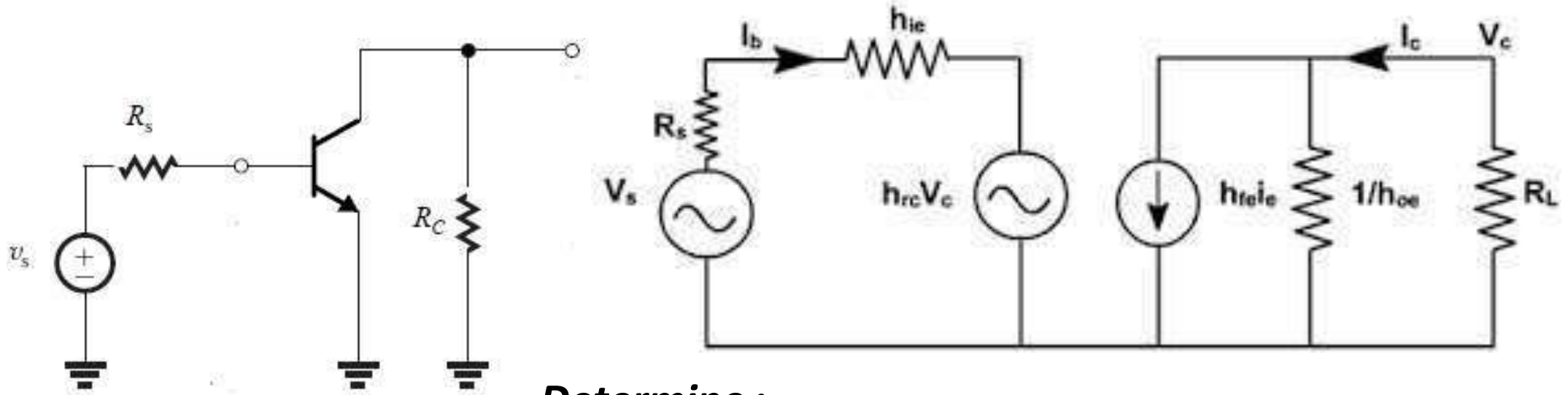
CE Amplifier Without Emitter Resistance (Using Hybrid Model)



Determine :

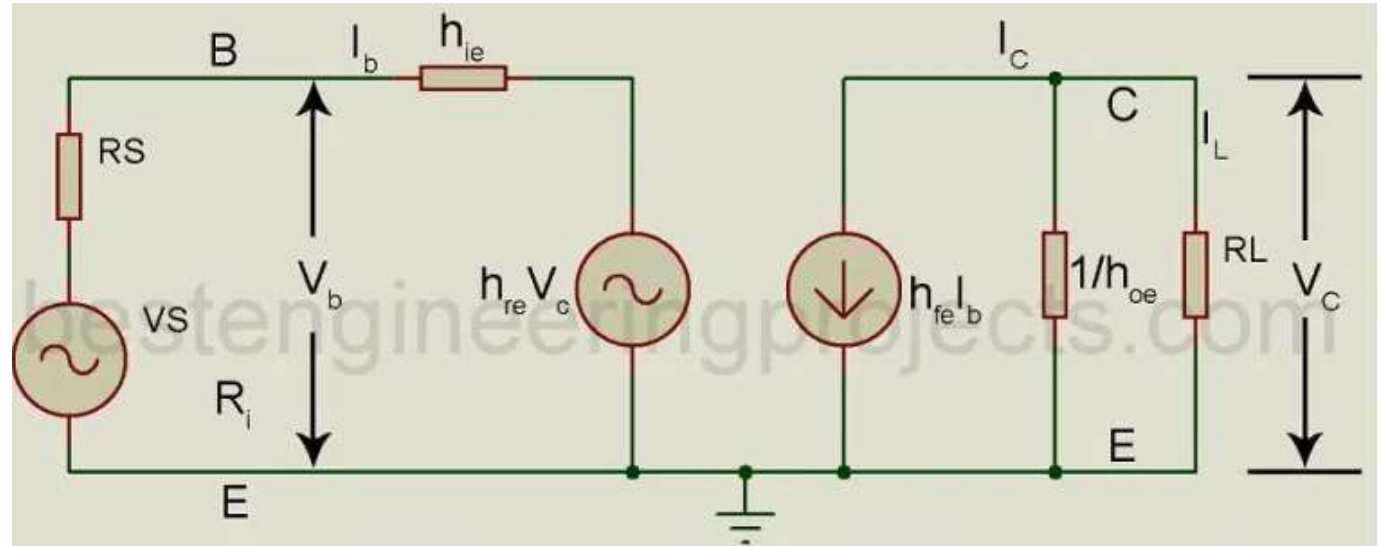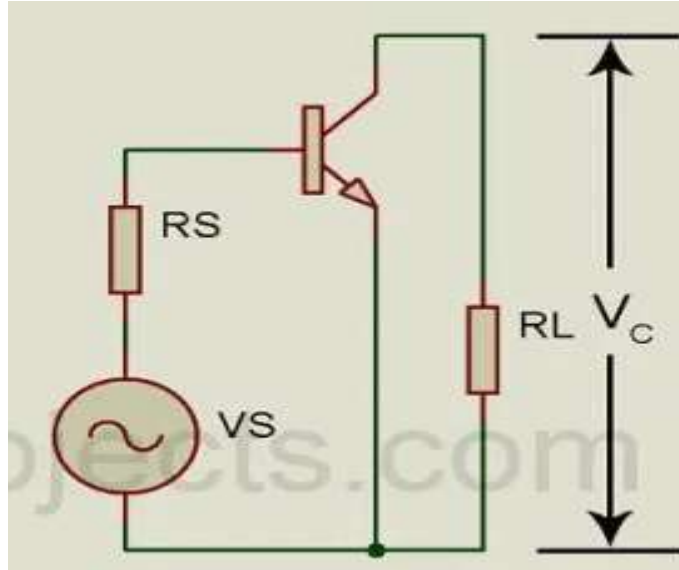- 1. Current Gain or Current Amplification A_i**
- 2. Input Resistance R_i**
- 3. Voltage Gain or Voltage Amplification A_v**
- 4. Output Admittance Y_o**
- 5. Output Resistance R_o**


CE Amplifier Without Emitter Resistance (Using Hybrid Model)



Determine :

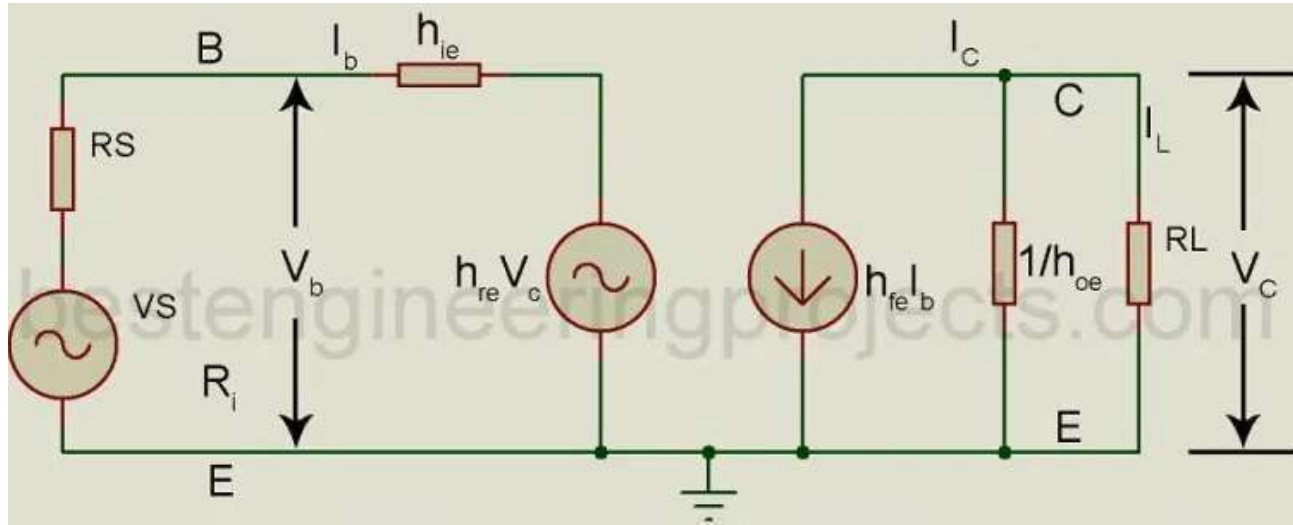1. **Current Gain or Current Amplification A_i**
2. **Input Resistance R_i**
3. **Voltage Gain or Voltage Amplification A_v**
4. **Output Admittance Y_o**
5. **Output Resistance R_o**

CE Amplifier Without Emitter Resistance (Using Hybrid Model)



- **Current Gain or Current Amplification:**
- Current gain is defined as the ratio of the load current I_L to the input current I_b .

$$A_i = \frac{i_c}{i_b} = -\frac{i_c}{i_b}$$

$$i_c = h_{fe} i_b + h_{oe} v_c$$


$$v_c = i_L R_L = -i_c R_L$$

$$i_c = h_{fe} i_b + h_{oe} (-i_c R_L)$$

$$i_c (1 + h_{oe} R_L) = h_{fe} i_b$$

$$A_i = \frac{i_c}{i_b} = -\frac{h_{fe}}{1 + h_{oe} R_L}$$

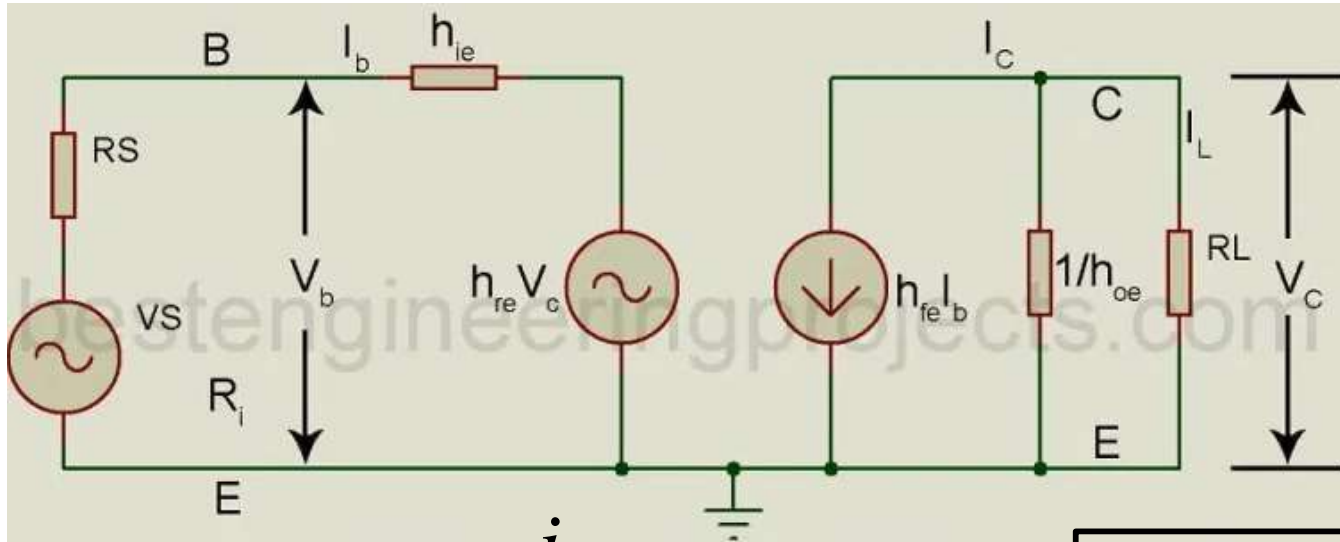CE Amplifier Without Emitter Resistance (Using Hybrid Model)



Input Resistance R_i

$$R_i = \frac{v_b}{i_b}$$

$$v_b = h_{ie} i_b + h_{re} v_c$$

But, $A_i = -\frac{i_c}{i_b} \Rightarrow i_c = -A_i i_b$


$$v_c = i_L R_L = -i_c R_L = A_i i_b R_L$$

$$v_b = h_{ie} i_b + h_{re} (A_i i_b R_L)$$

$$v_b = i_b (h_{ie} + h_{re} A_i R_L)$$

$$\Rightarrow R_i = \frac{v_b}{i_b} = h_{ie} + h_{re} A_i R_L$$

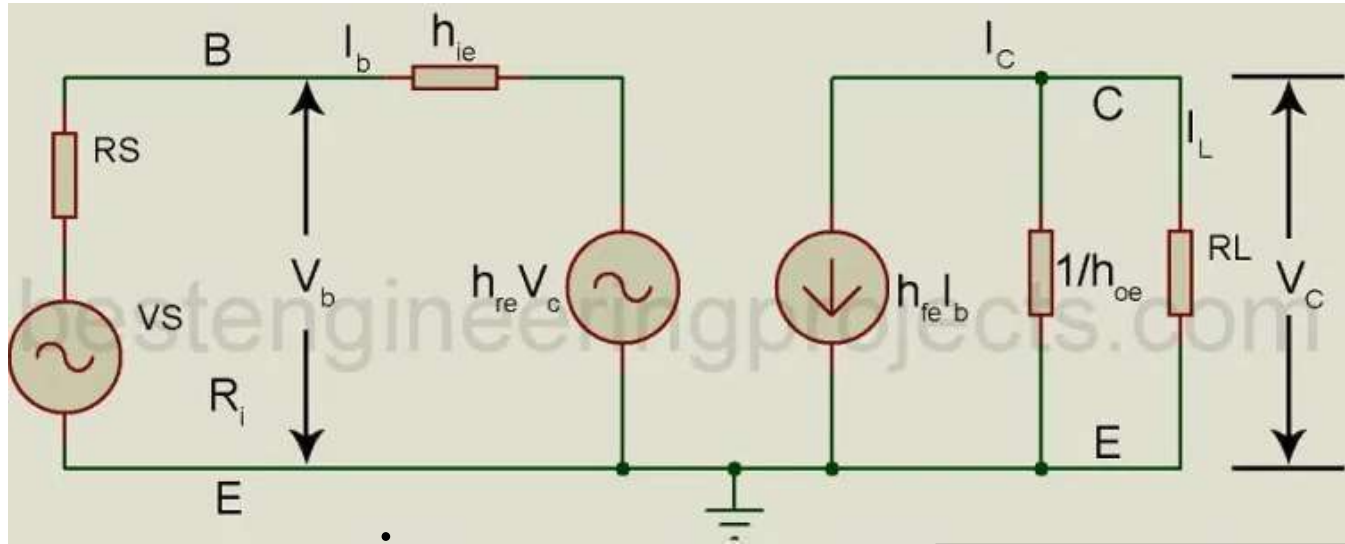CE Amplifier Without Emitter Resistance (Using Hybrid Model)



Voltage Gain A_v

$$A_v = \frac{V_c}{V_b}$$


But, $A_i = -\frac{i_c}{i_b} \Rightarrow i_c = -A_i i_b$

$$V_c = i_L R_L = -i_c R_L = A_i i_b R_L$$

$$\frac{1}{R_i} = \frac{i_b}{V_b}$$

$$\Rightarrow A_v = \frac{V_c}{V_b} = \frac{A_i i_b R_L}{V_b} = \frac{A_i R_L}{R_i}$$

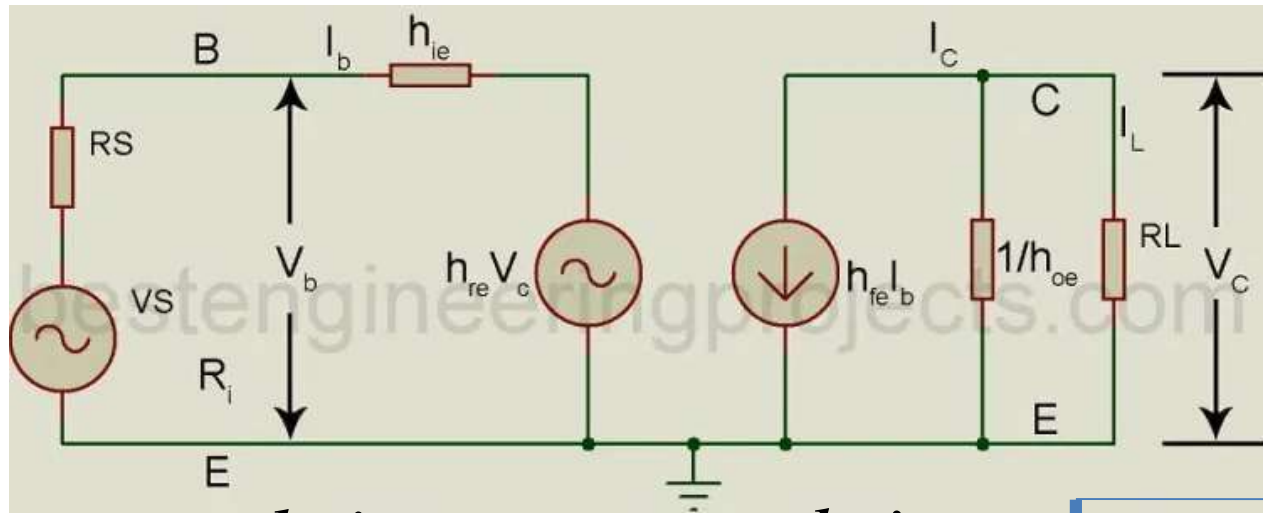CE Amplifier Without Emitter Resistance (Using Hybrid Model)



Output Admittance Y_o

$$Y_o = \frac{i_c}{v_c}$$

$$i_c = h_{fe} i_b + h_{oe} v_c$$

Dividing By V_c

$$\Rightarrow \frac{i_b}{v_c} = -\frac{h_{re}}{R_s + h_{ie}}$$



$$\frac{i_c}{v_c} = \frac{h_{fe} i_b}{v_c} + \frac{h_{oe} v_c}{v_c} \Rightarrow \frac{i_c}{v_c} = \frac{h_{fe} i_b}{v_c} + h_{oe}$$

$$v_s = 0, R_s i_b + h_{ie} i_b + h_{re} v_c = 0$$

$$(R_s + h_{ie}) i_b = -h_{re} v_c$$

$$\Rightarrow Y_o = h_{oe} - \frac{h_{fe} h_{re}}{R_s + h_{ie}} \text{ and } R_o = \frac{1}{Y_o}$$

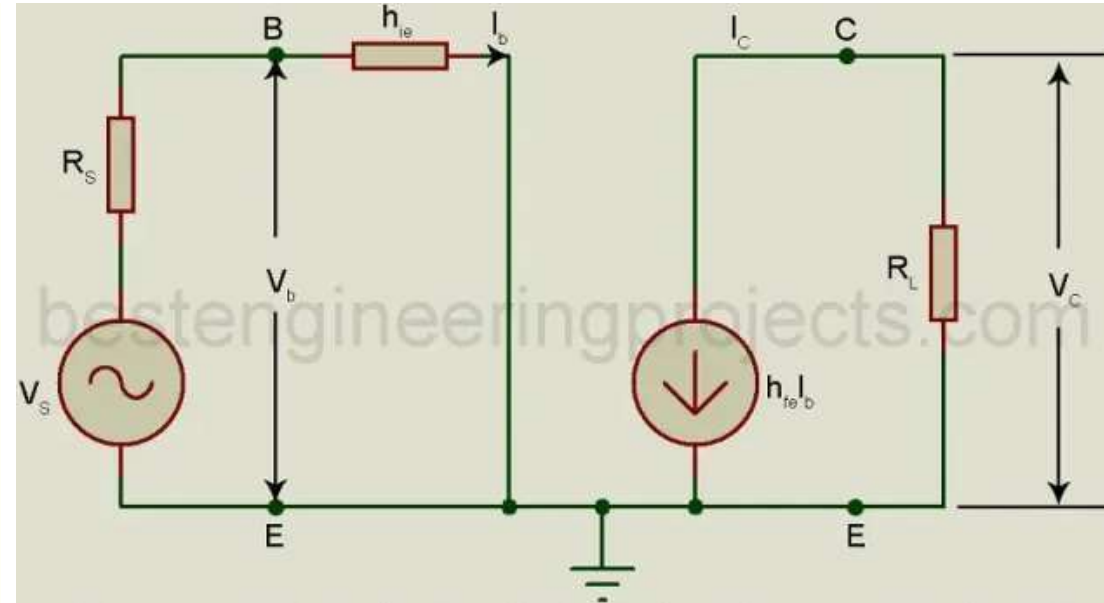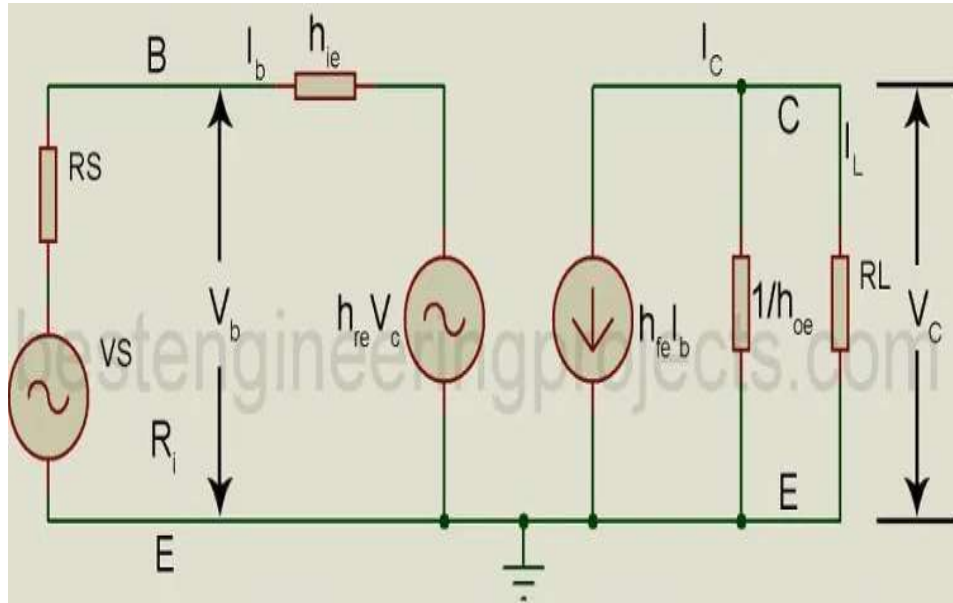CE Amplifier Without Emitter Resistance (Using Approximate Hybrid Model)



$$A_i = \frac{i_c}{i_b} = -\frac{h_{fe}}{1 + h_{oe}R_L}$$

$$R_i = \frac{V_b}{i_b} = h_{ie} + h_{re}A_iR_L$$


Neglecting

$$A_i = \frac{i_c}{i_b} = -h_{fe}$$


$$h_{oe} = 0, \text{ and } h_{re} = 0$$

$$\Rightarrow R_i = h_{ie}$$

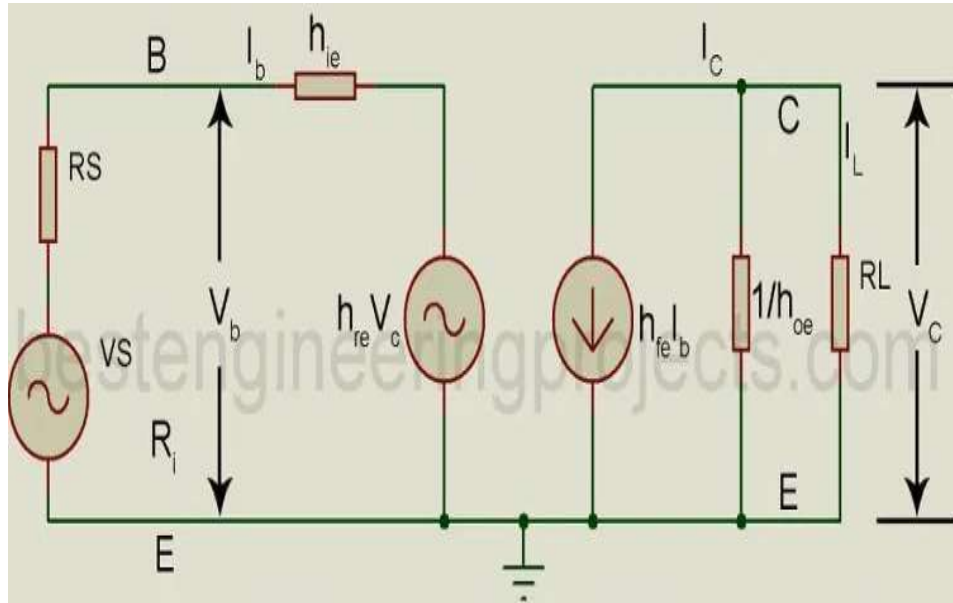CE Amplifier Without Emitter Resistance (Using Approximate Hybrid Model)


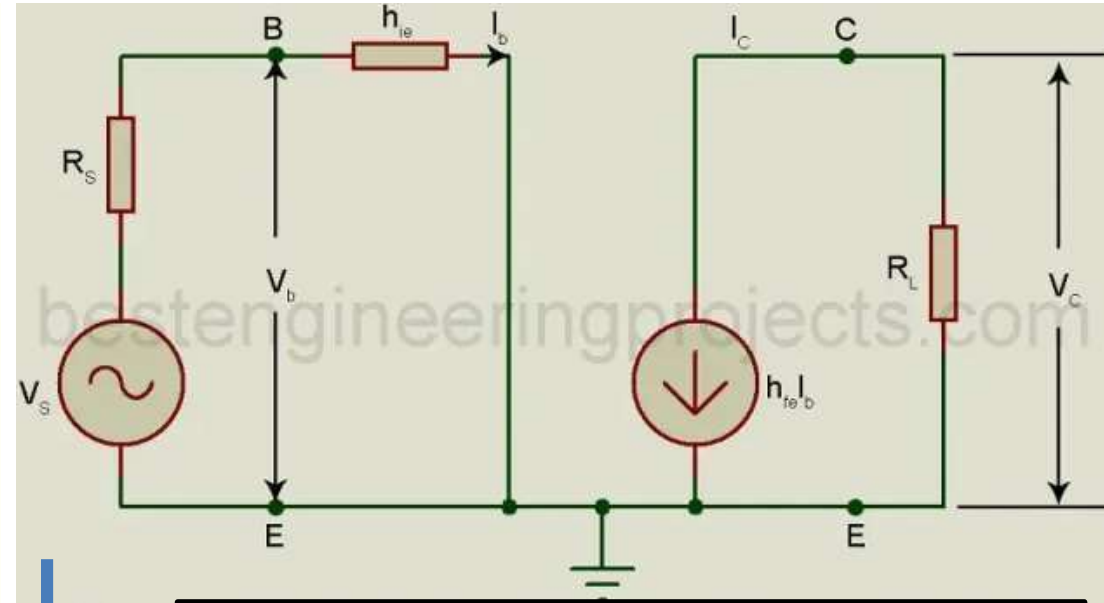
$$\Rightarrow A_v = \frac{A_i R_L}{R_i} = \frac{A_i R_L}{h_{ie}}$$



$$\Rightarrow Y_0 = h_{oe} - \frac{h_{fe} h_{re}}{R_s + h_{ie}} \text{ and } R_0 = \frac{1}{Y_0}$$

$$\Rightarrow Y_0 = 0 \text{ and } R_0 = \frac{1}{Y_0} = \infty$$