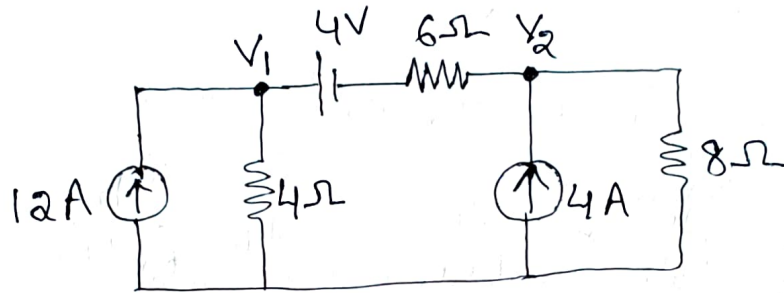



# section-C

①

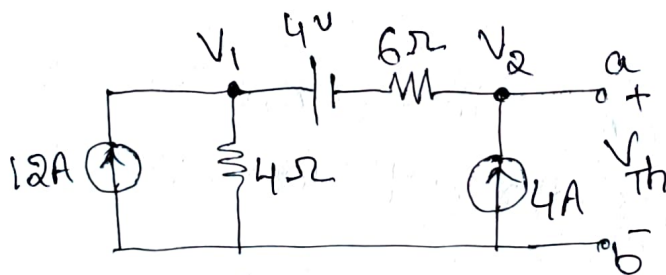7. using thevenin's theorem, find the current flowing through the  $8\Omega$  resistor of the network shown.



Sol:- (i) To find  $V_{th}$ : Remove  $R_L = 8\Omega$



$$V_{th} = V_2$$

By nodal analysis,

$$\text{At node-1: } \frac{V_1}{4} + \frac{V_1 - 4 - V_2}{6} = 12$$

$$3V_1 + 2V_1 - 8 - 2V_2 = 144$$

$$5V_1 - 2V_2 = 152 \rightarrow \textcircled{1}$$


$$\text{At node-2: } \frac{V_2 + 4 - V_1}{6} = 4$$

$$-V_1 + V_2 = 20 \rightarrow \textcircled{2}$$


solving eq- ① & ②, we get

$V_1 = 64V$	$V_{th} = V_2 = 84V$
-------------	----------------------

ii) To find  $R_{th}$ :

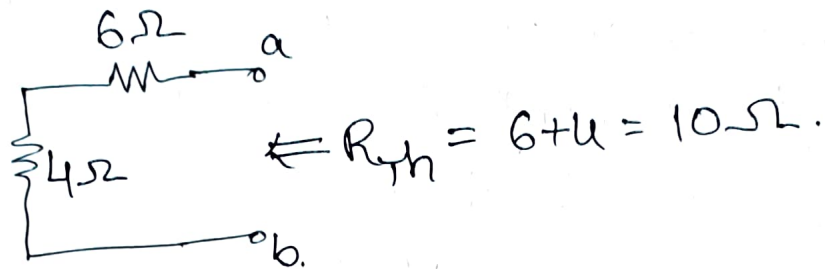

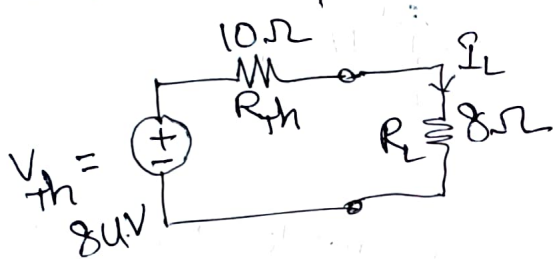
(iii) To find current in  $8\Omega$  resistor:




$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{84}{18}$$

$$I_L = 4.67A$$

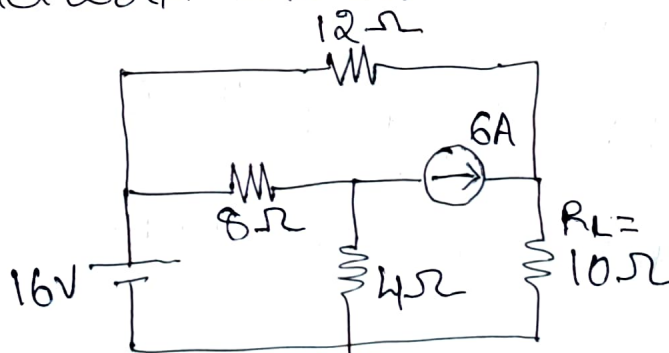⑧ Using Norton's theorem, find the current flowing through  $10\Omega$  resistor in the network shown.



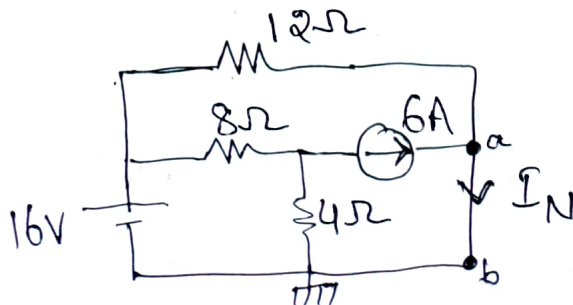Sol:- (i) To find short circuit current  $I_N$



current through  $12\Omega$  is


$$I_{12\Omega} = \frac{16}{12} = 1.33A$$

(2)

By KCL at node - a,

$$I_N = 6 + I_{12\Omega} = 6 + 1.33 = \underline{\underline{7.33A.}}$$

(ii) To find  $R_N$ :

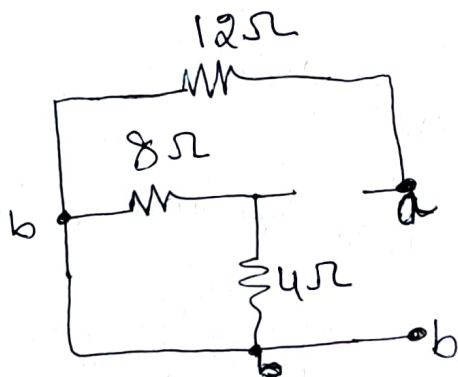


$R_N$  = Resistance between node - a and node - b.

$$R_N = 12\Omega$$

[ $\because (8+4)$  is parallel with short circuit]

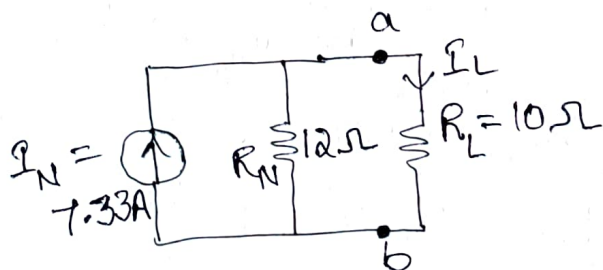
(iii) To find current in  $10\Omega$  resistor:




$$I_L = I_N \times \frac{R_N}{R_N + R_L}$$

$$I_L = 7.33 \times \frac{12}{22} = 4A$$

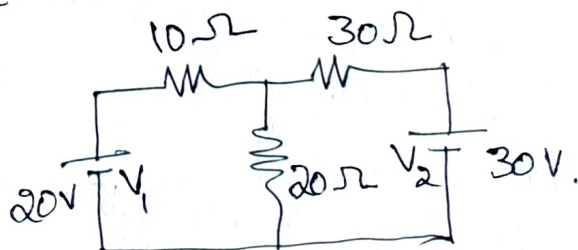(9) Using superposition theorem, find the current flowing through the  $20\Omega$  resistor of the network shown.



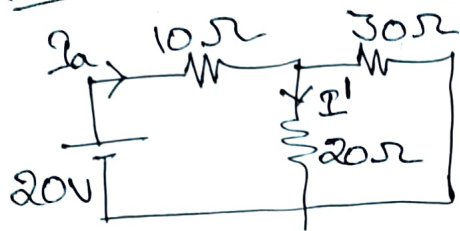Sol:- (i) with only 20V source in the network,




$$I_a = \frac{20}{10 + \frac{20 \times 30}{20 + 30}} = \frac{20 \times 50}{1100}$$

$$I_a = \frac{10}{11} = 0.91 \text{ A.}$$

then

$$I' = I_a \times \frac{30}{30 + 20} = \underline{\underline{0.55 \text{ A.}}}$$

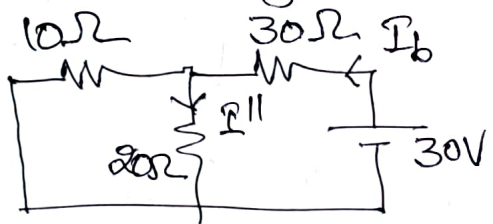(ii) with only 30V source in the network,



$$I_b = \frac{30}{30 + \frac{10 \times 20}{10 + 20}} = 0.82 \text{ A}$$


then

$$I'' = I_b \times \frac{10}{10 + 20} = 0.27 \text{ A}$$

(iii) By superposition theorem, the current flowing through 20Ω resistor is


$$I = I' + I'' = 0.55 + 0.27 = \underline{\underline{0.82 \text{ A}}}$$

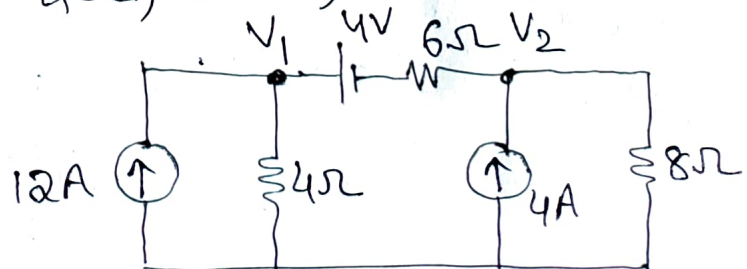(10) Using mesh analysis, determine the currents in 4Ω, 6Ω & 8Ω of the network shown.



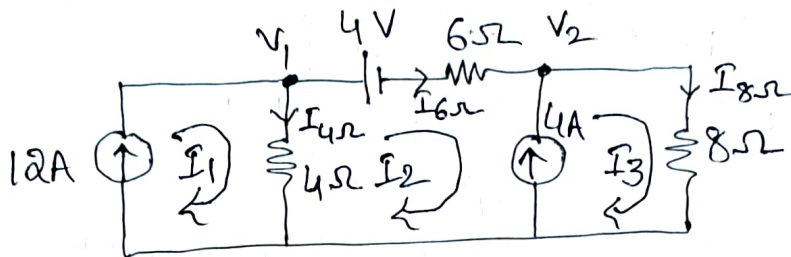(3)

Sol:- Let the mesh currents are  $I_1, I_2$  and  $I_3$  as shown



From mesh-1:  $I_1 = 12A$ .

from mesh-2 & 3 form a super mesh, then

$$4(I_2 - I_1) + 4 + 6I_2 + 8I_3 = 0$$

$$10I_2 + 8I_3 = 44 \rightarrow (1) \quad [\because I_1 = 12]$$

From 4A current source branch,

$$-I_2 + I_3 = 4 \rightarrow (2)$$

solving eq-① & ②, we get

$$I_2 = 0.67A \quad \text{and} \quad I_3 = 4.67A.$$

Now,


$$I_{4\Omega} = I_1 - I_2 = 12 - 0.67 = \underline{\underline{11.33A.}}$$

$$I_{6\Omega} = I_2 = \underline{\underline{0.67A}}$$

$$I_{8\Omega} = I_3 = \underline{\underline{4.67A.}}$$



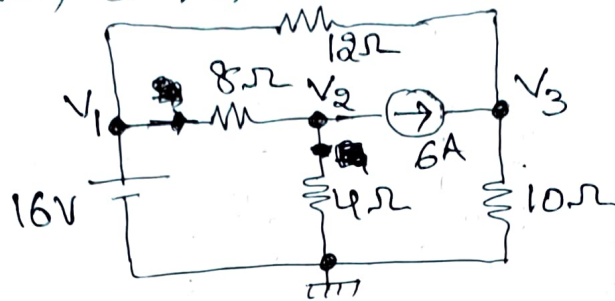⑪ using nodal analysis, determine the currents in  $4\Omega$ ,  $8\Omega$ ,  $10\Omega$  &  $12\Omega$  in the network shown.



Sol:- Let  $V_1$ ,  $V_2$  and  $V_3$  are the node voltages at node-1, 2, & 3, respectively, w.r.t ground.

From node-1:  $V_1 = 16\text{ V.}$

From node-2, by KCL:

$$\frac{V_2 - V_1}{8} + \frac{V_2}{4} + 6 = 0.$$

$$-V_1 + 3V_2 = -48 \rightarrow \textcircled{1} \therefore V_2 = -10.67\text{ V.}$$

From node-3, by KCL

$$\frac{V_3 - 16}{12} + \frac{V_3}{10} = 6 \Rightarrow 11V_3 = 280 \Rightarrow V_3 = 25.45\text{ V.}$$

~~$\therefore V_3 = 25.45\text{ V.}$~~

$V_3 = 40\text{ V}$

then,

$$I_{8\Omega} = \frac{V_1 - V_2}{8} = 3.33\text{ A.}$$

$$I_{4\Omega} = \frac{V_2}{4} = -2.67\text{ A}$$

$$I_{10\Omega} = \frac{V_3}{10} = 4\text{ A}$$


$$I_{12\Omega} = \frac{V_3 - V_1}{12} = \frac{24}{12}$$

$$= 2\text{ A.}$$


$$I_{12\Omega} = 2\text{ A.}$$

(4)

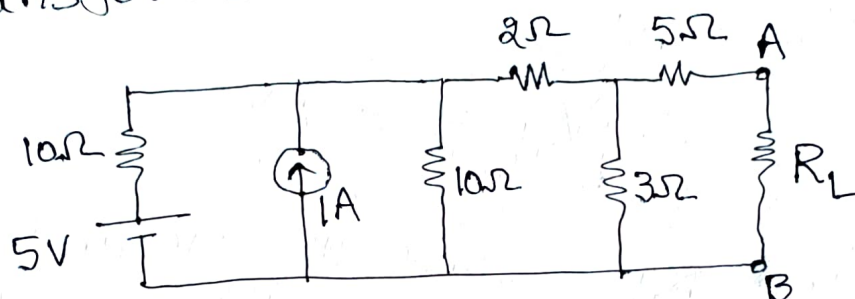- (12) In the circuit shown, (a) obtain the condition for maximum power transfer to the load  $R_L$ . (b) Hence determine the maximum power transferred.



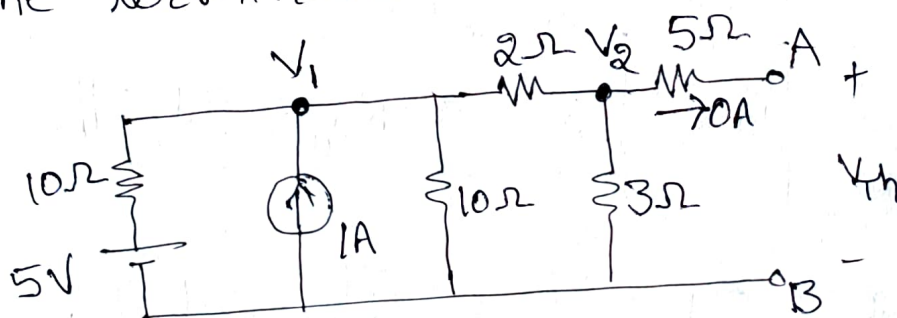Sol: (i) To find thevenin's voltage across the terminals A-B:



By nodal analysis; at node-1,

$$\frac{V_1 - 5}{10} + \frac{V_1}{10} + \frac{V_1 - V_2}{2} = 1$$

$$7V_1 - 5V_2 = 15 \rightarrow (1)$$

at node -2:

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} = 0 \Rightarrow -3V_1 + 5V_2 = 0 \rightarrow (2)$$


solving eq-(1) & (2), we get

$$V_1 = 3.75V \text{ and } V_2 = 2.25V.$$

As no current flow through  $5\Omega$  when load terminals are open, the thevenin's voltage  $V_{Th}$  across A-B terminals is equal to  $V_2$  only.

$$\therefore V_{Th} = 2.25V$$

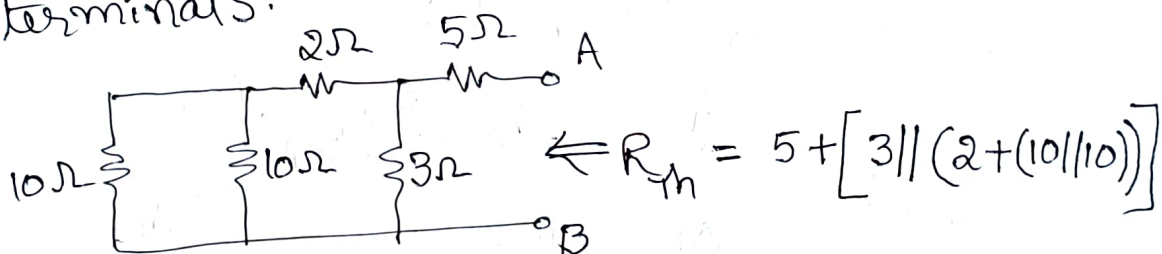
(ii) To find  $R_{Th}$ , short the  $5V$  and open the  $1A$  sources and calculate  $R_{Th}$  between load terminals.



$$R_{Th} = 5 + \frac{3 \times 7}{3 + 7} = \frac{71}{10} = 7.1\Omega$$

$$R_{Th} = 7.1\Omega$$

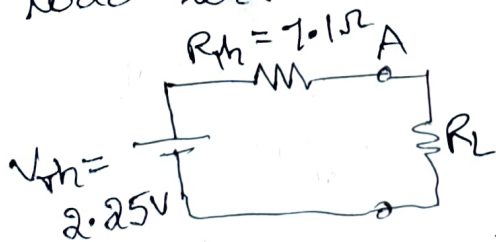(iii) the thevenin's equivalent circuit across load terminals is



According to maximum Power transfer theorem, for max. power transfer is possible when  $R_L = R_{Th}$ .

$$\therefore R_L = 7.1\Omega$$



5

(iv) The value of max. power transferred to the load  $P_{L, \max}$  is,

$$P_{L, \max} = \frac{V_{th}^2}{4R_{th}} = \frac{(2.25)^2}{4 \times 7.1}$$

$$P_{L, \max} = 0.18 \text{ W.}$$