

CO-2
ONE MINUTE PAPER (ALM-4)

Determine the charge and current in an LCR series circuit when inductance 3 H, resistance 6 ohms, capacitance $\frac{1}{3}$ F, and $E(t) = \sin 2t$.