

$$V_{CC} = 12V ; \beta = 100 ; I_C = 2mA$$

$$f_L = 100Hz ; R_L = 10K\Omega$$

Mid point of Quiescent ($V_{CEQ} ; I_{CQ}$)

$$V_{CE} = \frac{V_{CC}}{2}$$

Assume $I_C \cong I_E$ [for simplification]

$$\therefore V_E = I_E R_E$$

$$= I_C R_E \quad [\because I_E \cong I_C]$$

Drop across R_E must be 10% of V_{CC} .

R_E acting as feedback ; for stabilization only 10% feedback is enough. for max o/p drop should be less.

$$V_{CC} \Rightarrow 12V ; V_E = 10\% \text{ of } V_{CC} \Rightarrow 1.2V$$

$$R_E = \frac{V_E}{I_C} = \frac{1.2}{2 \times 10^{-3}} = 600\Omega$$

\Rightarrow KVL to o/p loop

$$V_{CC} = I_C R_C + V_{CE} + I_E R_E$$

$$= I_C R_C + V_{CE} + V_E$$

$$R_C = \frac{V_{CC} - V_{CE} - V_E}{I_C} = 2.4K\Omega$$

\Rightarrow finding R_1 & R_2

from Ckt KCL to I_D


$$I_1 = I_2 + I_B$$

I_2 must be 10 times of I_B .

$$I_2 = 10 I_B \Rightarrow I_1 = 10 I_B + I_B = 11 I_B$$

$$I_C = \beta I_B \quad \therefore I_B = \frac{I_C}{\beta} = \frac{2mA}{100} \Rightarrow 0.02 \times 10^{-3}$$
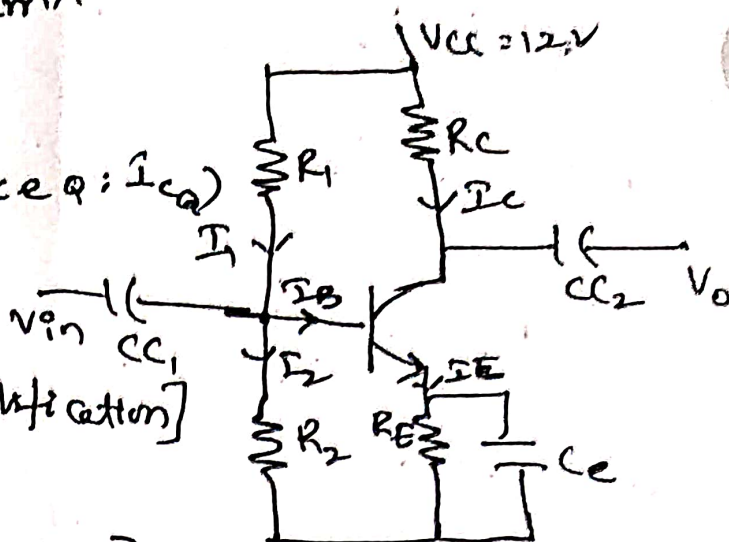
$$\Rightarrow 0.02mA \Rightarrow 20\mu A$$



$$\therefore V_{BE} = I_2 R_2$$

$$R_2 = \frac{V_{BE}}{I_2}$$

$$V_{BE} = V_B - V_E \Rightarrow V_B = V_{BE} + V_E$$

$$= 0.7 + 1.2 \Rightarrow 1.9V$$

$$\therefore R_2 = \frac{1.9}{10 \times 20 \mu A} \Rightarrow \frac{1.9}{200 \mu A}$$

$\underline{R_1}$ = Apply KVL to \uparrow loop

$$V_{CC} = I_1 R_1 + I_2 R_2$$

$$I_1 R_1 = V_{CC} - I_2 R_2$$

$$R_1 = \frac{V_{CC} - I_2 R_2}{I_1}$$

$$= \frac{V_{CC} - V_B}{I_1}$$

$$= \frac{12 - 1.9}{11 \times 20 \mu A}$$

\Rightarrow Design of Coupling Capacitors C_1 & C_2

$$f_L = \frac{1}{2\pi R_{eq} C_1} \Rightarrow C_1 = \frac{1}{2\pi R_{eq} f_L}$$


$$\Rightarrow C_2 = \frac{1}{2\pi R_L f_L}$$

\Rightarrow finding Bypass Capacitor (C_E)

X_{C_E} must be less than or equal $\frac{R_E}{10}$

$$C_E = \frac{1}{2\pi f_L \cdot X_{C_E}} = \frac{1}{2\pi f_L \cdot 60}$$
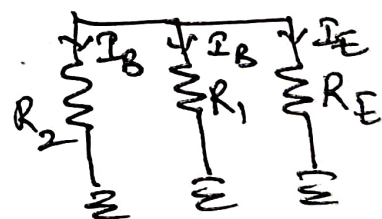
$$X_{C_E} = \frac{R_E}{10} = \frac{600}{10} = 60$$



$$R_{eq} = R_1 || R_2 || R_E$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_E} = \frac{R_1 R_2 R_E (1 + \beta)}{R_1 R_2 + R_2 R_E (1 + \beta) + R_1 R_E (1 + \beta)}$$

NOTE

$$I_E = I_B + I_C = I_B + \beta I_B = (1 + \beta) I_B$$