

Experiment 8: SCHMITT TRIGGER CIRCUITS

Aim/Objective: To Design a Schmitt trigger circuit using IC 741 and verify the output wave forms.

Pre-requisite: NI Multisim and MyDAQ

Description:

To design a Schmitt trigger for a given value of $+V_{sat}$, $-V_{sat}$, UTP and LTP.

$$+V_{sat} = V_{cc} - 3V \text{ (approx)}$$

$$-V_{sat} = V_{ee} + 3V \text{ (approx)}$$

Select V_{cc} and V_{ee} as per the design requirements. UTP and LTP depends on β i.e. $R_2 / (R_1 + R_2)$.

Select the resistors as per the UTP and LTP requirements.

$$V_{UTP} = \frac{R_2}{R_1 + R_2} V_{sat}$$

$$V_{LTP} = \frac{R_2}{R_1 + R_2} (-V_{sat})$$

Design a Schmitt Trigger for $+V_{sat} = 12V$ and $-V_{sat} = -12V$ and UTP and LTP as 4V and -4V.

For this requirement, $V_{cc} = +15V$ and $V_{EE} = -15V$ and the $\beta = 1/3$ (R_2 can be selected as 1K which gives R_1 as 2K)


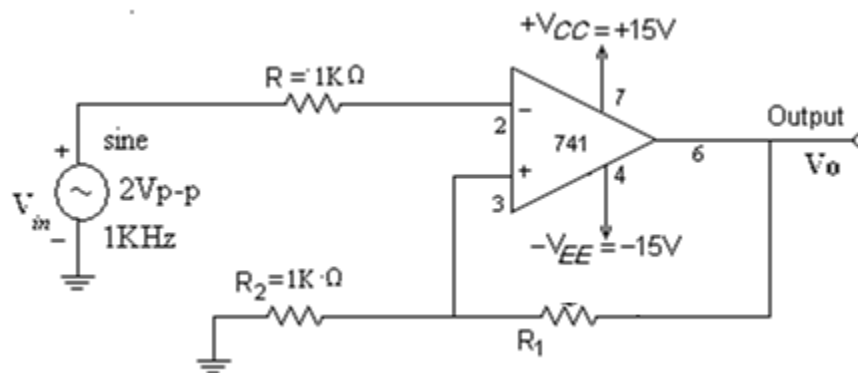


Figure 1: Schmitt trigger using IC 741

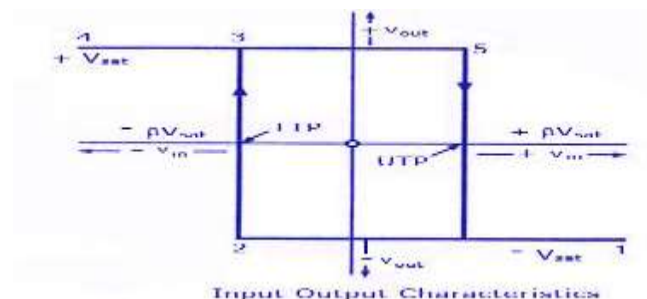


Pre-Lab Session

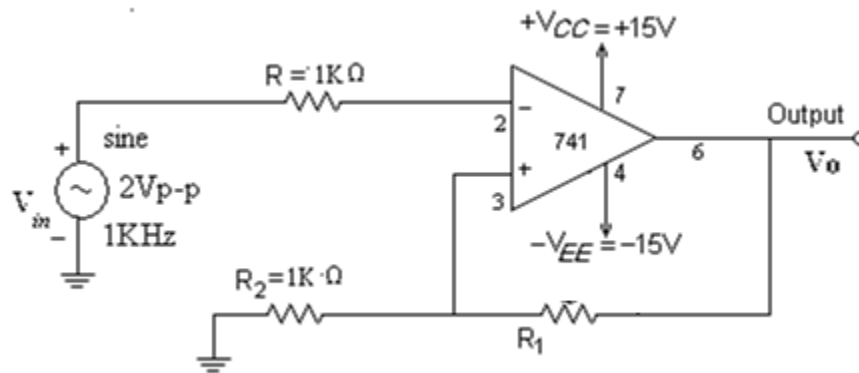- 1) What is a Schmitt Trigger and how does it differ from a simple comparator?
- 2) What is the duty cycle of the output square wave of the Schmitt Trigger?
- 3) Which type of feedback is used in Schmitt trigger?
- 4) Explain the role of the resistor network (R1 and R2) in the circuit shown. How does it affect the threshold levels?

In-Lab Session

It is a regenerative comparator or it is a comparator with hysteresis. This circuit uses positive feedback and the op-amp is operated in saturation. The output can take two values $+V_{sat}$ and $-V_{sat}$. When output = $+V_{sat}$, the voltage appearing at the non-inverting terminal is V_{UTP} . When output = $-V_{sat}$, the voltage appearing at the non-inverting terminal is V_{LTP} . When V_{in} is greater than UTP, the output will switch from $+V_{sat}$ to $-V_{sat}$. Similarly When V_{in} is less than LTP; the output will switch from $-V_{sat}$ to $+V_{sat}$ which is shown in the graph. The difference between UTP-LTP is called hysteresis. Hysteresis avoids false triggering of the circuit by noise. Hysteresis curve is the plot of V_o versus V_{in} . Schmitt trigger circuit is used to convert any irregular wave into square wave.




Procedure:

Using IC 741:

1. Connect the circuit as shown in fig 1(a) as Schmitt trigger using IC 741.
2. Give a 5 V_{p-p} sine wave of 1 kHz as input.
3. Observe the wave form on CRO and measure UTP and LTP, V_{sat} and $-V_{sat}$.
4. Use X-Y mode in CRO and observe hysteresis curve.
5. Repeat the above experiment for $R_1 = 5.1K\Omega$ and 15 K ohms and observe the effect.

Expected Waveforms

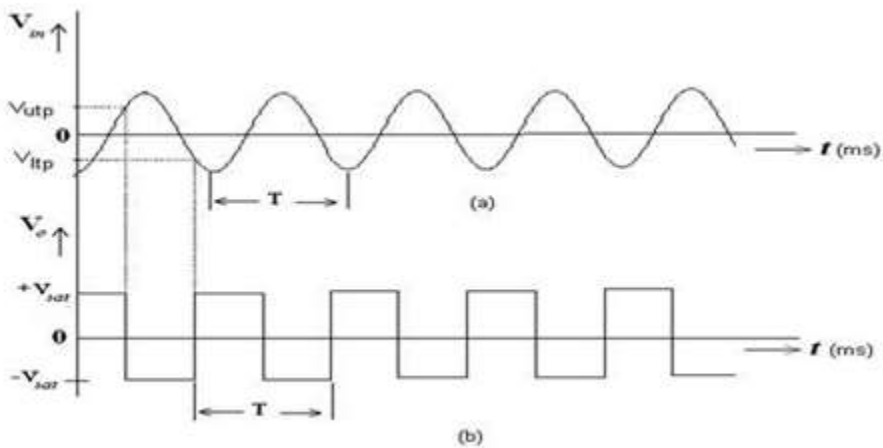

Analysis and Inference:

Parameter	Input	Output
Voltage(V_{p-p}), V		
Time period - Positive Half cycle(ms)		
Time period - Negative Half cycle(ms)		
	Theoretical	Observed
UTP		
LTP		

VIVA-VOCE Questions

1) A Schmitt Trigger circuit is primarily used to:

- A. Amplify analog signals
- B. Generate sine waves
- C. Convert noisy signals into clean digital transitions
- D. Multiply frequencies

2) The characteristic feature of a Schmitt Trigger is:

- A. Negative feedback
- B. High gain
- C. Hysteresis
- D. Low impedance

3) In a Schmitt Trigger, hysteresis refers to:

- A. Delay in output response
- B. Difference between two threshold levels
- C. Output oscillation frequency
- D. Input signal strength

4) A Schmitt Trigger can be implemented using:

- A. Low-pass filter
- B. Op-Amp with positive feedback
- C. Class B amplifier
- D. Zener diode

5) If the input signal is a slowly varying sine wave, the output of a Schmitt Trigger will be:

- A. A sine wave
- B. A triangular wave
- C. A square wave
- D. A constant voltage

Post-Lab Session

To analyze and understand the operation of a Schmitt Trigger circuit and explore its behavior with various input signals.

Apply a triangular wave and note the response

Result:

Studied the Schmitt trigger using opamps

Evaluator Remark (if Any):	Marks Secured: ____ out of 50
	Signature of the Evaluator with Date