
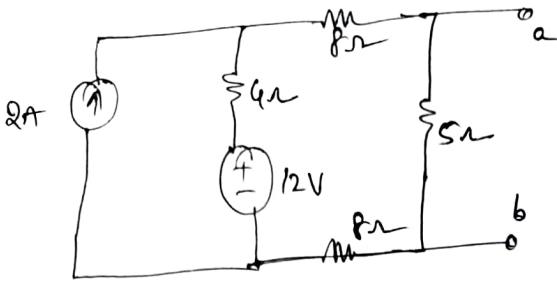


Norton's Theorem

①

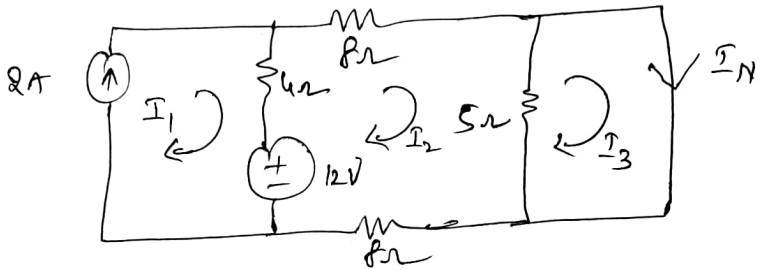

To find I_N : Short circuit a,b



$$I_1 = 2A$$

$$-12 + 4(I_2 - I_1) + 8I_2 + 5(I_2 - I_3) + 8I_2 = 0$$

$$-4I_1 + 25I_2 - 5I_3 = 12$$

Substitute I_1 ; $-4(2) + 25I_2 - 5I_3 = 12$

$$25I_2 - 5I_3 = 12 + 8 = 20$$

$$25I_2 - 5I_3 = 20 \quad \text{--- (1)}$$

$$5(I_3 - I_2) = 0$$

$$I_3 = I_2 \quad \text{--- (2)}$$


$$25I_2 - 5I_2 = 20$$

$$20I_2 = 20 \Rightarrow I_2 = 1A$$

$$I_3 = 1A$$

$$I_N = 1A$$

To find R_N :

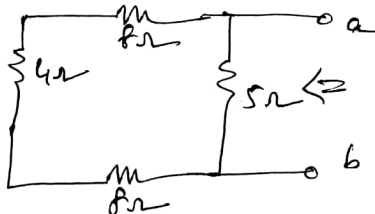

$$4 + 8 + 8 = 20\Omega$$


$$5\Omega \parallel 20\Omega = \frac{100}{25} = 4\Omega$$

Norton eq circuit:

$$R_N = 4\Omega$$




②

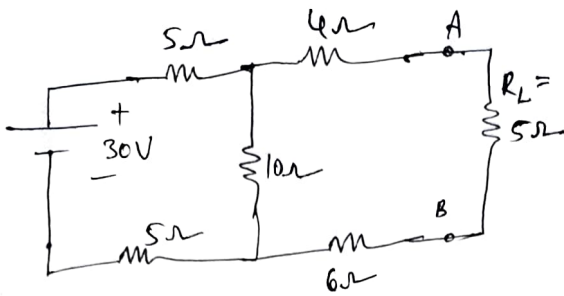

Current in load resistor
 $I_{5\Omega} = ?$ using Norton's theorem

Open A, B; short circuit. to find R_N

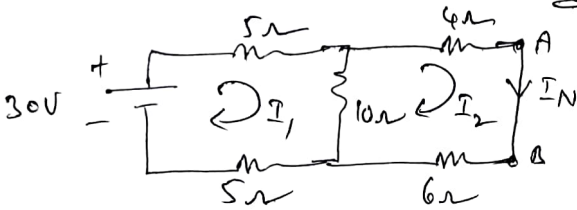

$$-30 + 5I_1 + 10(I_1 - I_2) + 5I_1 = 0$$

$$20I_1 - 10I_2 = 30 \quad \text{--- (1)}$$

$$10(I_2 - I_1) + 4I_2 + 6I_2 = 0$$


$$-10I_1 + 20I_2 = 0 \quad \text{--- (2)}$$

$$I_1 = 2A$$

$$I_2 = 1A$$

$$\text{So, } I_N = I_2 = 1A$$

Norton's resistance: R_N

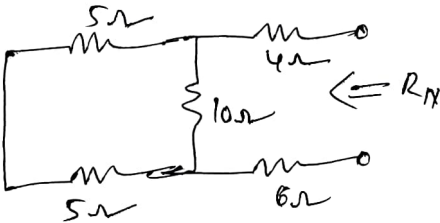


$$5 + 5 = 10\Omega$$

$$10 \parallel 10 = \frac{100}{20} = 5\Omega$$

$$5 + 4 + 6 = 15\Omega$$

Norton's eq circuit:

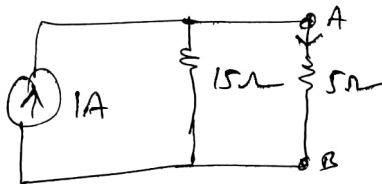

$$I_{AB} = I_{5\Omega} = 1 \times \frac{15}{15+5} = \frac{15}{20} = 0.75A$$