

ALM-1 - Brainstorming Session (24EC2104)

2400040454

2)

Illustrate with reason how Voltage divider bias help in stabilizing the operating point of a bjt amplifier Compared fixed bias!

Ans:

Voltage divider bias stabilizes the operating point better than fixed bias.

→ The Q-point (Quiescent point) is the dc current and Voltage of a transistor when no input signal

→ It sets the starting Condition of the transistor so it can amplify signals without distortion.

→ For good amplification, the Q-point should stay stable even if temperature or transistor parameter change.

<u>Fixed bias</u>	<u>Voltage Divider bias</u>
1) In fixed bias, a single Resistor R_b connects the base of the transistor to a Voltage source.	1) Voltage Divide bias two resistor (R_1 & R_2) to create stable Voltage at the base, plus an emitter resistor R_E for feedback.
2) Base Current I_B depend only on R_B and V_{CC}	2) Voltage Divide $V_B = V_{CC} \cdot \frac{R_2}{R_1 + R_2}$
3) Transistor p(gain) $I_C = \beta I_B$	3) A emitter resistance R_E creates negative feedback.
4, shift the Q-point,	

→ Voltage Divider bias provide a more stable and reliable Q-point by using a resistive divider and negative feedback, making it much better than fixed bias of amplifier design.