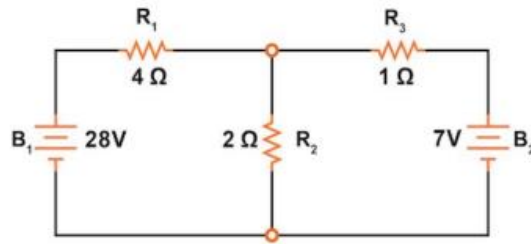


1. Calculate the current passes through the  $2\Omega$  resistor in the given network using the superposition theorem.




OR

State and Prove Superposition theorem?

In any linear circuit containing multiple independent sources, the current through (or voltage across) an element in this circuit is the algebraic sum of the currents through (or voltages across) that element due to each independent source acting alone.

Ans:

With first voltage source:

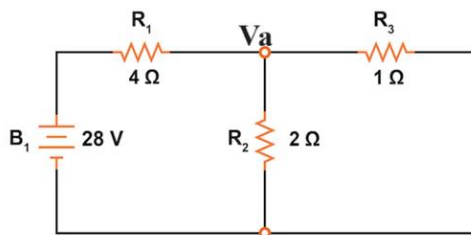

Using Nodal analysis:


$$\frac{(v_a - 28)}{4} + \frac{(v_a - 0)}{2} + \frac{(v_a - 0)}{1} = 0$$

solving the above equation

We will get  $V_a = 4V$

$$I_1 = V/R = 4/2 = 2A$$

With second voltage source:

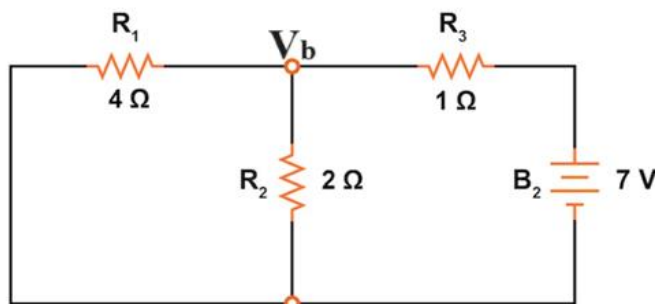

Using Nodal analysis:

$$\frac{(v_b - 0)}{4} + \frac{(v_b - 0)}{2} + \frac{(v_b - 7)}{1} = 0$$


solving the above equation

We will get  $V_b = 4V$

$$I_2 = V/R = 4/2 = 2A$$

Total current when two sources acting =  
 $2A + 2A = 4A$

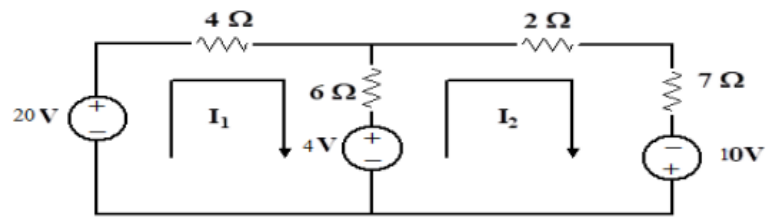2. Write the mesh equations and solve for the currents  $I_1$ , and  $I_2$



Mesh1 KVL Equation:

$$20 - 4I_1 - 6(I_1 - I_2) - 4 = 0$$

Mesh2 KVL Equation:

$$4 - 6(I_2 - I_1) - 2I_2 - 7I_2 + 10 = 0$$

Solve the above equations...


$$10I_1 - 6I_2 = 16$$

$$6I_1 - 15I_2 = -14$$

$$I_1 = 54/19 = 2.8\text{ A}$$

$$I_2 = 118/57 = 2.07\text{ A}$$

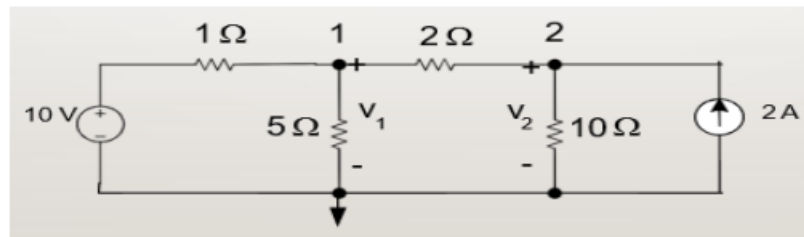3. Determine the voltage  $V_1$  and  $V_2$  using node analysis.



Node voltage equation at node 1

$$\frac{(v_1 - 10)}{1} + \frac{(v_1 - 0)}{5} + \frac{(v_1 - v_2)}{2} = 0$$

Node voltage equation at node 2


$$\frac{(v_2 - v_1)}{2} + \frac{(v_2 - 0)}{10} - 2 = 0$$

Solving above equations



We will get

$$v_1 = 9.09\text{V} \quad v_2 = 10.91\text{V}$$

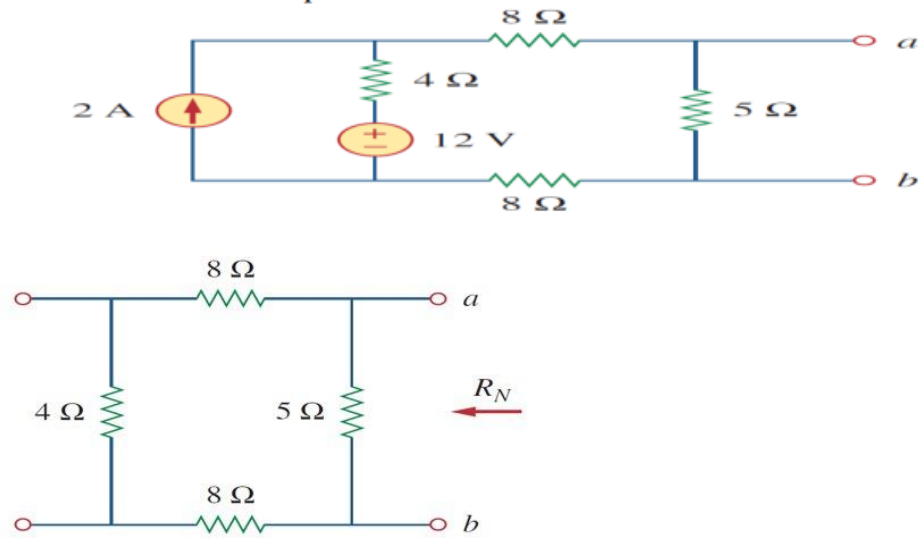4. Find the Norton's equivalent for the circuit shown below


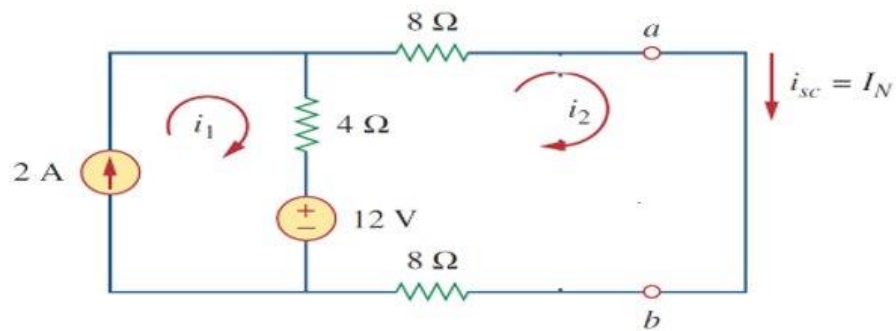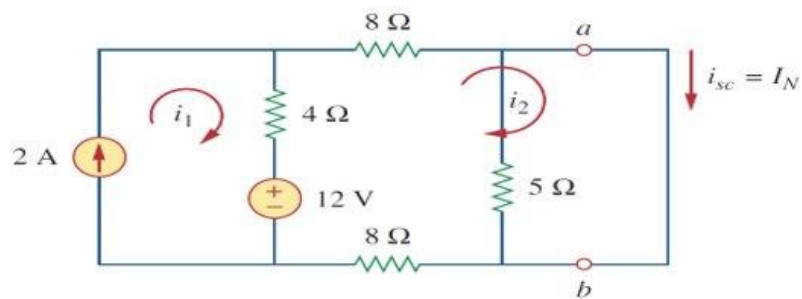
$$R_N = 5 \parallel (8 + 4 + 8) = 5 \parallel 20 = \frac{20 \times 5}{25} = 4 \Omega$$




**Applying Mesh analysis**

$$i_1 = 2 \text{ A}$$

$$20i_2 - 4i_1 - 12 = 0$$

$$i_2 = 1 \text{ A} = i_{sc} = I_N$$

**NORTON'S EQUIVALENT CIRCUIT**

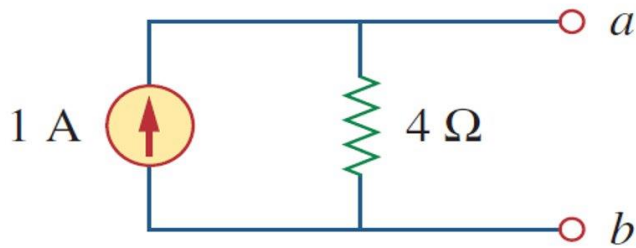

6. If four Inductors are connected in case i) parallel each of 60 Henry each ii) in series with  $L_1=L_2=10H$ ,  $L_3=L_4=20H$ , then calculate the total equivalence inductance in both cases?

Inductors are in parallel:

$$\frac{1}{L_{total}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \frac{1}{L_4}$$

$$\frac{1}{L_{total}} = \frac{1}{60} + \frac{1}{60} + \frac{1}{60} + \frac{1}{60}$$

$$\frac{1}{L_{total}} = \frac{4}{60}$$

$$L_{total} = \frac{60}{4} = 15H$$

Inductors are in series:

$$L_{total} = L_1 + L_2 + L_3 + L_4$$

$$L_{total} = 10 + 10 + 20 + 20$$

$$L_{total} = 60H$$

7. Calculate

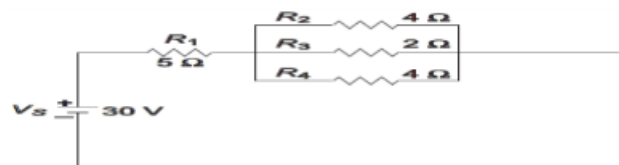


Fig. 1.34

Total Resistance in the circuit is  $R = 5 + (4 || 2 || 4) = 6\ \Omega$

OHMS law:  $V = I R$


$$V = 30V$$

$$R = 6\ \Omega$$


$$I = V/R = 30/6 = 5 \text{ Amp}$$
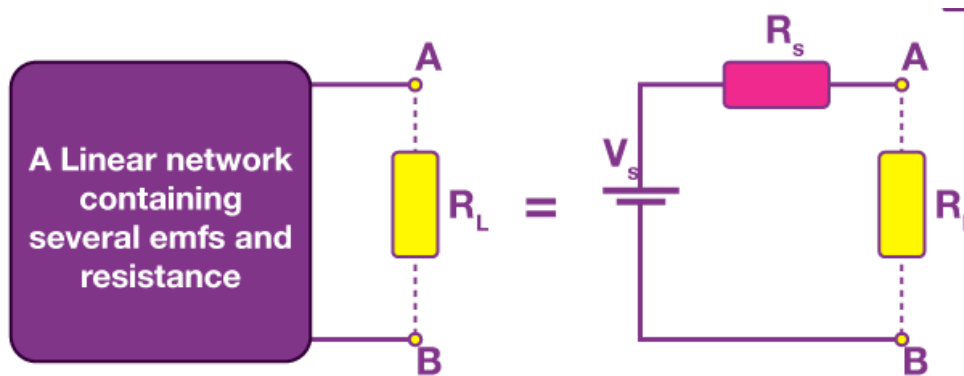
### 8. State and explain Thevenin's Theorem Explanation

Thevenin's theorem states that it is possible to simplify any linear circuit, irrespective of how complex it is, to an equivalent circuit with a single voltage source and a series resistance.




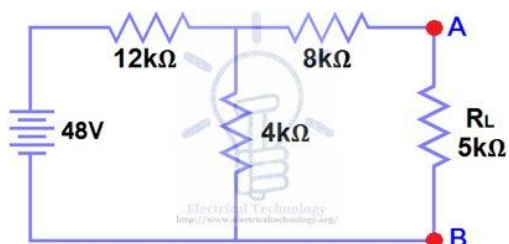Find  $V_{TH}$ ,  $R_{TH}$  and the load current flowing through and load voltage across the load resistor in figure by using Thevenin's Theorem.




Thevenin's Theorem. Easy Step by Step Procedure with Example (Pictorial Views)


**Step 1.** Open the 5kΩ load resistor

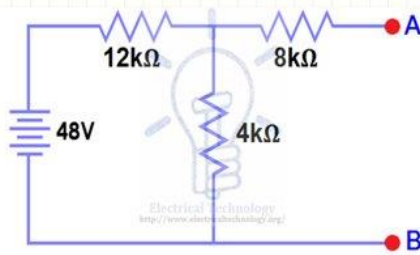

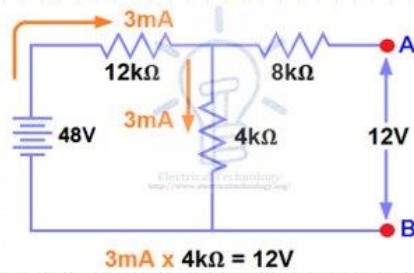
**Step 2.** Calculate / measure the Open Circuit Voltage. This is the Thevenin Voltage ( $V_{TH}$ ).



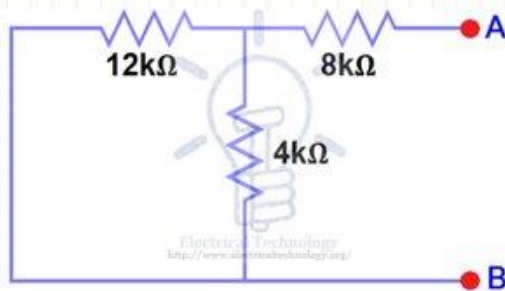
**Step 3.** Open Current Sources and Short Voltage Sources.



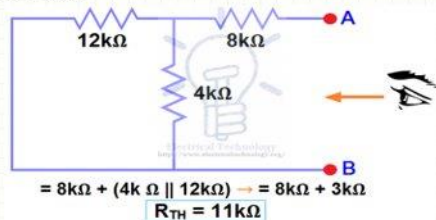
**Step 4.** Calculate /measure the Open Circuit Resistance. This is the Thevenin Resistance ( $R_{TH}$ ).



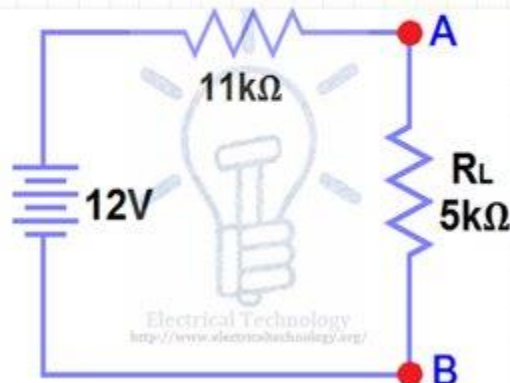**Step 5.** Connect the  $R_{TH}$  in series with Voltage Source  $V_{TH}$  and re-connect the load resistor. This is shown in fig (6) i.e. Thevenin circuit with load resistor. This is the Thevenin's equivalent circuit.



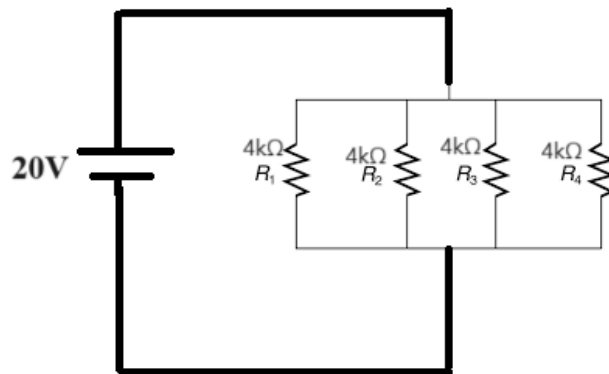11. If Four resistors  $R_1=R_2=R_3=R_4=4\text{k}\Omega$ , is connected in parallel with a power supply of 20V , then calculate total circuit current and individual currents flowing in each resistor



$$R = 4 \parallel 4 \parallel 4 \parallel 4 = 1\text{k}\Omega$$

$$I = V/R = 20 / 1\text{K} = 20\text{mA}$$

$$I_1 = V/R_1 = 20/4\text{K} = 5\text{mA}$$

$$I_2 = V/R_2 = 20/4\text{K} = 5\text{mA}$$


$$I_3 = V/R_3 = 20/4\text{K} = 5\text{mA}$$

$$I_4 = V/R_4 = 20/4\text{K} = 5\text{mA}$$



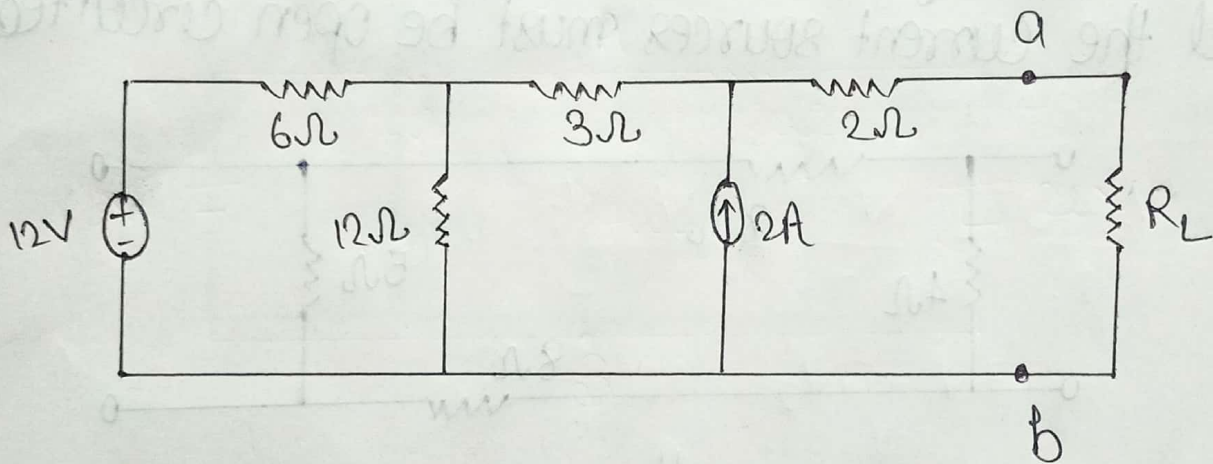
## Norton's Equivalent Circuit

⑤ Find the value of  $R_L$  for  $\max^m$  power transfer for the below mentioned circuit and also find the  $\max^m$  power



for  $V_{th}$

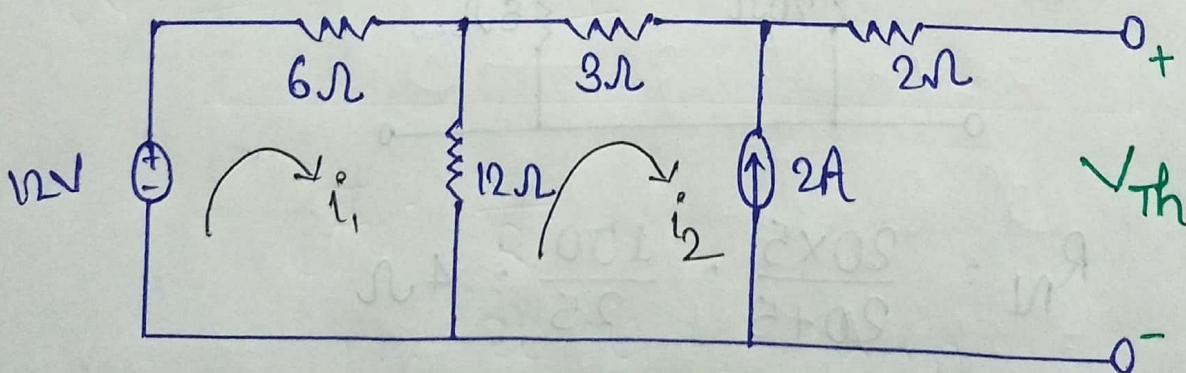

$$i_2 = -2A$$

$$6i_1 + 12(i_1 - i_2) = 12$$

$$18i_1 - 12i_2 = 12$$

$$18i_1 - 12(2) = 12$$

$$18i_1 = -12$$

$$i_1 = -\frac{2}{3} \text{ A}$$


$$6i_1 + 3i_2 + 2(0) = 12 - V_{Th}$$

$$-4 - 6 = 12 - V_{Th}$$

$$V_{Th} = 22 \text{ V}$$

for  $R_{Th}$

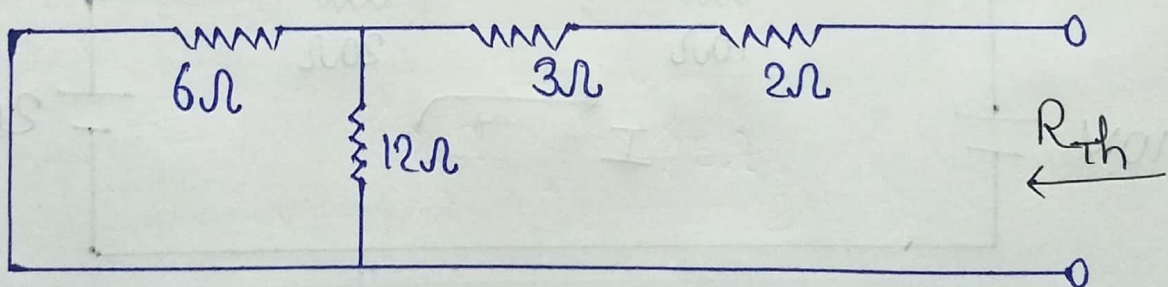- \* All the voltage sources must be short circuited
- \* All the current sources must be open circuited



$$R_{Th} = 5\Omega + \frac{6 \times 12}{6 + 12} = 5\Omega + 4\Omega$$

$$R_{Th} = 9\Omega$$



for max<sup>m</sup> power transfer



$$R_L = R_{Th} = 9\Omega$$

max<sup>m</sup> power

$$P_{max} = \frac{V_{Th}^2}{4R_L} = \frac{(22)^2}{4 \times 9} = 13.44W$$

$$P_{max} = 13.44W$$

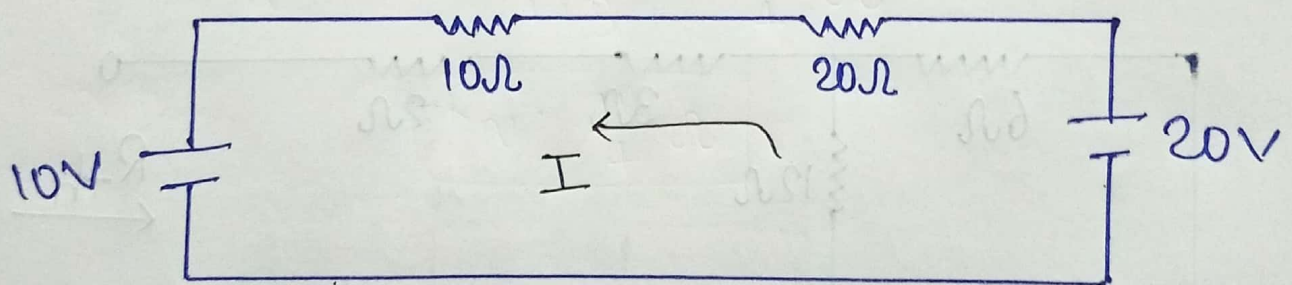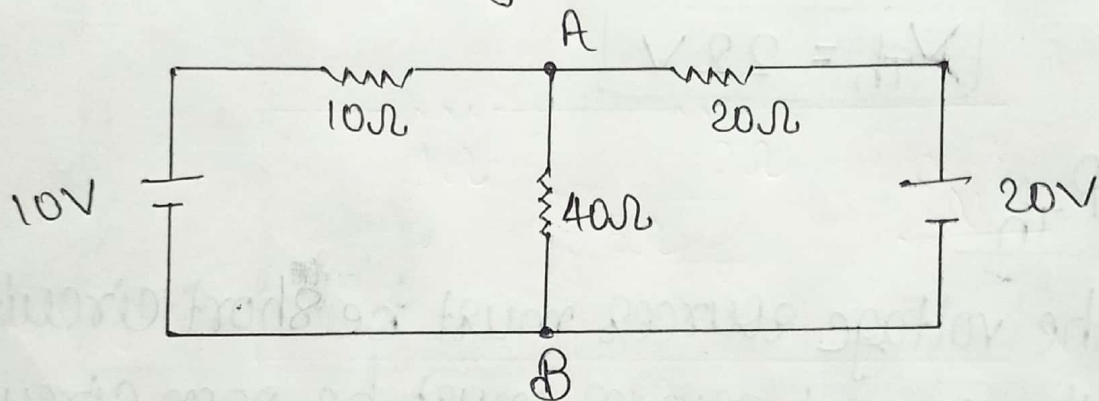
⑥ Find the Thevenin's voltage across 40Ω resistance in the given circuit?



$$I = \frac{V}{R}$$

$$I = \frac{20-10}{20+10} = 0.33A$$

$$I = 0.33A$$

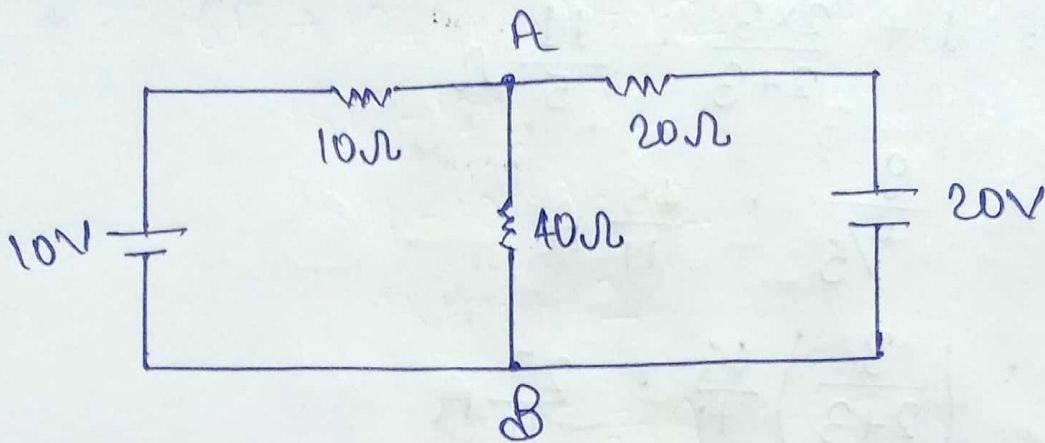


$$V_{AB} = 10V + (10\Omega \times 0.33A) = 13.33V$$


OR

$$V_{AB} = 20V - (20\Omega \times 0.33A) = 13.33V$$

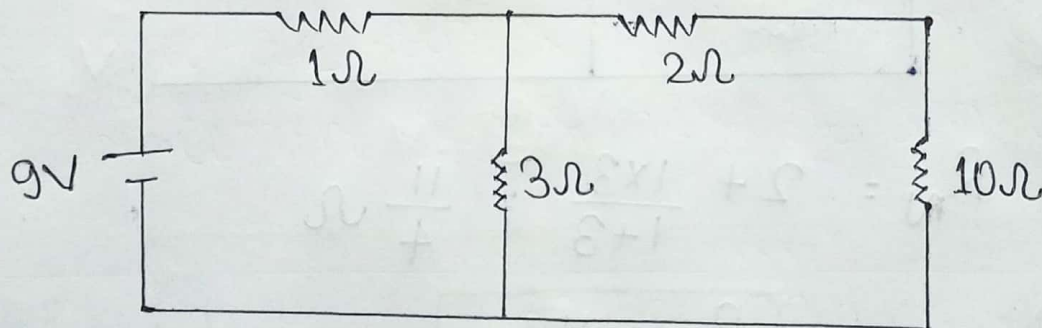⑦ Determine the current flowing through  $10\Omega$  resistor using Norton's theorem



for  $I_N$

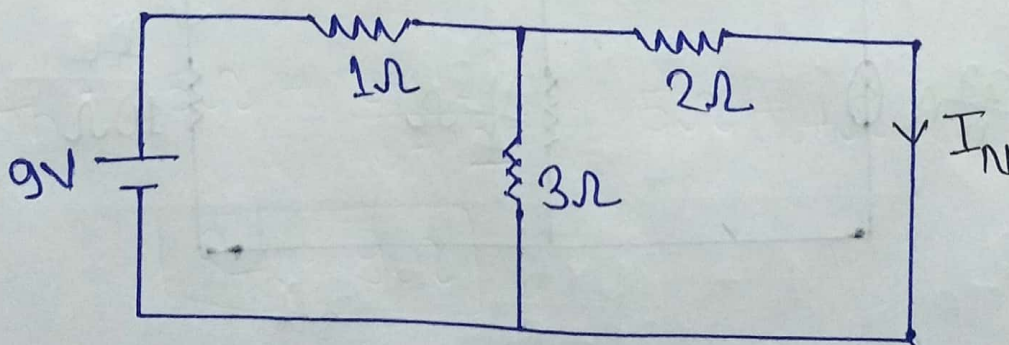




$$R_{eq} = 1 + \frac{2 \times 3}{2+3} = \frac{11}{5} \Omega$$

$$I = \frac{9}{11/5} = \frac{45}{11} A$$

$$I_N = \left( \frac{3}{2+3} \right) \frac{45}{11} = \frac{27}{11} A$$


$$I_N = \frac{27}{11} A$$

for  $R_N$

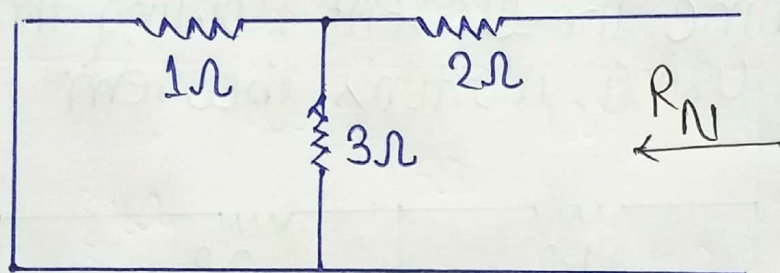

$$R_N = 2 + \frac{1 \times 3}{1+3} = \frac{11}{4} \Omega$$

$$R_N = \frac{11}{4} \Omega$$

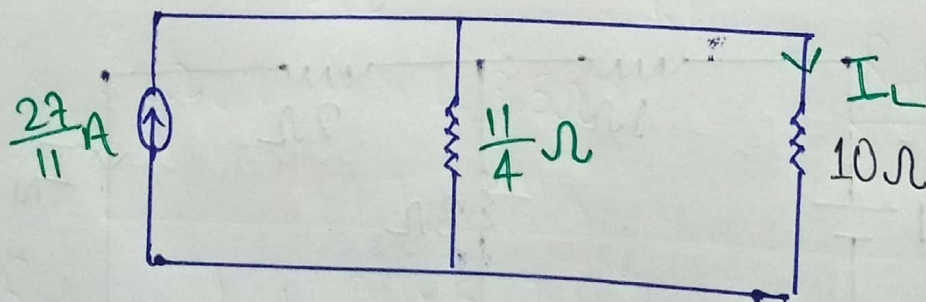


$$I_L = \left( \frac{\frac{1}{4}}{\frac{1}{4} + 10} \right) \frac{27}{11}$$

$$I_L = \frac{2.75 \times 27}{12.75 \times 11} = \frac{74.25}{140.25} \approx 0.529 \text{ A}$$

$$I_L = 0.529 \text{ A}$$

⑧ In the circuit shown in figure, determine the mesh currents  $i_1, i_2, i_3$

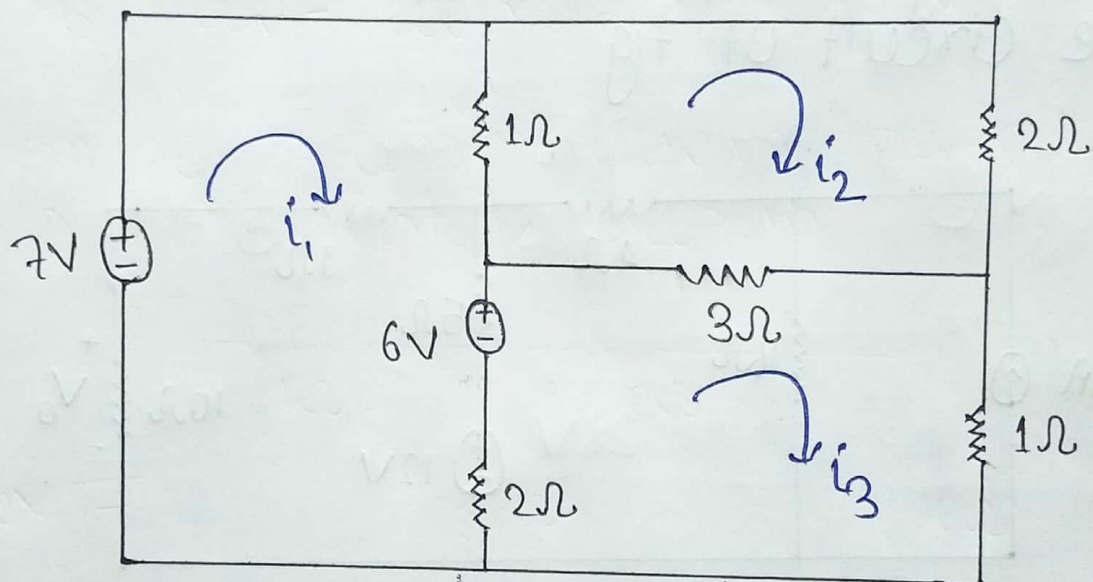

Mesh 1

$$1(i_1 - i_2) + 2(i_1 - i_3) = 7 - 6$$

$$3i_1 - i_2 - 2i_3 = 1 \quad \text{--- (i)}$$

Mesh 2

$$1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$$

$$-i_1 + 6i_2 - 3i_3 = 0 \quad \text{--- (ii)}$$



### Mesh 3

$$2(i_3 - i_1) + 3(i_3 - i_2) + i_3 = 6$$

$$-2i_1 - 3i_2 + 6i_3 = 6 \quad \text{--- (iii)}$$


from eq<sup>n</sup>: (i), (ii) & (iii), we get

$$i_1 = 3 \text{ A}$$


$$i_2 = 2 \text{ A}$$

$$i_3 = 3 \text{ A}$$

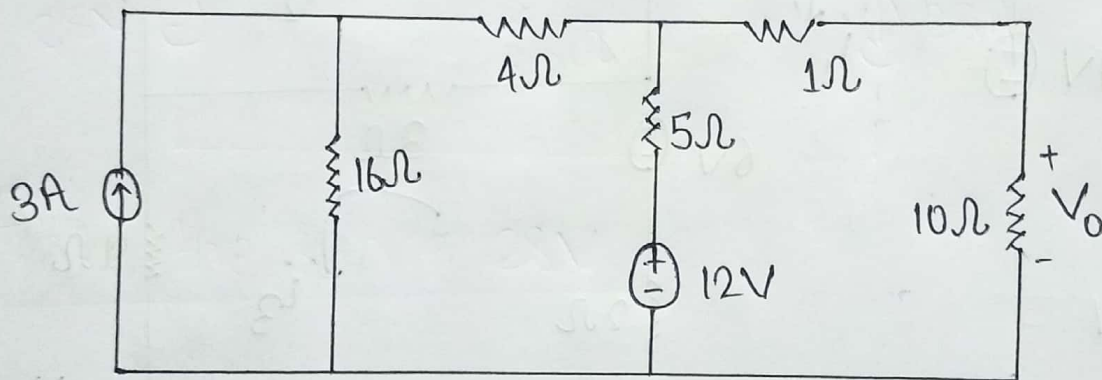(9) Apply Thevenin's theorem to find  $V_0$  in the circuit of fig




for  $R_{Th}$

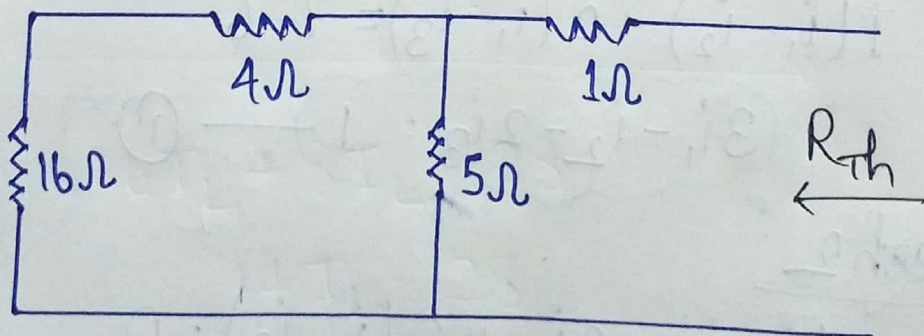

$$R_{Th} = 1 + \frac{20 \times 5}{20 + 5} = 5 \Omega$$

$$R_{Th} = 5 \Omega$$

for  $V_{th}$

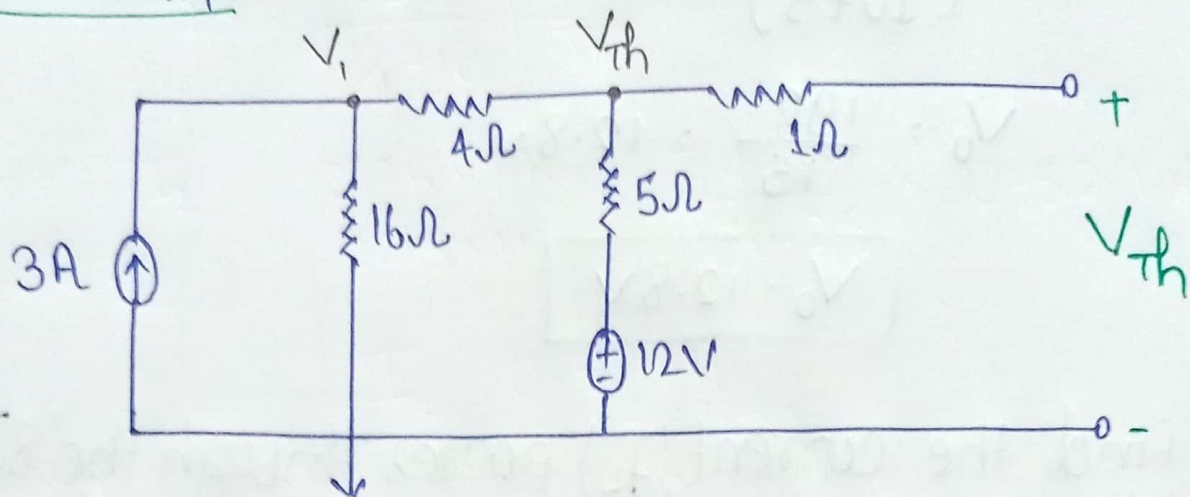

at node  $V_1$

$$\frac{V_1}{16} + \frac{V_1 - V_{th}}{4} = 3$$

$$5V_1 - 4V_{th} = 48 \quad \text{--- (i)}$$


at node  $V_{th}$

$$\frac{V_1 - V_{th}}{4} + \frac{12 - V_{th}}{5} = 0$$

$$5V_1 - 9V_{th} = -48 \quad \text{--- (ii)}$$

from eq<sup>n</sup>: (i) & (ii), we get

$$V_{th} = 19.2 \text{ V}$$

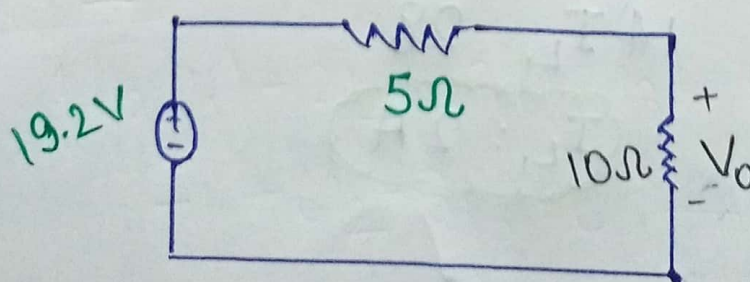




$$V_0 = \left( \frac{10}{10+5} \right) 19.2$$


$$V_0 = \frac{192}{15} = 12.8 \text{ V}$$

$$V_0 = 12.8 \text{ V}$$

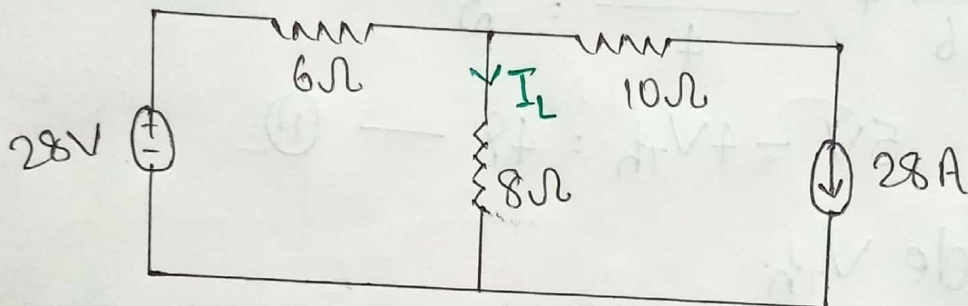(10) Find the current ( $I_L$ ) passes through the  $8\Omega$  resistor in the given network using the superposition theorem



Take the source 28V

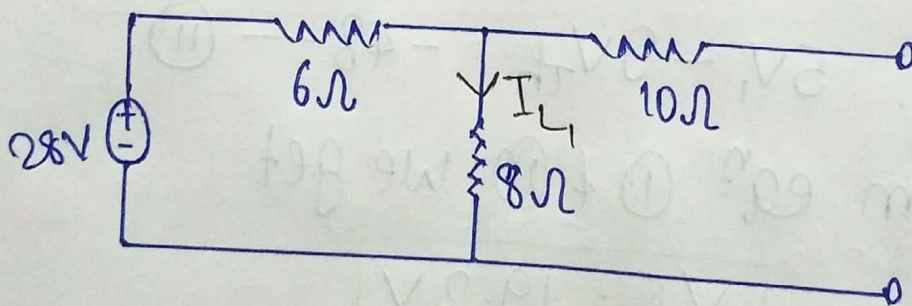


$$6I_L + 8I_L = 28$$

$$14I_L = 28$$

$$I_L = 2 \text{ A}$$

Take the source 28 A

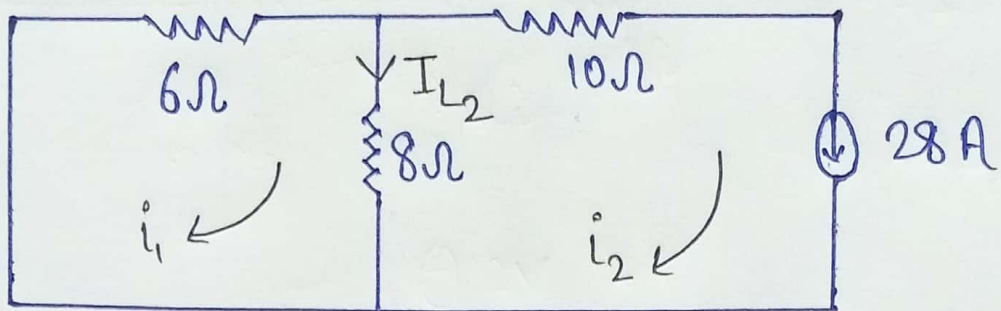

$$i_2 = 28 \text{ A}$$

$$6i_1 + 8(i_1 - i_2) = 0$$

$$14i_1 - 8i_2 = 0$$

$$14i_1 = 224$$

$$i_1 = 16 \text{ A}$$

$$I_{L2} = i_1 - i_2$$

$$I_{L2} = 16 - 28$$

$$I_{L2} = -12 \text{ A}$$

$$I_{L1} = 2 \text{ A}$$

$$I_{L2} = -12 \text{ A}$$

NOW,

$$I_L = I_{L1} + I_{L2}$$

$$I_L = -10 \text{ A}$$