



AY-2025-2026
ODD SEM

Department of ECE

ANALOG ELECTRONIC CIRCUIT DESIGN
24EC2104

Topic:

BJT BIASING CIRCUITS

Session - 04

SESSION CONTENT

- General Biasing Circuits
- Fixed Bias
- Emitter Feedback Bias
- Collector Feedback Bias

AIM OF THE SESSION



To demonstrate Biasing of BJT to desired Q-point

INSTRUCTIONAL OBJECTIVES

This Session is designed to:

1. Demonstrate BJT biasing circuits
2. Describe BJT desired operating point



LEARNING OUTCOMES

At the end of this session, you should be able to:



1. Describe BJT biasing circuits
2. Select biasing circuit for given application



Biasing in BJT Amplifier Circuits



- Fixed Bias(Base Bias)
- Self Bias/Voltage Divider Bias Circuits
- **Biasing Using a Collector-to-Base Feedback Resistor**
- Biasing using a Constant-Current Source

Biasing in BJT Amplifier Circuits

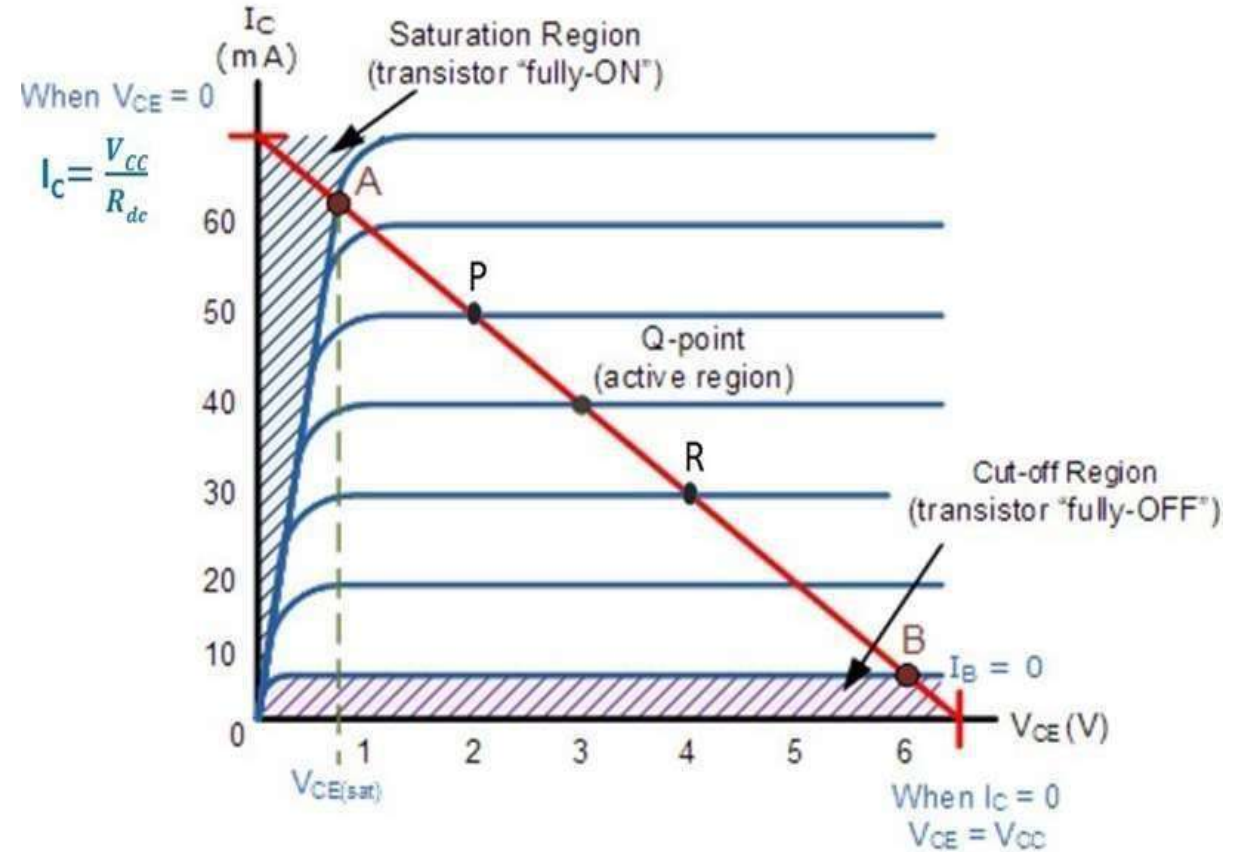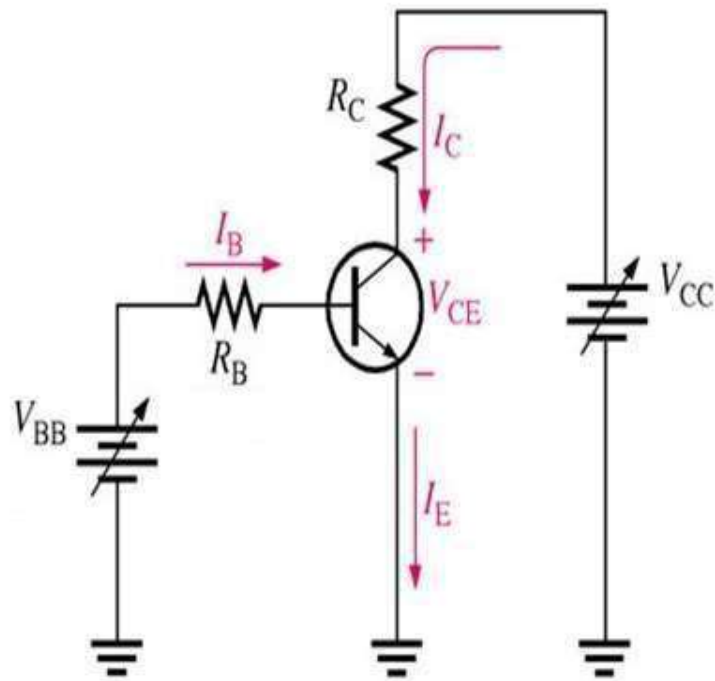


- ❖ The biasing problem is that of establishing a **constant dc current** in the collector of the BJT.

Biasing in BJT Amplifier Circuits

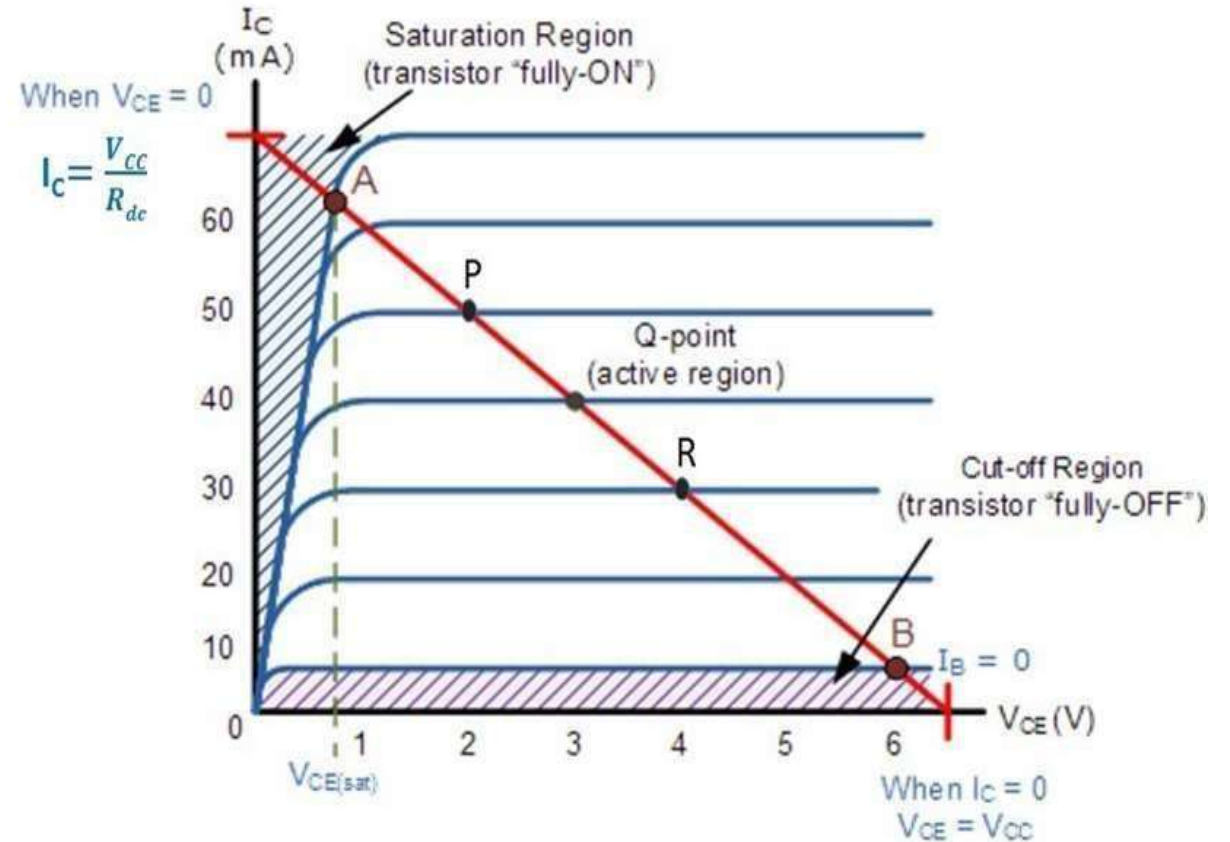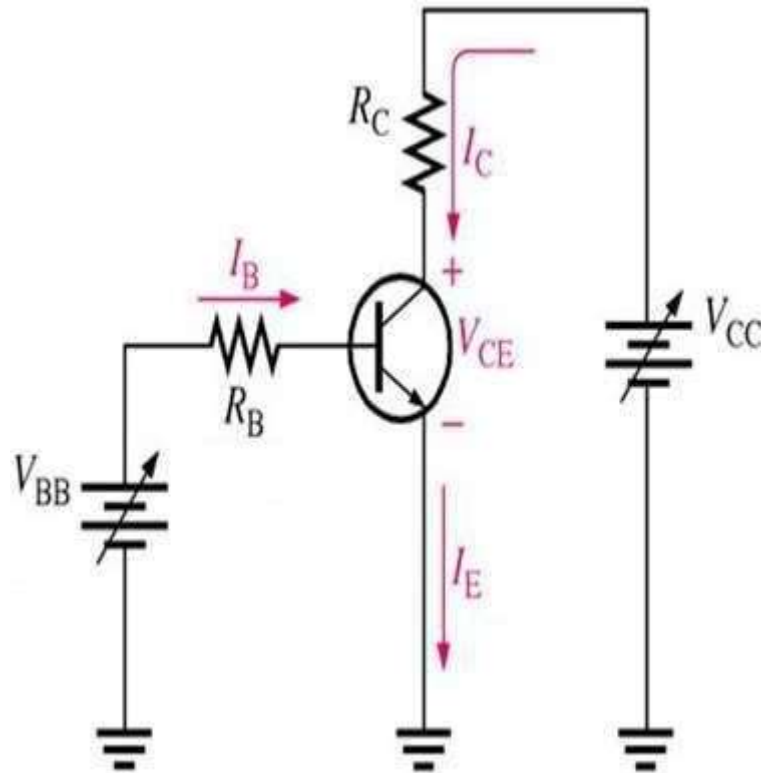


- ❖ This current has to be **calculable, predictable, and insensitive** to variations in temperature and to the large variations in the value of β encountered among transistors of the same type.

Biasing in BJT Amplifier Circuits

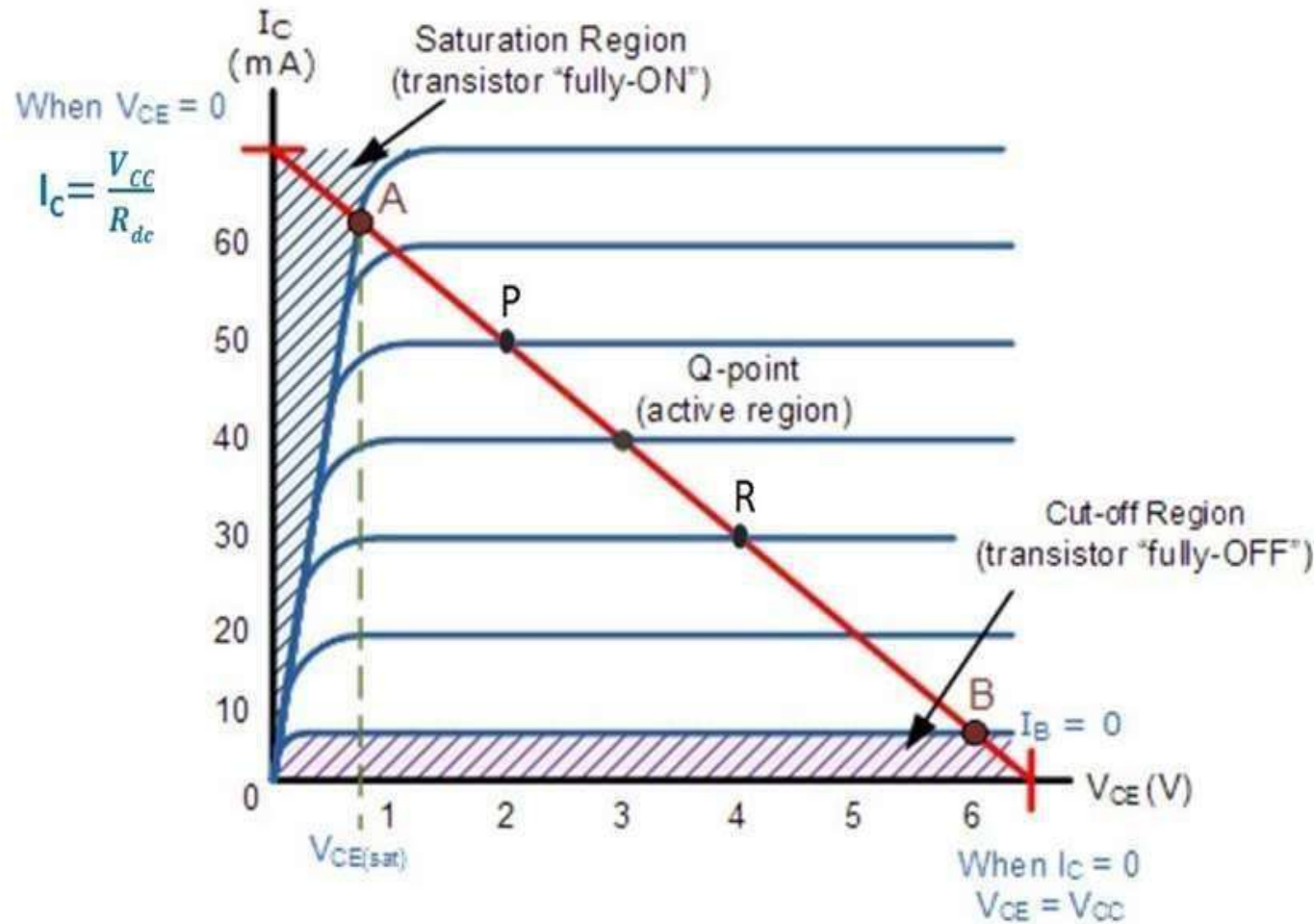


❖ Another important consideration in bias design is **locating the dc bias point in the i_C-v_{CE} plane to allow for maximum output signal swing.**

Fixed Bias/Base Bias

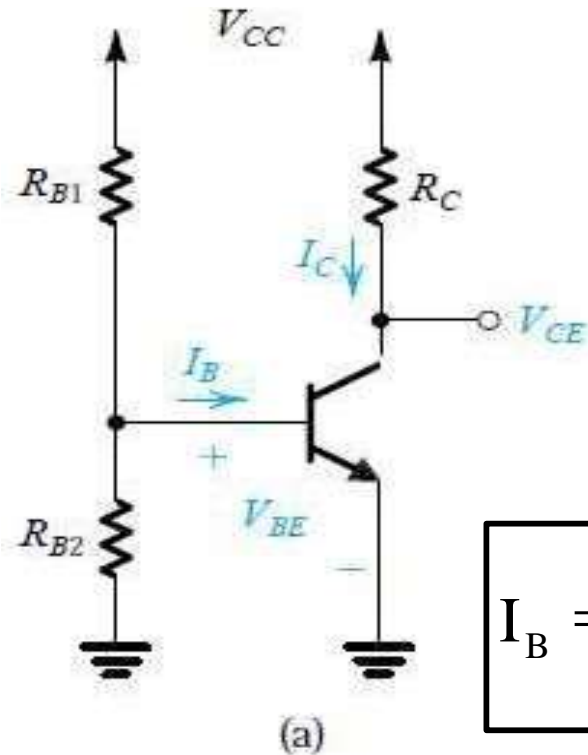

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

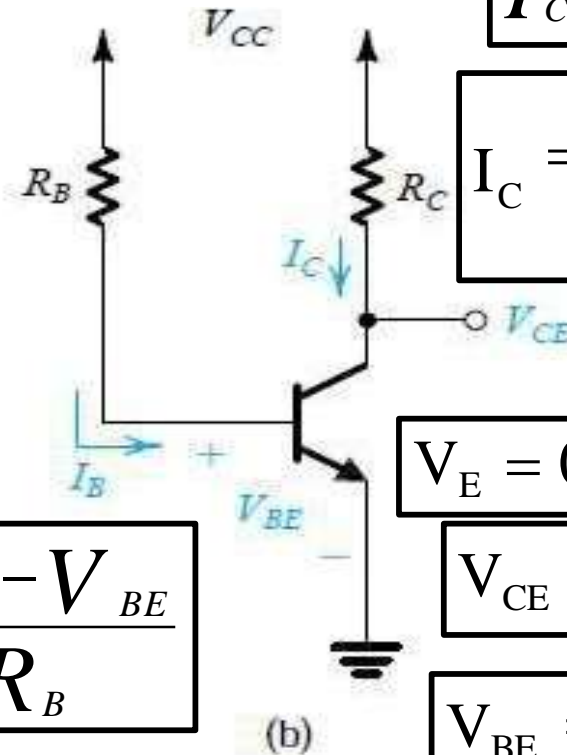

$$I_C = \beta I_B$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_E = 0$$

$$V_{CE} = V_C - V_E$$

$$V_{CE} = V_C$$

$$V_{BE} = V_B - V_E$$

$$V_{BE} = V_B$$

Two obvious schemes for biasing the BJT: (a) by fixing V_{BE} ; (b) by fixing I_B . Both **result** in wide variations in I_C and hence in V_{CE} and therefore are considered to be “bad.” Neither scheme is recommended.

GENERAL BIASING CIRCUITS

Base bias

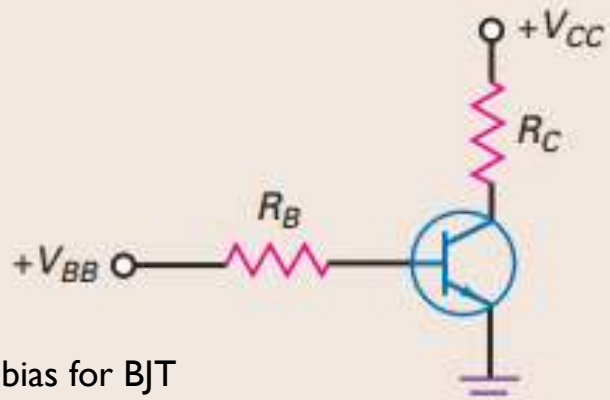


Fig. 4.1. Base bias for BJT

$$I_B = \frac{V_{BB} - 0.7 \text{ V}}{R_B}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_C R_C$$

Few parts; β dependent; fixed base current

Switch; digital



Fixed Bias/Base Bias

- First, attempting to bias the BJT by fixing the voltage V_{BE} by, for instance, using a voltage divider across the power supply V_{CC} , is **not** a viable approach:
- The very sharp exponential relationship i_C – v_{BE} means that any small and inevitable differences in V_{BE} from the desired value will result in large differences in I_C and in V_{CE} .
- Second, biasing the BJT by establishing a constant current in the base, which is also not a recommended approach.
- Here the typically large variations in the value of β among units of the same device type will result in correspondingly **large variations** in I_C and hence in V_{CE} .

Fixed Bias/Base Bias

ADVANTAGES OF FIXED BIAS CIRCUIT

1. Simple circuit as it uses few components.
2. It provides max flexibility, because the biasing conditions are easily set by changing the value of R_B .


DISADVANTAGES OF FIXED BIAS CIRCUIT

Poor stability

1. There is no means to stop self increase of I_C due to increase in temperature.
So, thermal stability is not provided.
2. If β increases due to transistor replacement then, I_C also increases by factor β
Therefore there is a chance of **thermal runaway** $I_C = \beta I_B$

GENERAL BIASING CIRCUITS

Emitter bias

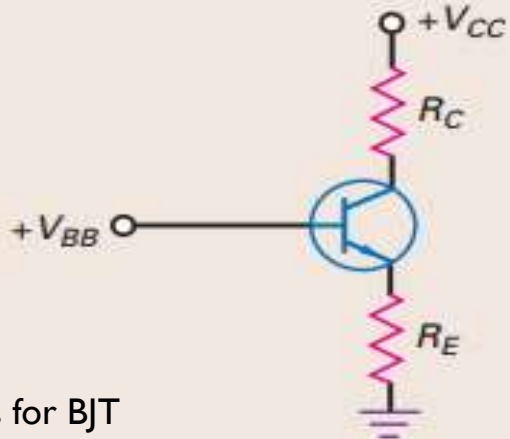

$$V_E = V_{BB} - 0.7 \text{ V}$$

$$I_E = \frac{V_E}{R_E}$$

$$V_C = V_{CC} - I_C R_C$$

$$V_{CE} = V_C - V_E$$

Fixed emitter
current; β
independent


I_C driver;
amplifier

Fig. 4.2. Emitter bias for BJT



GENERAL BIASING CIRCUITS

Two-supply emitter bias

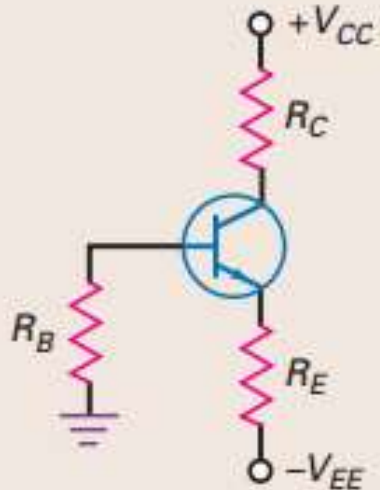

$$V_B \approx 0 \text{ V}$$

$$V_E = V_B - 0.7 \text{ V}$$

$$V_{RE} = V_{EE} - 0.7 \text{ V}$$

$$I_E = \frac{V_{RE}}{R_E}$$

$$V_C = V_{CC} - I_C R_C$$

$$V_{CE} = V_C - V_E$$

Needs positive
and negative
power
supplies; β
independent

Amplifier

Fig. 4.3. Two supply emitter bias for BJT



FIXED BIAS AND EMITTER FEED BACK BIAS

Fixed Bias

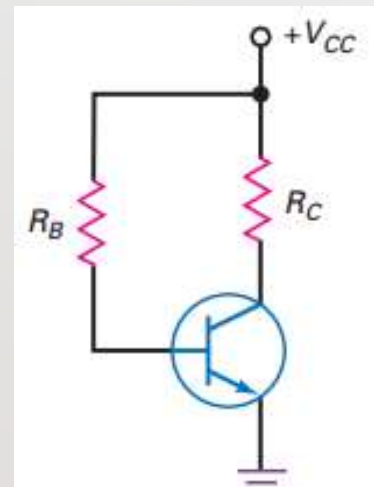


Fig. 4.4. Fixed Bias

- No Q-point Stabilization

Emitter Feedback Bias

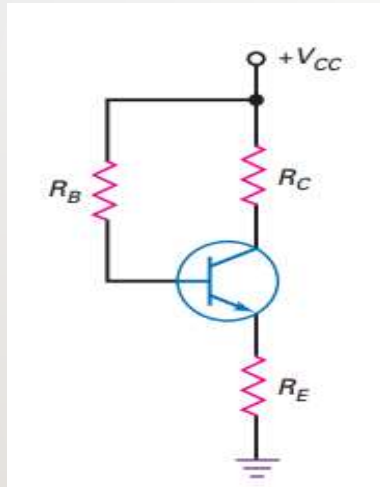


Fig. 4.5. Emitter Feedback Bias

- First attempt for Q-Point stabilization using Emitter resistance

Circuit Equations

$$I_E = \frac{V_{CC} - V_{BE}}{R_E + R_B/\beta_{dc}}$$

$$V_E = I_E R_E$$

$$V_B = V_E + 0.7 \text{ V}$$

$$V_C = V_{CC} - I_C R_C$$

- Design

Large R_E value to swap out variations in β_{dc}


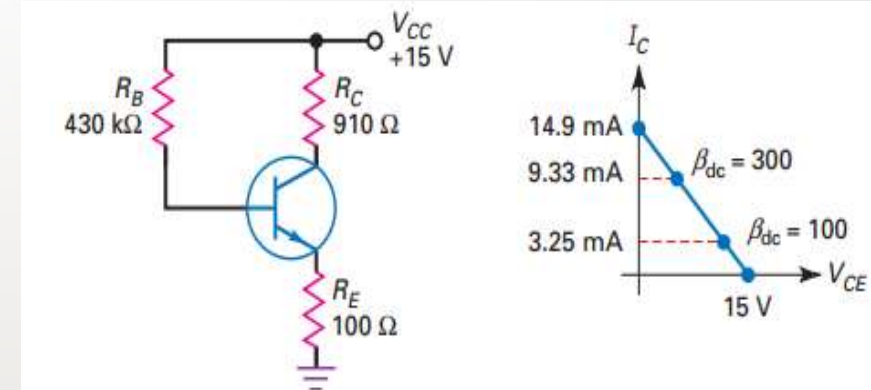


Fig. 4.6. Depicting Limitations of Emitter Feedback Bias – Variation in Q-point for change in β_{DC}

- Large change in collector current for 3:1 change in current gain


Biasing Using a Collector-to-Base Feedback Resistor

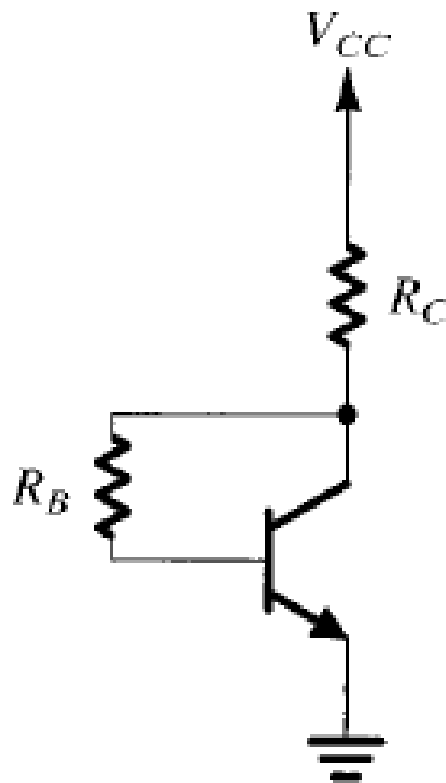❖ The circuit employs a resistor R_B connected



(3)

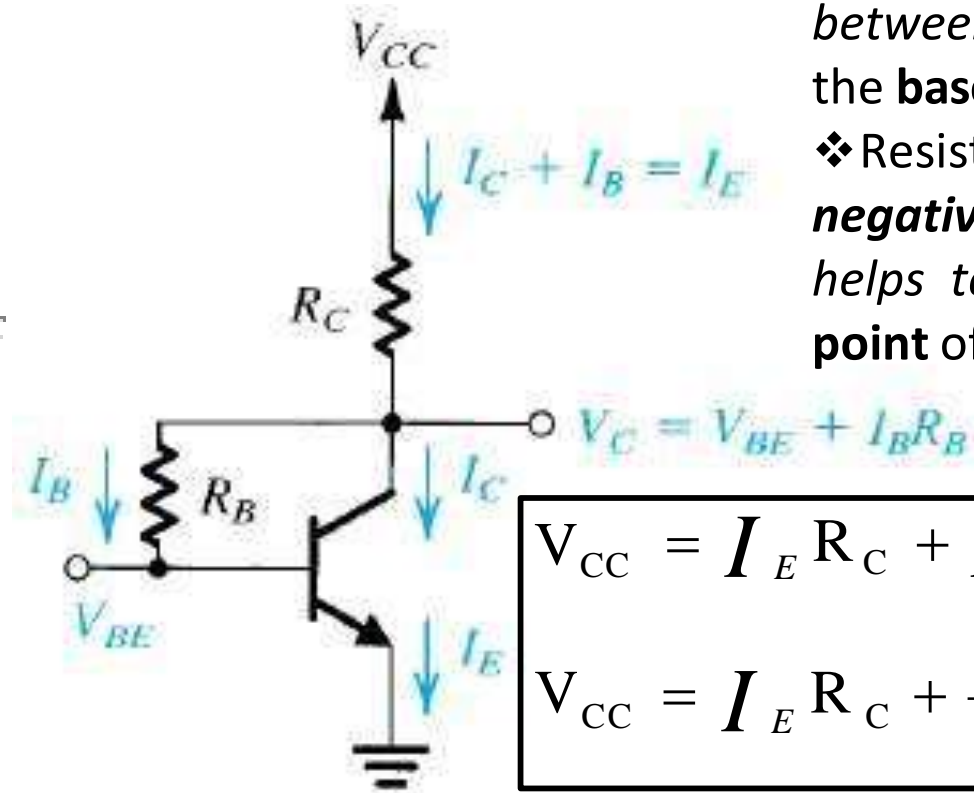(a) A CE transistor amplifier biased by a feedback resistor R_B .



(b)


(b) Analysis of the circuit in (a).

- ❖ The circuit employs a **resistor R_B** *connected between the **collector** and the **base**.*
- ❖ Resistor R_B *provides **negative feedback**, which helps to **stabilize the bias point** of the BJT.*

$$V_{CC} = I_E R_C + I_B R_B + V_{BE}$$

$$V_{CC} = I_E R_C + \frac{I_E}{\beta + 1} R_B + V_{BE}$$

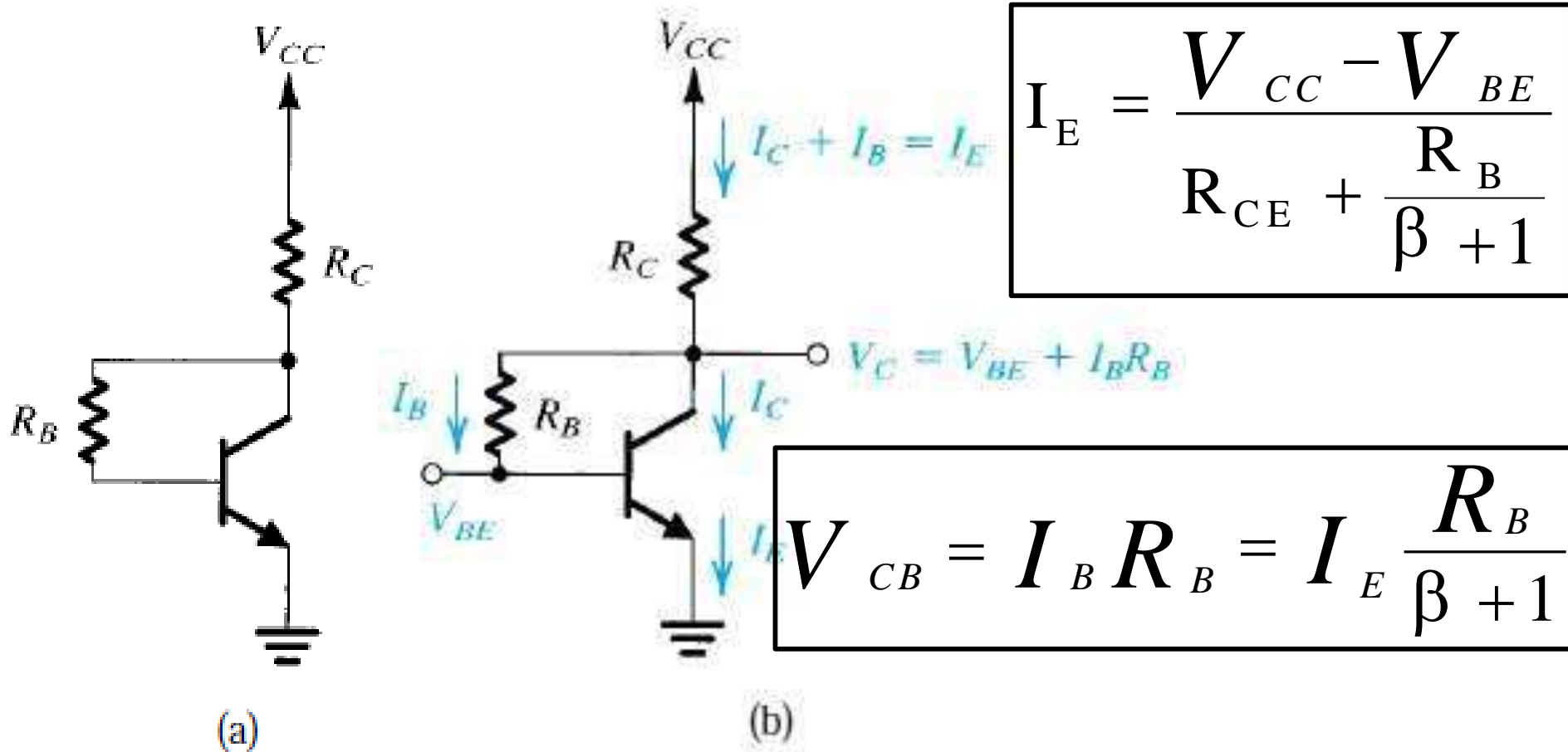
Biasing Using a Collector-to-Base Feedback Resistor




(a) A CE transistor amplifier biased by a feedback resistor R_B .

(b) Analysis of the circuit in (a).

Biasing Using a Constant-Current Source

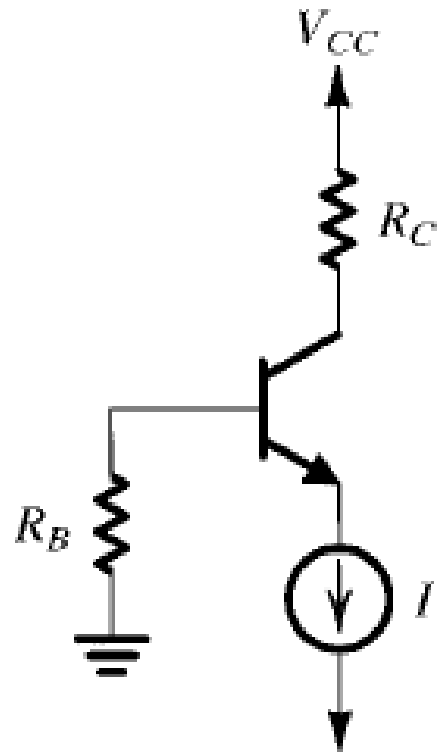

(a)

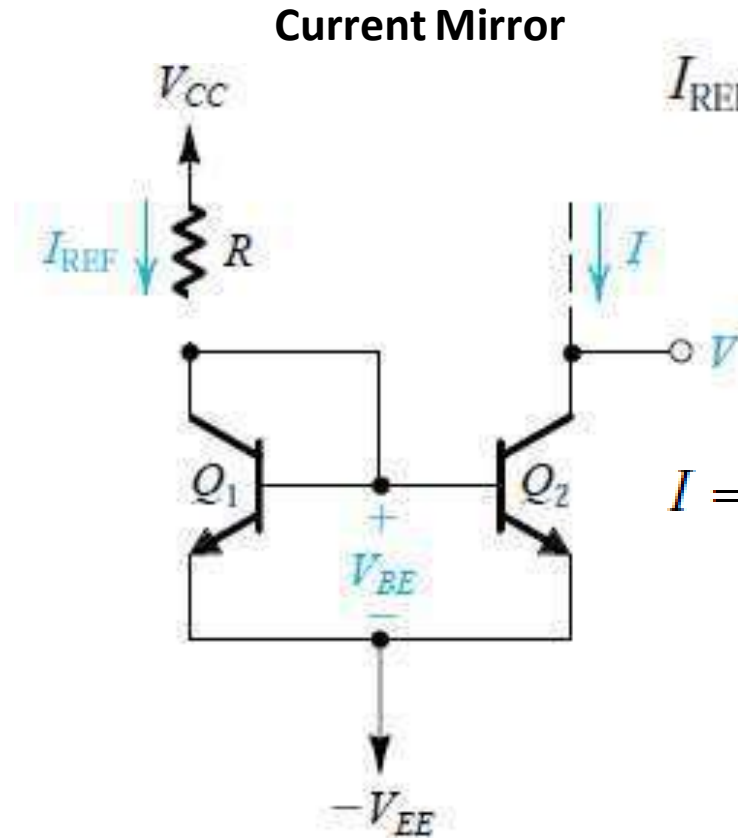


(b)

$$I_{REF} = \frac{V_{CC} - (-V_{EE}) - V_{BE}}{R}$$

$$I = I_{REF} = \frac{V_{CC} + V_{EE} - V_{BE}}{R}$$

COLLECTOR FEED BACK BIAS

Collector Feedback Bias

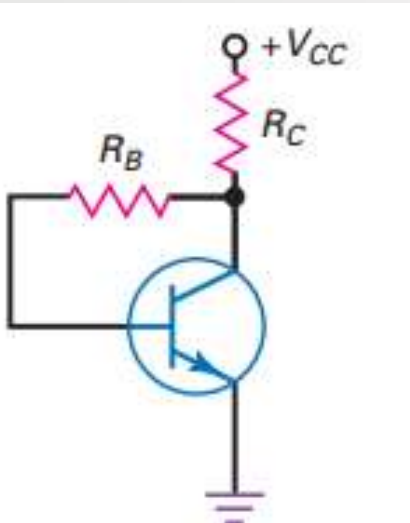

Circuit Equations

$$I_E = \frac{V_{CC} - V_{BE}}{R_C + R_B/\beta_{dc}}$$

$$V_B = 0.7 \text{ V}$$

$$V_C = V_{CC} - I_C R_C$$

• Design

$$R_B = \beta_{dc} R_C$$

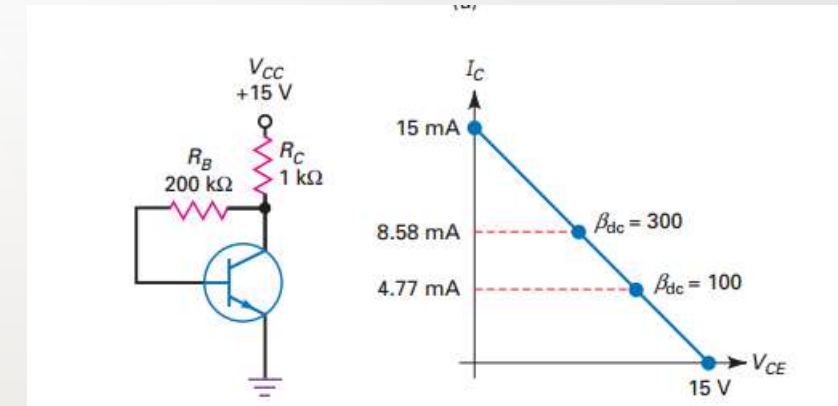


Fig. 4.8. Q-point for change in β_{DC}

- Better Q-Point stabilization using Collector feedback resistance

- Q point is less sensitive to changes in current gain

Example Problems

4.1 Calculate the Emitter resistance for Emitter bias as shown in Fig. 4.9 which could drive an LED of 21 mA Fig. 4.9.

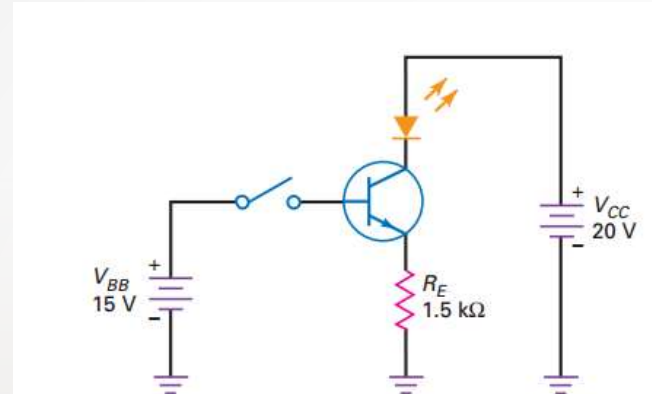


Fig. 4.9. Emitter bias for LED driving

Solution: Considering $I_E \sim I_C$

$$I_E = 21 \text{ mA}$$

KVL in input loop gives

$$V_{BB} = V_{BE} + I_E R_E$$

$$\text{Now, } R_E = (15 - 0.7) / (21 \text{ mA}) = 680 \, \Omega$$

Example Problems

4.2. Identify the application of the Base Biased BJT circuit shown in Fig. 4.10.

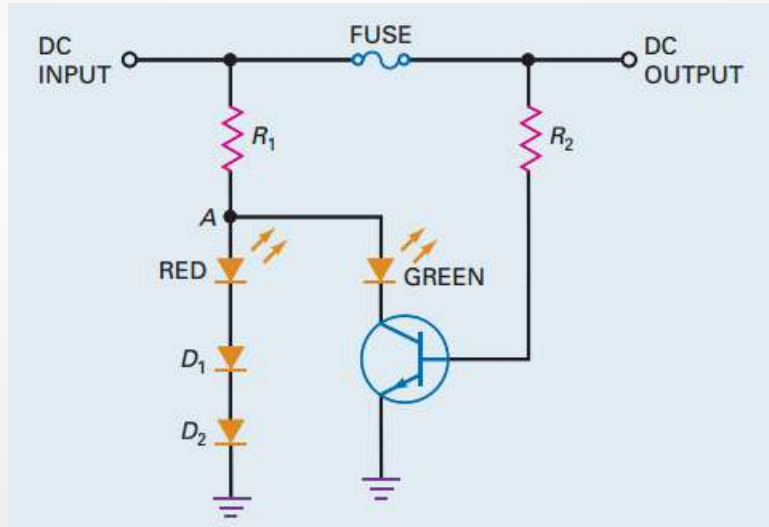


Fig. 4.10. Base bias for BJT

SOLUTION This is a blown-fuse indicator for a dc power supply. When the fuse is intact, the transistor is base-biased into saturation. This turns on the green LED to indicate that all is OK. The voltage between point A and ground is approximately 2 V. This voltage is not enough to turn on the red LED. The two series diodes (D_1 and D_2) prevent the red LED from turning on because they require a drop of 1.4 V to conduct.

SELF-ASSESSMENT QUESTIONS

1. Which Bias is suitable for Digital circuits?

- (a) Emitter Bias
- (b) Base Bias
- (c) Collector feedback Bias
- (d) Emitter feedback Bias

2. Which of the following bias is less effected by Beta variation?

- (a) Emitter feedback bias
- (b) Collector feedback bias

SELF-ASSESSMENT QUESTIONS

3. Which of the following biasing is suitable for IC driver application?

- (a) Emitter Bias
- (b) Base Bias
- (c) Collector feedback Bias
- (d) Emitter feedback Bias

4. Operating point of the BJT does not depend on temperature

- (a) False
- (b) True

ANSWERS

1. B
2. B
3. A
4. A

TERMINAL QUESTIONS

1. Describe the operation of Base bias. Sketch circuit obtain operating point.
2. Describe the operation of Emitter bias. Sketch circuit obtain operating point.
3. Describe the operation of two-supply bias. Sketch circuit obtain operating point.
4. Describe the operation of Fixed bias. Sketch circuit obtain operating point.
5. Describe the operation of Collector feedback bias. Sketch circuit obtain operating point.

REFERENCES FOR FURTHER LEARNING OF THE SESSION

Reference Books:

1. Albert Malvino, David Bate, “Electronic Principles”
2. Robert L. Boylestad and Louis Nashelsky - “Electronic Devices and Circuit Theory”

THANK YOU



Team – ANALOG ELECTRONIC CIRCUIT DESIGN

Prepared by – Mr. S. Ravi Teja