

23 | 9 | 24.

CO-3.

PWV


$$\underline{5V - 72V}$$

OP-AMP. → Analog.

- Voltage controlled voltage source
- High gain differential amplifier.

→ In form \*

Open loop  $\Rightarrow$  No feedback.

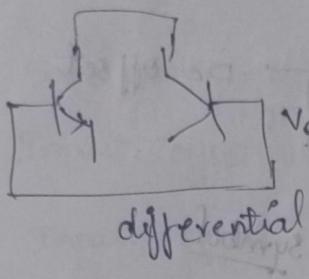

$$V_0 = V_1 - V_2$$

## differential amplifier.

## voltage amplifiers

$\mu A$   $\text{74IC} \leftrightarrow \text{omp}$

- metal can (TO) package
  - Dual in line (DIP)
  - flat package (chip pins)

manufactured by - fairchild - ua-741

## Natural semiconductors

## Texas industries.



~~Working~~ → ~~No connection~~  
~~power~~ → ~~mine~~

active pins  
 functional pins  
power.

capable of  
 taking ip  
 (ip, op, vcc, vdd)


# Op-Amp (741)

pin diagram.

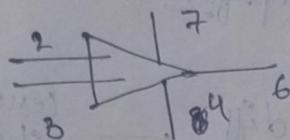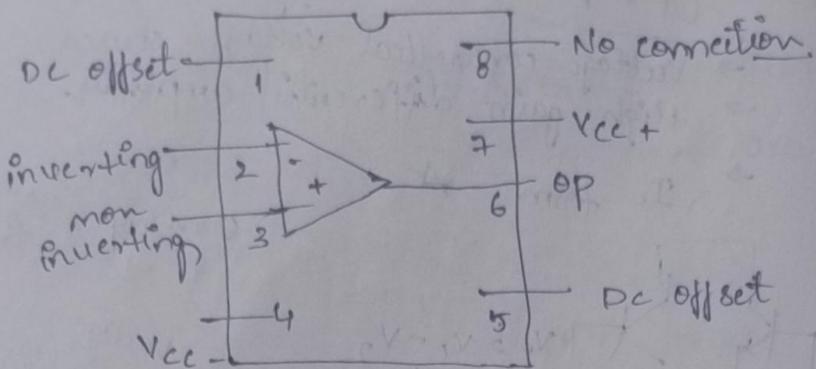

symbol

① high gain differential amplifier.

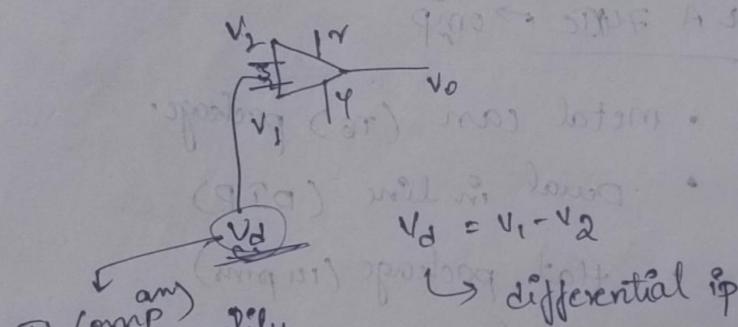

If (comp) <sup>any</sup> should amplify

higher where

differential ip


Vo  $\propto$  Vd

$$V_{oL} = A_{OL} V_d$$

$$\frac{V_o}{V_d} = A_{OL} \text{ open loop}$$

(Gain  $\cdot$  OP/ip).
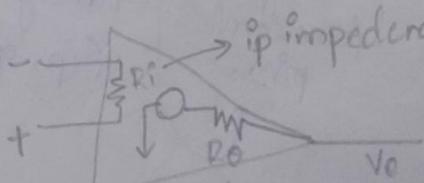
$$A_{OL} = \frac{V_o}{V_d} = \frac{V_o}{V_{in}}$$



ip impedance

op impedance

## Ideal characteristics:


Suitable for high gain (20V)

- ① Input impedance  $R_{in} | Z_{in} = \infty$  source
- ② can drive  $\infty$  load  $\Rightarrow R_{in} = \frac{V_{in}}{I_{in}} = \infty$
- ③ output impedance  $= 0$  means opamp is not drawing any current
- ④ Bandwidth  $= \infty$  more op can be connected
- ⑤ Input offset voltage  $= 0$
- ⑥ Input offset current  $= 0$
- ⑦ open loop gain  $= \infty$  Ad differential mode gain
- ⑧ CMRR  $\rightarrow \infty$  common mode gain, common mode rejection ratio, common mode rejection rate,  $V_{cm}$ ,  $Ad/AC$
- ⑨ common mode voltage  $\approx \frac{V_1 + V_2}{2}$  when  $V_1 = V_2$  what better  
should be rejected and ideally  $= 0$  rejection rate.  
 $V_d$  is to be considered.
- ⑩ slew rate  $\rightarrow$  time taken to react for given ip  
Rate of change of op when step ip given

$$\frac{dV_o}{dV_i} = \frac{\Delta V_o}{\Delta V_i} = \frac{V}{t} \text{ V/μs}$$

(NOS) input offset voltage  
 Step (FOS)  
 " bias current  
 " current  
 (IB)

$I_B$  = differential amplifier.

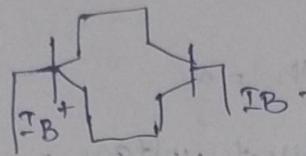

$$I_B = \frac{I_{B+} + I_{B-}}{2}$$

offset.  $\Rightarrow i_p = 0 \rightarrow O_P = 0$  not possible b/c of  
internal R | temp.

min voltage / current to nullify the op.

input offset voltage

or

input offset current.

$$I_{OS} = |I_{B+} - I_{B-}|$$

$$\text{for BJT } N_{OS} = 50 \text{ pA} \rightarrow 10^{-12}$$

$$\text{for FET } N_{OS} = 50 \text{ pA}$$

$$\text{for } I_B - BJT = 200 \text{ pA}$$

$$\text{for FET } I_B = \frac{200 \text{ pA}}{\frac{V_b}{9V_b}}$$


$$\frac{V_b}{9V_b}$$

## Equivalent circuit

$$V_o = A_{OL} V_{in} \rightarrow \text{op voltage}$$

↔ open loop gain

DC

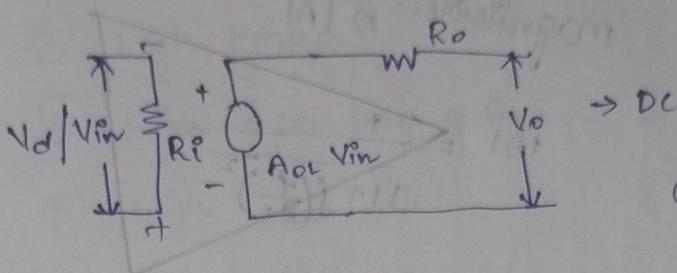

gain = const


for higher frequency there is  $\omega$  roll off,

gain starts to

roll off.

which is


compensated by capacitor at op

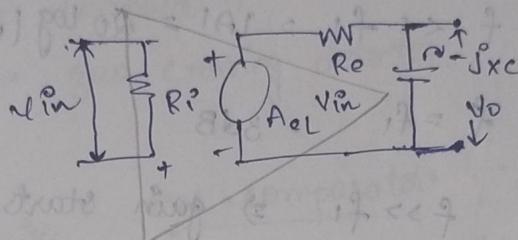

## A.C. characteristics

### ① Frequency response, equation for $\frac{\text{dB}}{\text{dB}}$

logarithmic freq

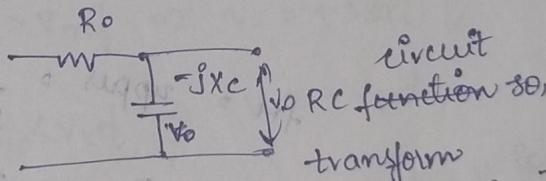

circuit

to RC function

transform

function

$$\frac{-jX_c A_{OL}}{R_o + jX_c}$$

$$A = \frac{-jX_c}{R_o + jX_c} A_{OL}$$

$$= \frac{1}{1 + j\omega R_o C} A_{OL}$$

$$\text{decay} \Leftrightarrow f_1 = \frac{1}{2\pi R_o C} \quad \begin{matrix} \text{cutoff frequency} \\ \text{corner frequency} \end{matrix}$$

$$\Rightarrow A = \frac{1}{1+j(\frac{f}{f_1})} A_{02}$$

\*  
\*

magnitude  $\Rightarrow |A|$

$$|A| = \frac{1}{\sqrt{1+j(\frac{f}{f_1})^2}}$$

$$\text{phase } (\phi) = \tan^{-1}(\frac{f}{f_1}).$$

magnitude plot,

$$f \ll f_1 \Rightarrow |A| = 20 \log |A_{02}|$$

$$f = f_1 = 3 \text{ dB}$$

$f \gg f_1 \Rightarrow$  gain starts to roll off  
at once only

there is only 1 corner freq so one roll off

~~decay~~  
 $f_1 \rightarrow$  is where gain starts to roll off.

$$f_1 = \text{upper} = \frac{1}{2\pi R_C}$$

$$R_C = -20 \text{ dB/dB}$$

phase plot:

$$\phi = \tan^{-1}(\frac{f}{f_1})$$


①  $f \ll f_1$

②  $f = f_1$

③  $f \gg f_1$

Phase angle

(for example)

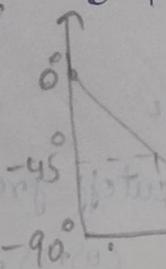

## PRACTICAL CHARA.

① high input impedance

② low output "

③ high CMRR

④ high open loop gain

⑤ high slew rate

⑥ Bandwidth is high

high gain  
high amplif.

open loop configuration

No feedback

appl.


→ comparator

→  $V_{in}$  &  $V_{reference}$

→ zero crossing detector.

Limitation  
when noise  
is present op  
voltage is  
effected,  $V_{ref}$

+ve. comparator

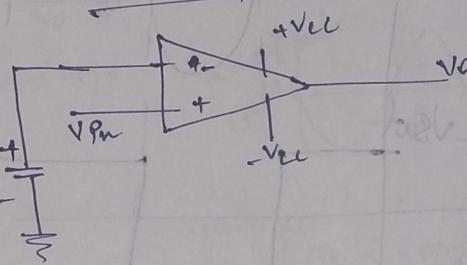

$$V_{in} > V_{ref} \Rightarrow V_o = +V_{sat}$$

$$V_{in} < V_{ref} \Rightarrow V_o = -V_{sat}$$


$$V_o = A_{OL} V_{in} \quad V_{in} = 2$$

$$V_o = A_{OL}^2 V_{in}$$


op. v is limited  
by power supp. b.

dead band:  $\pm$


+ve. comparator

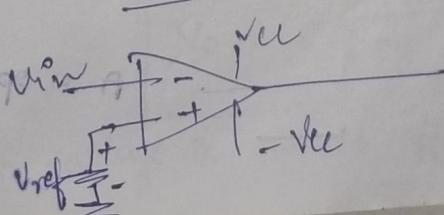


$$V_{in} > V_{ref}, V_o = +V_{sat}$$

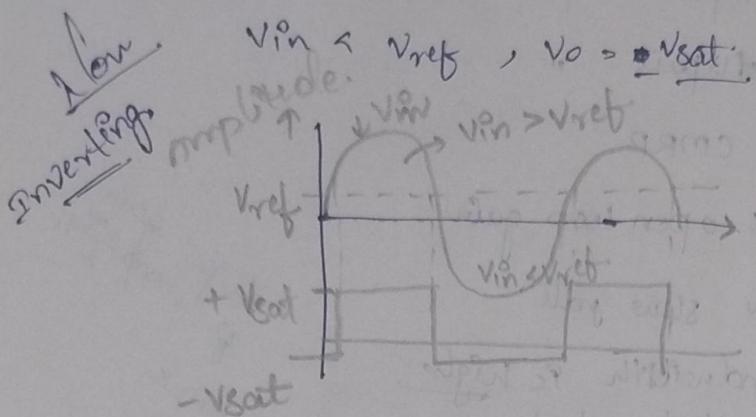

zero crossing detector.

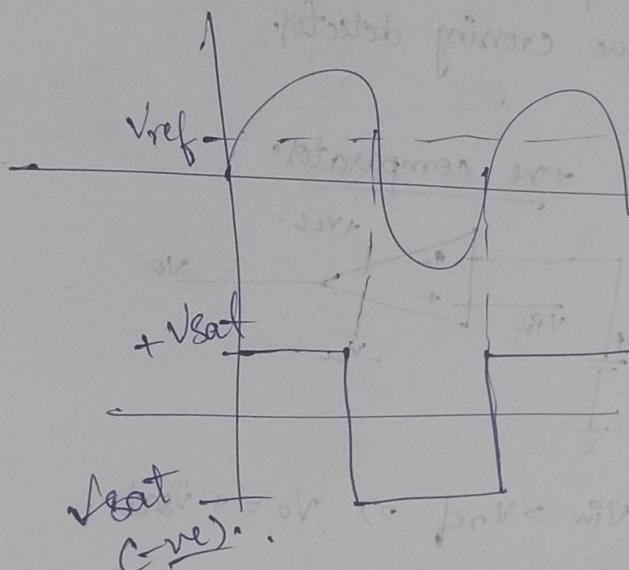

Inverting  
comparator

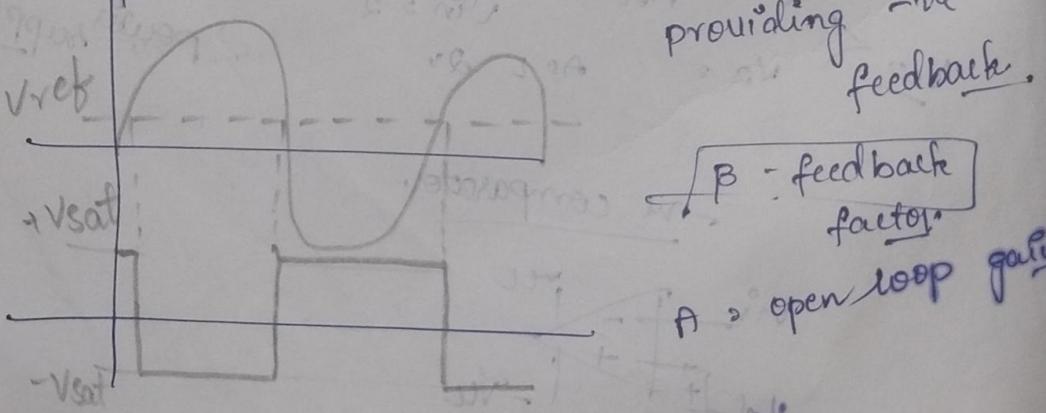

$$A_{CL} = \frac{A}{1+AB}$$

$$A_{CL} = \frac{A}{1-(-AB)}$$

$A_{CL} > A \rightarrow$  oscillations are produced.

Sol 19 part

- Buddhadev
- Hackathon
- ② Samyak fee
- ③ SIL
- ④ meeting



### Closed Loop Configuration:

$$A_{OL} = \alpha$$

$\Rightarrow A_{CL} \rightarrow \text{loses}$

$\rightarrow$  Amplifiers - negative feedback.

Inverting -

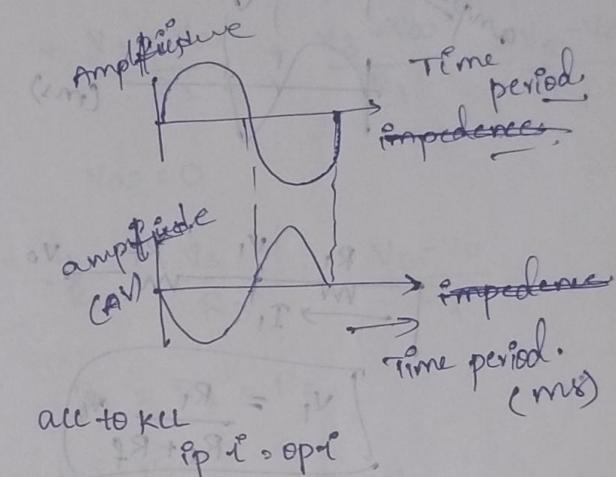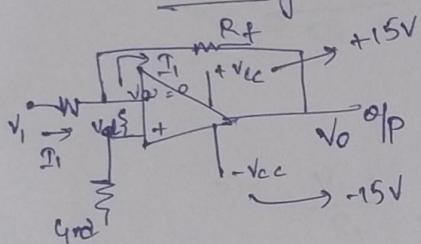

$$\text{all to KCL} \quad \text{ip} \leftarrow \text{op} \leftarrow$$

$$\frac{V_o - V_i}{R_1} \equiv \frac{V_o - V_o}{R_f}$$

$$V_o = 0 \text{ Volts.}$$

$$A_{CL} = \frac{-R_f}{R_1}$$

$$\frac{-V_i}{R_1} - \frac{V_o}{R_f} = 0$$

close loop gain.




$$\frac{-V_i}{R_1} = \frac{V_o}{R_f}$$

$$V_o = -\left(\frac{R_f}{R_1}\right) V_{in}$$

$\rightarrow$  op voltage is clipped off at  $+15V$  &  $-15V$ .

→ more than  $\pm 15$  V op. voltage clipped off.

Non Inverting.

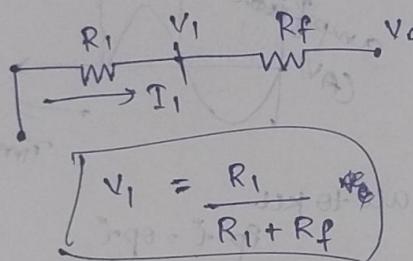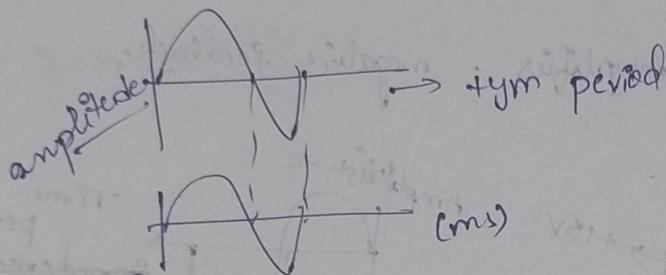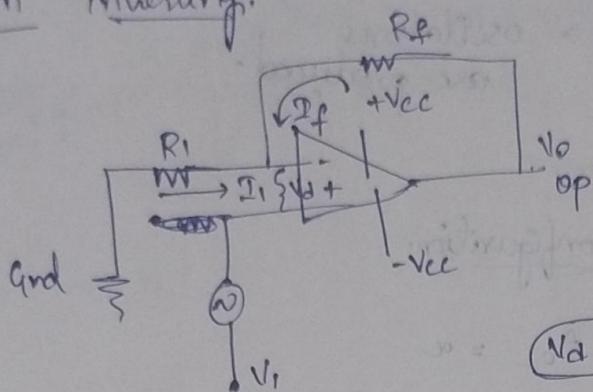


$$V_1 = \frac{R_1}{R_1 + R_f} V_o$$

$$V_o = \frac{R_1 + R_f}{R_1} V_1$$

$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_1$$

$$V_o = A_{cl} V_1$$

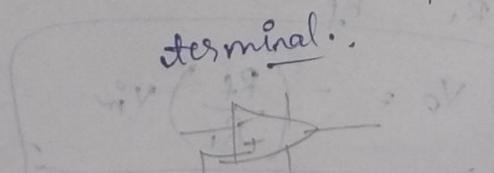To compensate offset voltage ( $R_{comp}$ ) Resistor compensator is ~~noted for~~ placed at non-inverting terminal.




non-inverting terminal to  $R_{comp}$  is not shown

OP-AMP as adder.

→ V<sub>output</sub> is sum of all V<sub>in</sub>.

• Inverting adder. → OP is 180° out of phase.

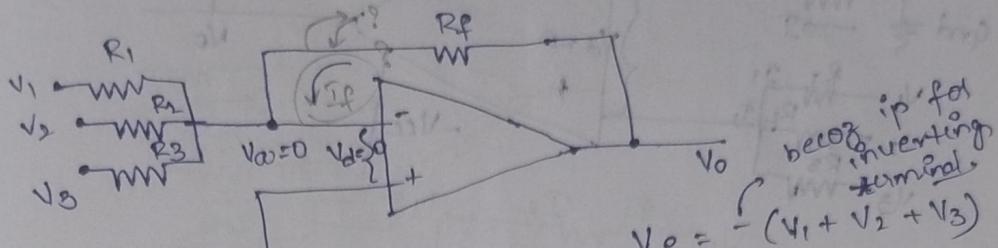∴ V<sub>1</sub>, V<sub>2</sub>, V<sub>3</sub> & R<sub>1</sub>, R<sub>2</sub>, R<sub>3</sub> are given.



By Ohm's law

$$I_1 + I_2 + I_3 = I_f$$

$$V = IR$$

$$\frac{V_1 - V_{AO}}{R_1} + \frac{V_2 - V_{AO}}{R_2} + \frac{V_3 - V_{AO}}{R_3} = \frac{V_{AO} - V_0}{R_f}$$

$$V_{AO} = 0$$

$$\Rightarrow \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = \frac{V_{AO} - V_0}{R_f}$$

$$R_1 = R_2 = R_3$$

$$\frac{V_1 + V_2 + V_3}{R} \Rightarrow \frac{V_{AO} - V_0}{R_f}$$

$$V_{AO} - V_0 = (V_1 + V_2 + V_3) \frac{R_f}{R}$$


$$\left( \frac{V_1 + V_2 + V_3}{R} \right) + V_0 = (V_1 + V_2 + V_3) - \frac{R_f}{R}$$

$$R_f = R$$

$$\Rightarrow V_0 = -(V_1 + V_2 + V_3)$$

$$R_f = 10R \Rightarrow V_0 = -10(V_1 + V_2 + V_3)$$

## Non-Inverting Adder.

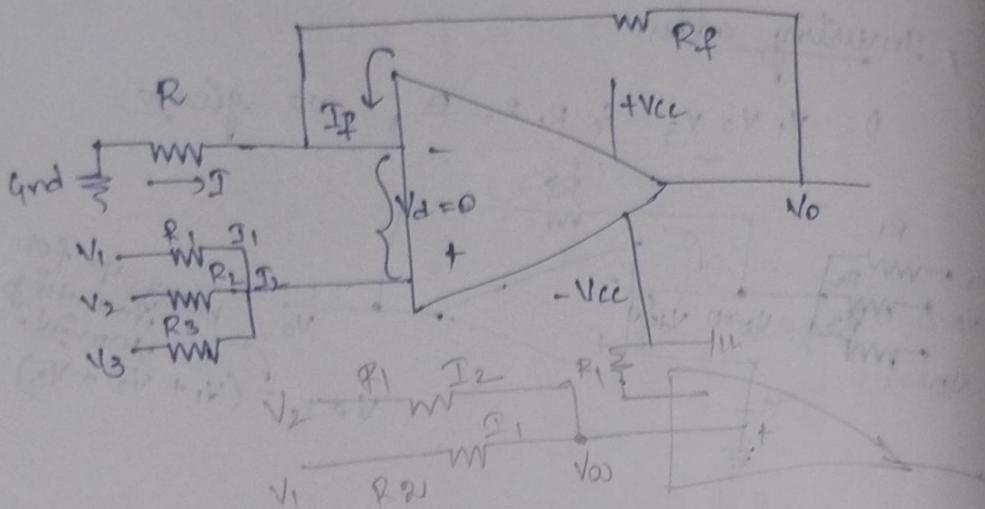

non-inverting terminal.

$$V_{d} = + (V_1 + V_2)$$

$$I_p = I_1 + I_2$$

$$\frac{V_{d0} - 0}{R_{sp}} + \frac{V_{d0} - V_0}{R_f} = 0$$

$$\frac{V_{d0}}{R} + \frac{V_{d0}}{R_f} = \frac{V_0}{R_f}$$

$$V_{d0} \left( \frac{1}{R} + \frac{1}{R_f} \right) = \frac{V_0}{R_f}$$

$$V_{d0} \left( \frac{R + R_f}{R R_f} \right) = \frac{V_0}{R_f}$$



$$(R + R_f) V_{d0} = \frac{V_0}{R_f} \left( \frac{R R_f}{R + R_f} \right)$$

$$V_{d0} = \left( \frac{R}{R + R_f} \right) V_0$$

$$V_0 = \frac{V_{d0} (R + R_f)}{R}$$



Op-amp as integrator  $\rightarrow$  low pass filter.

DC circuit  $\rightarrow$  capacitor

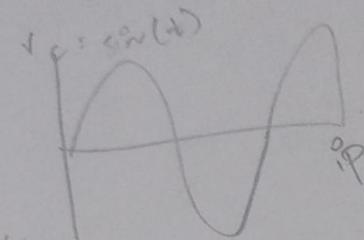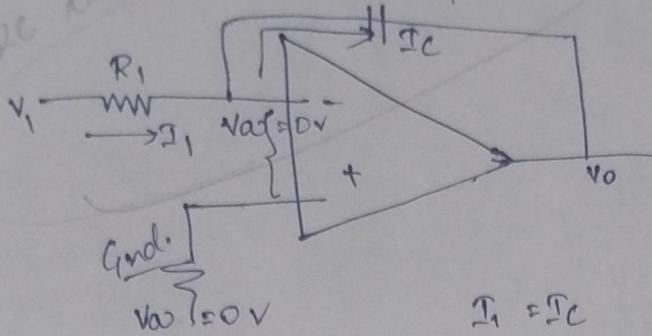

$$\frac{V_1 - V_0}{R_1} = \frac{CdV_C}{dt}$$
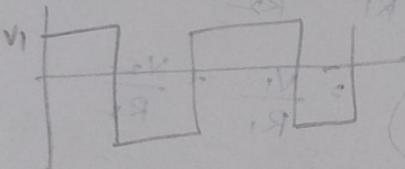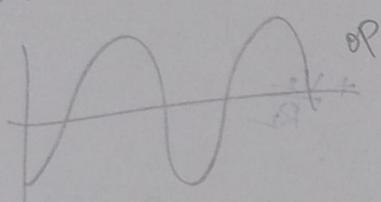
$$\frac{V_1 - V_0}{R_1} = \frac{Cd(V_0 + V_0)}{dt}$$



integrate



$$\int \frac{V_1}{R_1} dt = \int -C \frac{dV_0}{dt} dt$$

$$V_0 = -\frac{1}{R_1 C} \int V_1 dt$$


$$V_0 = -\frac{1}{R_1 C} \int_0^t V_1(t) dt + C$$

$R_1 = R$


$RC = \text{time const.}$

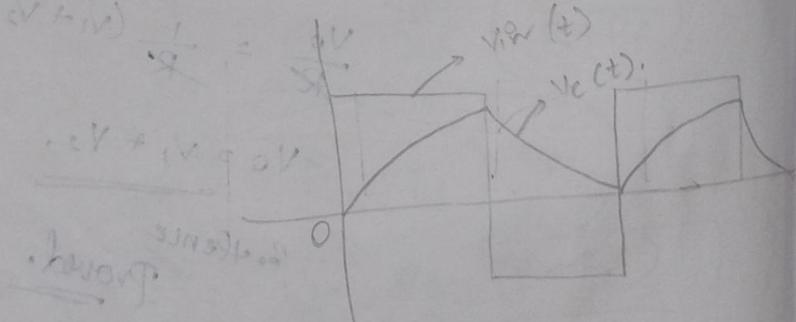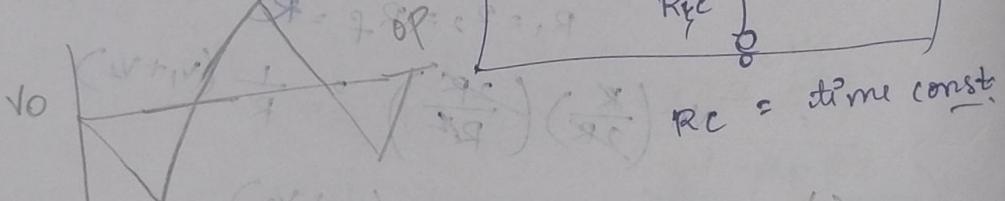

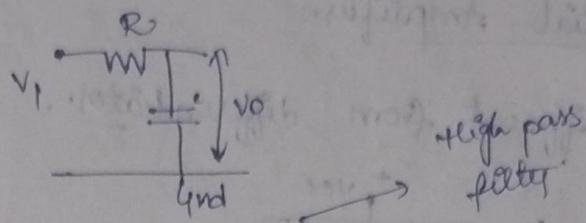when cap 1 end is ground then it's called low pass filter.



Op-Amp differentiator:

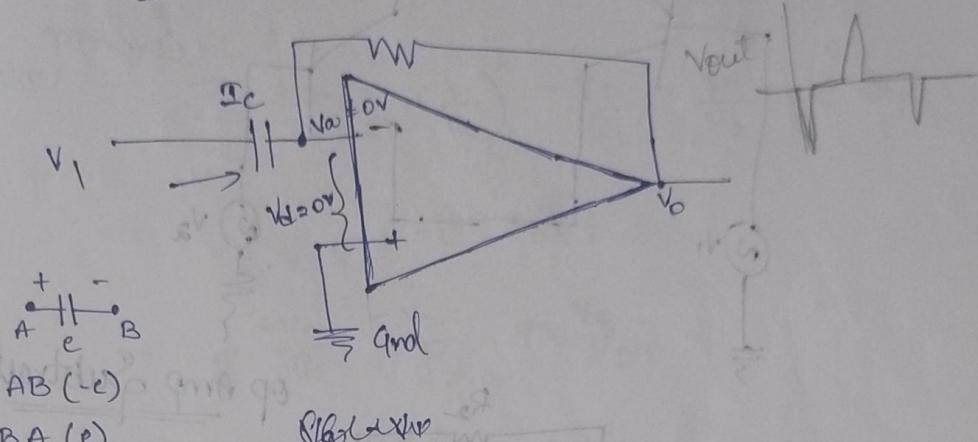

AB (-e)  
BA (e)

current in capacitor,

$$C \frac{dV_C}{dt} = \frac{V_{AO} - V_O}{R_f}$$

$$(V_C = V_{AO} - V_1)$$

$$\Rightarrow C \frac{d(V_{AO} - V_1)}{dt} = \frac{V_O}{R_f}$$

$V_{AO} = 0V$

$$C \frac{d}{dt} (-V_1) = \frac{V_O}{R_f}$$

$$-C \frac{dV_1}{dt} = \frac{V_O}{R_f}$$


$$V_O = -RC \frac{dV_1}{dt}$$

time const when  $R_f > R$

$$V_O = -R_f C \frac{dV_1}{dt}$$

differential Amplifier.


it's different from Differentiator.

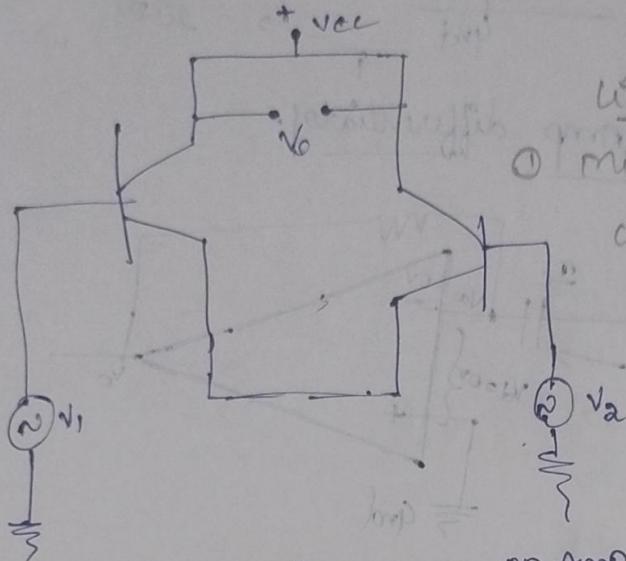

Limitation:

① might amplify common voltage.

Op Amp Subtractor.

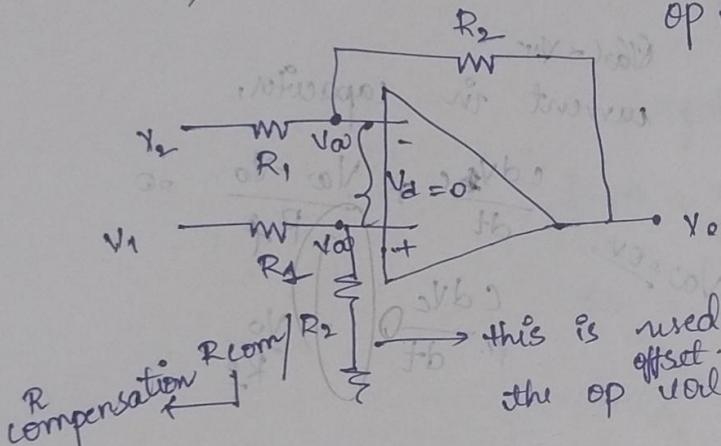

this is used to nullify  
the op voltage.

$$(V_1 - 0)V = 0$$

Using super position theorem

→ signal  $V_1$

→ ground  $V_2$

$$\frac{\partial V}{\partial V_1} = \frac{(V_1 - 0)}{R_1} + \frac{V_{AO} - V_0}{R_2} = 0 \quad \text{--- (1)}$$

$$\frac{\partial V}{\partial V_2} = \frac{V_{AO} - V_1}{R_1} + \frac{V_{AO} - V_0}{R_2} = 0 \quad \text{--- (2)}$$

Step under Brackets

from ① & ②

$$\frac{V_0}{R_1} - \frac{V_2}{R_1} + \frac{V_0}{R_2} - \frac{V_0}{R_2} = 0$$

$$V_0 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{V_2 - V_0}{R_1 R_2} = 0$$

$$\rightarrow V_0 \left( \frac{1}{R_1} + \cancel{\frac{1}{R_2}} \right) - \frac{V_1}{R_1} = 0 \quad \text{--- ④}$$

$$\rightarrow V_0 \left( \frac{1}{R_1} + \cancel{\frac{1}{R_2}} \right) - \frac{V_2}{R_1} = \frac{V_0}{R_2} \quad \text{--- ③}$$

$$-④ + ⑧$$

$$\frac{+V_1}{R_1} - \frac{V_2}{R_1} = \frac{V_0}{R_2}$$

$$\frac{V_1 - V_2}{R_1} = \frac{V_0}{R_2}$$

$$V_0 = \frac{(V_1 - V_2) R_2}{R_1}$$

Suppose  
 $R_2 = 100 R_1$

$$V_0 = \frac{100 R_1 (V_1 - V_2)}{R_1} \star$$

$V_0 = 100$  times of  
diff in ip voltages.

modes

Common mode ( $V_1 = V_2$ )

difference mode

the ability of common ~~reject~~ mode transistors  
to reject the differential signal & giving  
amplified signal is called common mode  
rejection.

$$V_0 = V_1 A_1 + V_2 A_2$$

$$V_{cm} = \frac{V_1 + V_2}{2}$$

common mode voltage

$$V_d = V_1 - V_2$$

difference mode

$$V_1 = V_{cm} + \frac{1}{2} V_d$$

$$V_2 = V_{cm} - \frac{1}{2} V_d$$

$$A_{dm} = \frac{1}{2} (A_1 - A_2)$$

$$A_{cm} = A_1 + A_2$$

$$\Rightarrow V_o = V_{dm} A_{dm} + V_{cm} A_{cm}$$

$$\rightarrow V_o = V_d A_d + V_c A_c$$

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right|$$

we use buffer circuit.

$$in dB \quad CMRR = 20 \log \frac{A_{dm}}{A_{cm}}$$

Voltage follower — acts as buffer circuit.

$$V_o = V_{in}$$


$$\Rightarrow A_{cl} = V_o / V_{in}$$

$$A_{cl} = 1$$

Non inverting

$$V_o = \left( 1 + \frac{R_f}{R_i} \right) V_{in}$$

Acl (gain)

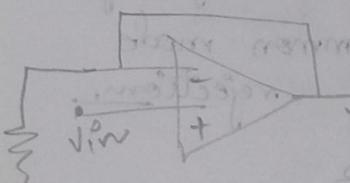

$$when \quad R_f = 0 \quad R_i = \infty$$


$$V_o = V_{in}$$

$$V_o = V_{in}$$

Differential amplifier  
buffering  
Instrumental amplifier  
high ip  
impedance

Differential amplifier + Buffer circuit  
voltage followers at 2 inputs = Instrumental amplifier.  
to ↑ gain

Instrumental amplifier.

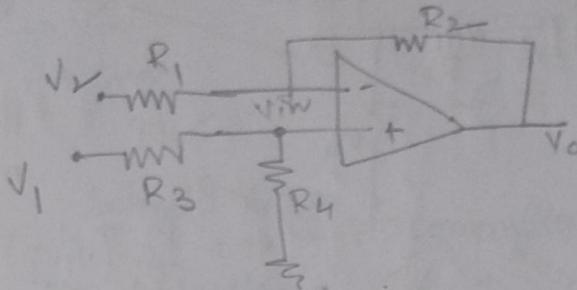

$$V_{in} = \frac{R_3}{R_3 + R_4} V_1 - \frac{R_2}{R_1 + R_2} V_2$$

$$\text{① } \frac{V_{in}}{V_{in} - \Delta V} = \rho_1 \quad V_{in} = \frac{R_3}{R_3 + R_4} V_1 - \frac{R_2}{R_1 + R_2} V_2$$

No i same  
same diff

$$(1 + \rho_1) \rho_1 = \Delta V - \Delta V$$

$$\text{② } V_0 = \left( 1 + \frac{R_2}{R_1} \right) \frac{R_4}{R_4 + R_3} V_1 - \frac{R_2}{R_1} V_2$$

$$\text{③ } (1 + \rho_1) \rho_1 = \Delta V - \Delta V$$

$$\Rightarrow V_0 = \frac{R_4}{R_3} \cdot \frac{1 + \frac{R_2}{R_1}}{1 + \frac{R_4}{R_3}} V_1 - \frac{R_2}{R_1} V_2$$

$$(1 + \rho_1) \frac{\Delta V - \Delta V}{\Delta V}$$

$$\text{when } \frac{R_4}{R_3} = \frac{R_2}{R_1}$$

$$\left( \frac{R_2}{R_1} + 1 \right) \frac{\Delta V - \Delta V}{\Delta V}$$


$$\boxed{V_0 = \frac{R_2}{R_1} (V_A - V_B)}$$

$$\Rightarrow V_0 = \frac{R_2}{R_1} (V_A - V_B)$$

$$\left( \frac{R_2}{R_1} + 1 \right) \frac{\Delta V - \Delta V}{\Delta V} = 0$$

with transmission  
no load

# Instrumental Amplifier

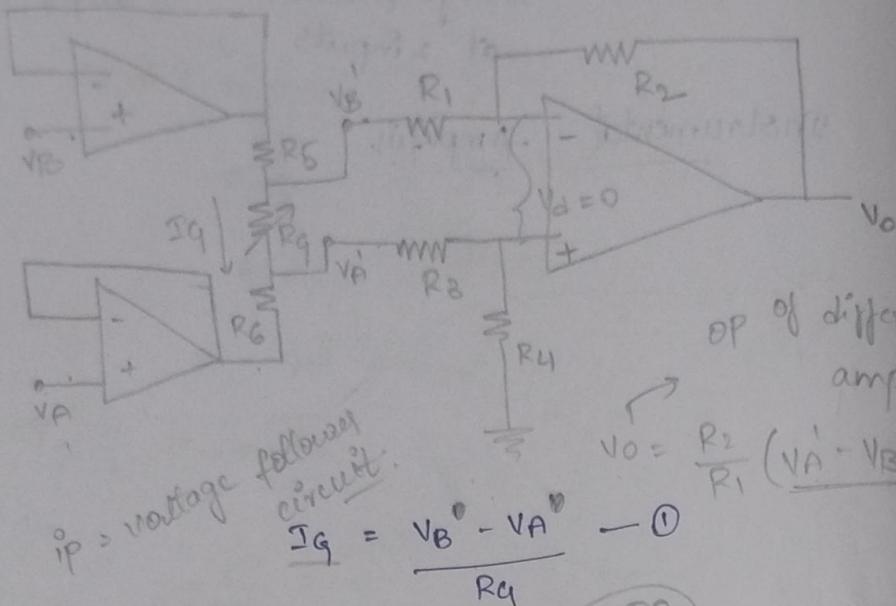

$$\frac{V_B - V_A}{R_g} = \frac{V_B - V_A}{R_5 + R_g + R_6} \quad \text{--- ③}$$

$$V_B - V_A = i_g (2R_5 + R_g) \quad \text{--- ④}$$

$$V_B - V_A = \frac{V_B - V_A}{R_g} (2R_5 + R_g) \quad \text{--- ⑤}$$

$$V_B - V_A = \frac{V_B - V_A}{R_g} (2R_5 + R_g)$$

$$\frac{V_B - V_A}{R_g} = \frac{V_B - V_A}{R_1 + 2R_5} \quad \text{(using ③)}$$

$$V_B - V_A = V_B - V_A \left( 1 + \frac{2R_5}{R_g} \right)$$

$$\Rightarrow V_A - V_B = V_A - V_B \left( 1 + \frac{2R_5}{R_g} \right)$$

OP of  
Instrumentation  
amplifier.

$$V_o = \frac{R_2}{R_1} \left( V_A - V_B \left( 1 + \frac{2R_5}{R_g} \right) \right)$$


OP of instrumentation amplifier.

# Schmitt Trigger.

- 1) positive feedback. 2) Regenerative circuit  
signals  
comparators.
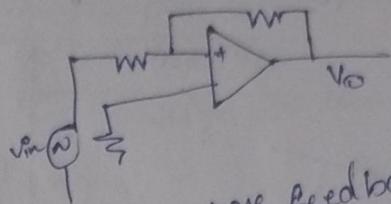
## Inverting

-  $\rightarrow V_{in}$   
+  $\rightarrow$  Gnd.



(LVI)  
Schmitt trigger  
↓  
Vupper threshold  
↓ lower "

comparators  $\rightarrow$  has noise effect on op +  
hysteresis  $\rightarrow$  to nullify this noise effect on output

responds to  $V_{sat}$  &  $-V_{sat}$ .



$$V_{UT} = \begin{matrix} \text{low to} \\ \text{high to} \end{matrix} V_{IP}$$

~~Point-to-point~~ high to  $V_{IP}$

$$V_{LT} = \begin{matrix} \text{high to} \\ \text{low to} \end{matrix} V_{IP}$$

$$\text{hysteresis } V_H = V_{UT} - V_{LT}$$


## Schmitt trigger.

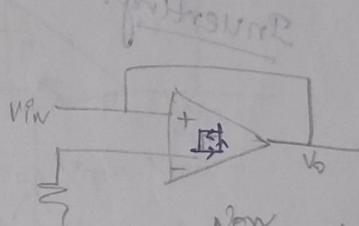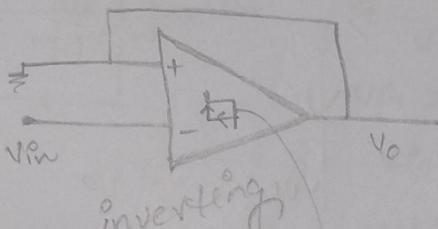

inverting  
 $V_{IP} < V_{LT}$  hysteresis


when  $V_o = 0V$

$V_{IP} > V_{LT}$   
when  $V_o = 0V$

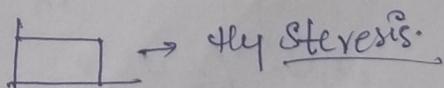

Transfer characteristics of hysteresis curve.

Now Inverting

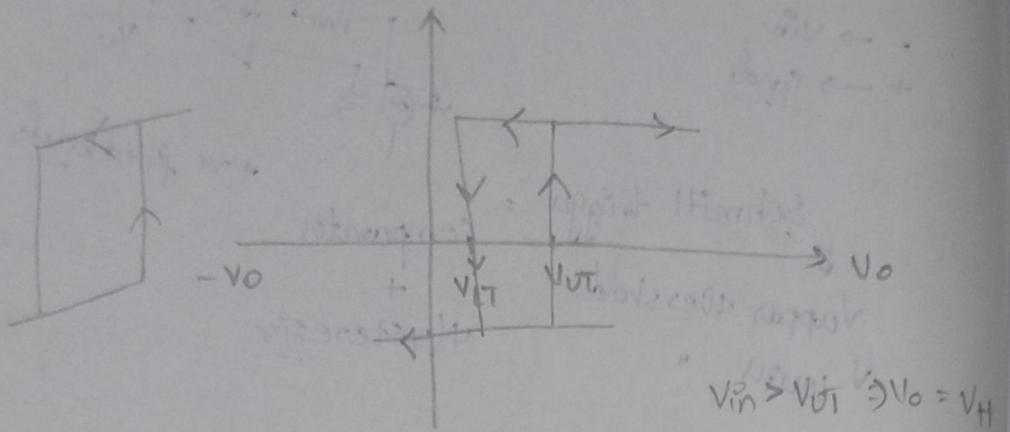


$$V_{UT} = V_H$$


$$V_{LT} = V_L$$

$$V_{in} > V_{UT} \Rightarrow V_o = V_H$$
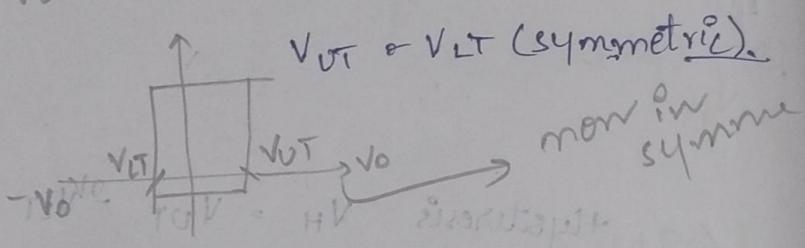
$$V_{in} < V_{LT} \Rightarrow V_o = V_L$$



Inverting

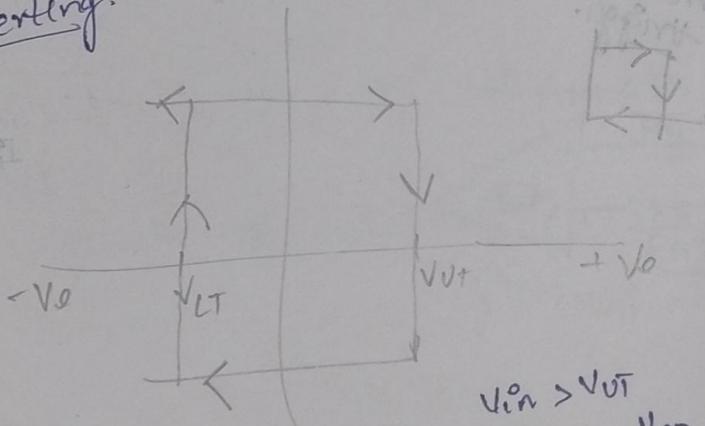


$$V_{in} > V_{UT}$$

$$V_{op} > V_{low}$$

$$V_{in} < V_{UT}$$

$$V_{op} > V_{high}$$


# Schmitt Trigger.

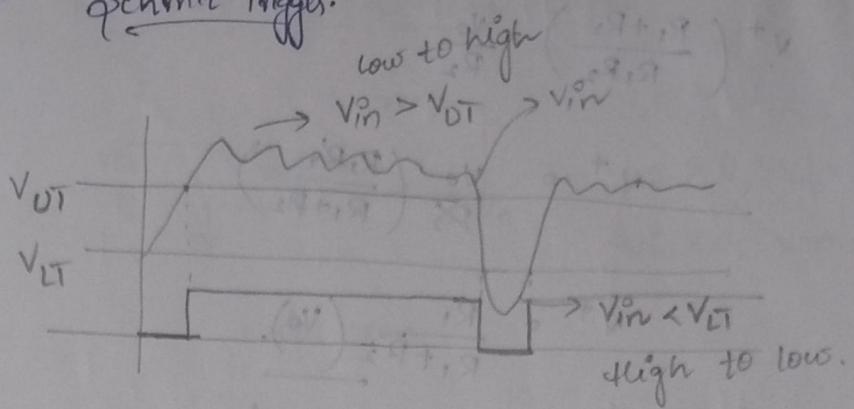

→ Inverting

→ Non inverting


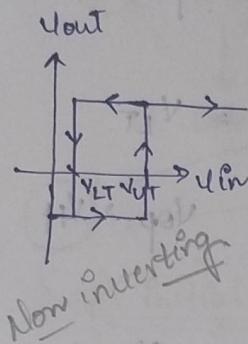
Hysteresis curve is the transfer charac curve drawn b/w  $V_{in}$  &  $V_{out}$ .



Non inverting

$V_{in}$  remains low until  $V_{in} > V_{UT}$   
once it reaches  $V_{UT}$   $V_{in}$  increases &  
remains const but there is a change  
in  $V_{in}$ .

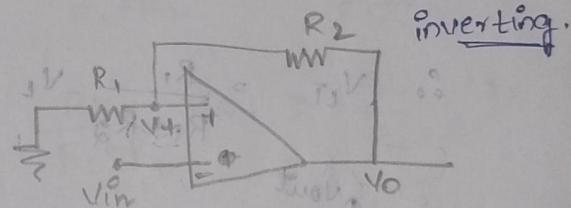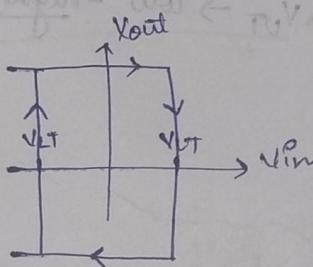Once when it reaches  $V_{in}$  is less  
than  $V_{LT}$  it decreases.



$V_{in} > V^+ \Rightarrow V_{op} = V_{low}$

$V_{in} < V^+ \Rightarrow V_{op} = V_{high}$

Nodal analysis

$$\frac{V^+ - 0}{R_1} + \frac{V^+ - V_o}{R_2} = 0$$

$$\frac{V^+}{R_1} + \frac{V^+ - V_o}{R_2} = V_o / R_2$$

$$V^+ \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = V_o / R_2$$

$$V^+ \left( \frac{R_1 + R_2}{R_1 R_2} \right) = \frac{V_o}{R_2}$$

$$N^+ = \frac{V_o}{R_2} \left( \frac{R_1 R_2}{R_1 + R_2} \right)$$

$$V^+ = \frac{R_1}{R_1 + R_2} (V_o).$$

$V_o$  possible are  $V_L$  |  $V_H$

$$\Rightarrow V_1 = \frac{R_1}{R_1 + R_2} N_H = V_{LT}$$

$V_{in} > V_1$ ,  $V_{op} \approx V_L$



$$\Rightarrow V_2 = \frac{R_1}{R_1 + R_2} V_L \Rightarrow V_{LT}$$

$V_{in} > V_2$ ,  $V_{op} \approx V_H$


$$\therefore V_{LT} = \frac{R_1}{R_1 + R_2} N_H \rightarrow V_{LT} \rightarrow \text{high-low}$$

$\rightarrow V_{LT} \rightarrow \text{low-high}$
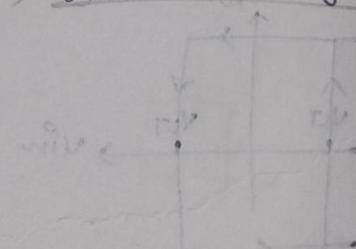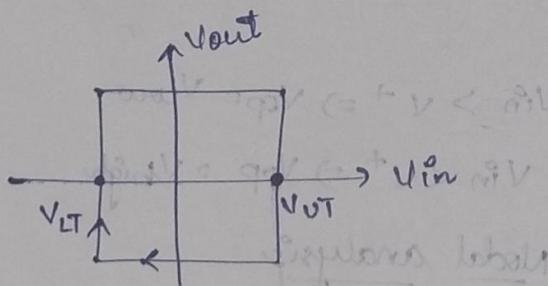
$$\therefore V_{LT} = \frac{R_1}{R_1 + R_2} V_L$$



## Non inverting switch triggered.

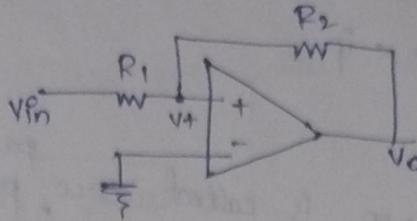

$$V_{in} > 0, V_{op} = V_{High}$$

$$V_{in} < 0, V_{op} = V_{Low}$$

Nodal eqn

$$\frac{V_+ - V_{in}}{R_1} + \frac{V^+ - V_o}{R_2} = 0$$

initial op low

↓ high

↓ low

$$UT V^+ \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_{in}}{R_1} + \frac{V_o}{R_2}$$

$$V^+ \left( \frac{R_1 + R_2}{R_1 R_2} \right) = \frac{V_{in}}{R_1} + \frac{V_o}{R_2}$$

$$V^+ = \frac{V_{in} R_2 + R_1 V_o}{R_1 + R_2} \quad V_o$$

\* initial op to be low  $\rightarrow V_{in} > 0, V_{op} = V_H$

initial op = L

V\_L

$$V_{in} + \frac{R_1}{R_1 + R_2} V_L = \frac{R_2}{R_1 + R_2} V_o$$

low

$$\frac{R_2}{R_1 + R_2} V_{in} > -\frac{R_1}{R_1 + R_2} V_L$$

$$V_{in} > -\frac{R_1}{R_2} V_L \rightarrow V_o = V_H$$

$$V_{LT} = -\frac{R_1}{R_2} V_L$$

high  $\rightarrow V_{in} < 0$


$$\frac{R_2}{R_1 + R_2} V_{in} < -\frac{R_1}{R_1 + R_2} V_H$$

$$\therefore V_{LT} = -\frac{R_1}{R_2} V_H \cdot \frac{R_1}{R_1 + R_2} V_L$$


$$V_{in} < -\frac{R_1}{R_1 + R_2} V_H \rightarrow V_{LT}$$

# FILTERS.

attenuation  $\rightarrow$  op < ip

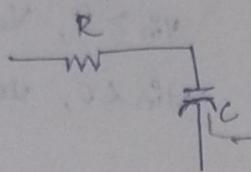

op is called low pass passive

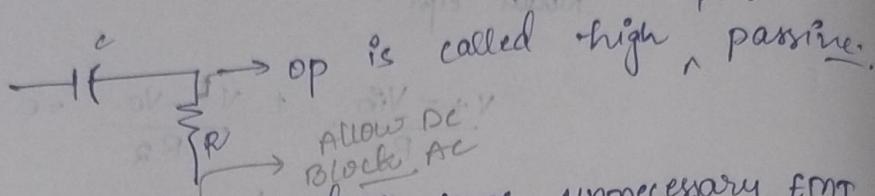


using inductors produces some unnecessary EMI  
cap connected as feedback allows DC  
blocks AC  
so inductors are not used.

short time const.  $\int \frac{dt}{10}$

ip impedance is high  
of non inverting than inverting


Between 1,2 pins there is an Resistor with  $1,2 M\Omega$   
so called Input impedance.

Inverting

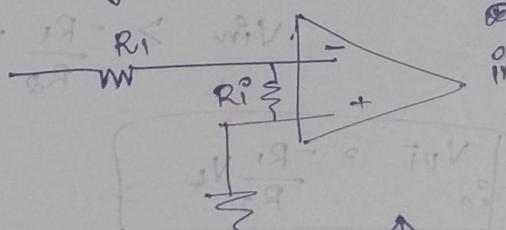

$$ip \text{ impedance} = R_1 \parallel R_2$$

Non - inverting  $\rightarrow$

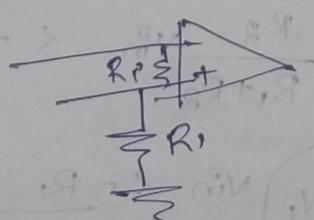

ip impedance  $\rightarrow R_1 + R_2$

$$\approx R_1 + R_2$$

Bandwidth of NI is high than Inverting.

that's filters are with Non inverting only.



### Active filter

- ① Dual power supply
- ② costly for higher frequencies designs

### Passive filter

- ① No power supply
- ② less cost.

first order low pass

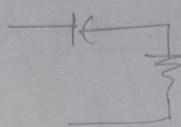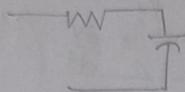

first order high pass

series

cascaded  
OP of 1 is given to another one  
as IP.

Band pass.

ideal.  
~~if pass w<sub>o</sub> stop~~  
low pass allows only less frequencies.

Order of pass (from low) 20 (low)


20 (l)

20 (l) = 64.0

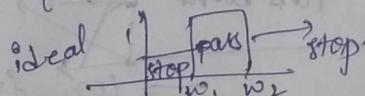60.

high pass → allow high

Band pass → only certain frequencies are allowed.



band stop — stops that particular range of frequencies.

### TYPES OF FILTERS

① Butterworth

Capacitor  $\rightarrow$  Allow AC  
Blocks DC


② Chebyshov.

③ Cauer.

### Butterworth

$$R = \frac{1}{\sqrt{2}}$$

$$W = \frac{C}{L} \frac{dV}{dt}$$

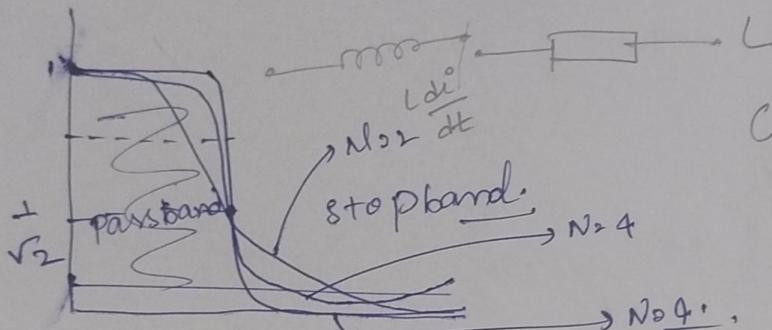

$$j\omega L = jX_L = \frac{1}{\sqrt{L/C}}$$

Active filters



mostly we use op amp

for  $\uparrow$  voltage gain.

$$\sqrt{C} = \frac{1}{\sqrt{\omega^2 C_0}}$$



### Frequency Response

low pass filter

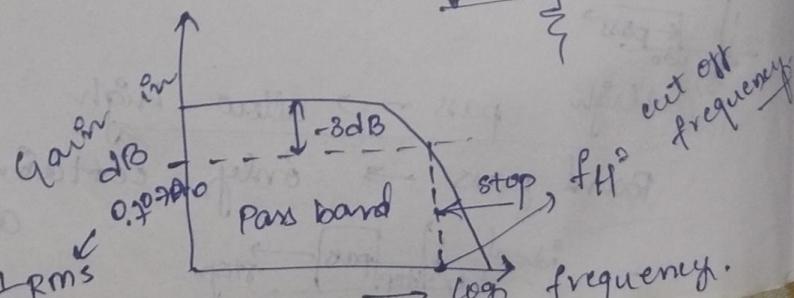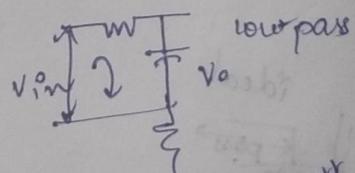

$\omega < f_L \rightarrow$  pass band  
 $> f_L \rightarrow$  stop | attenuate.


+ high pass frequency.

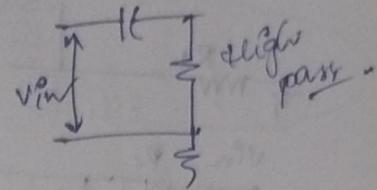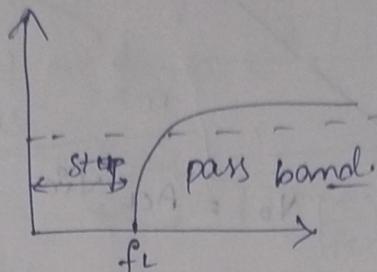

$$f_C = f_H = f_C$$

Band pass filter


low + high pass

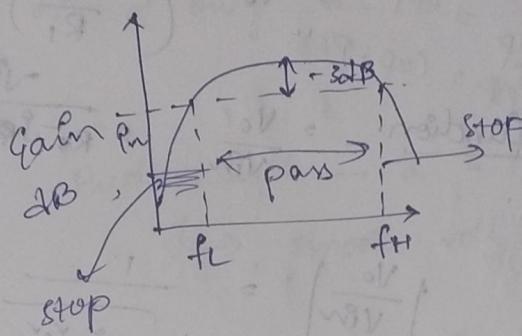

$$f_H - f_L = \text{pass band}$$

Band stop | Reject

low || high

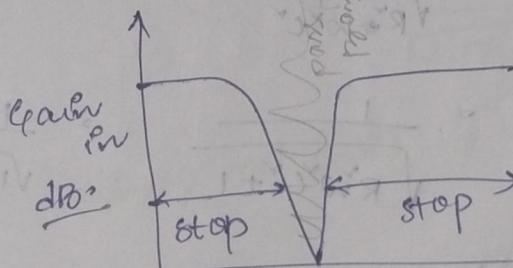


voltage follower  $\Rightarrow V_{\text{output}} = V_{\text{in}}$

$$V_{\text{Gain}} = 1$$

Active low pass filter

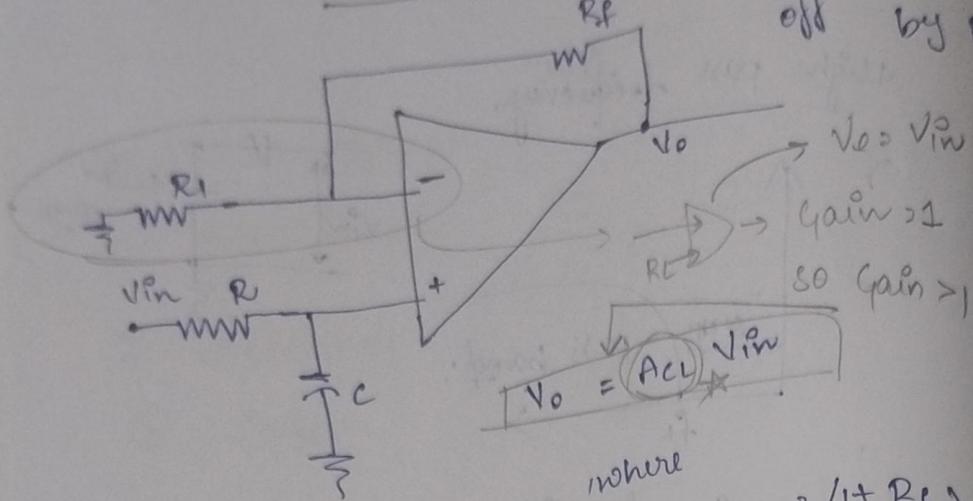frequency Selecting  
circuit bcoz off is selected  
by  $R_f$



$$V_o = V_{in}$$

$$\text{Gain} > 1$$

$$\text{so Gain} > 1$$

$$V_o = (A_{cl}) V_{in}$$

where

$$A_{cl} = \left( 1 + \frac{R_f}{R_1} \right)$$

low pass op at cap  
 $V_{outP} > \text{Cap} \Rightarrow V_o = \left( 1 + \frac{R_f}{R_1} \right) V_{in}$   
 $V_{inP} > \text{Cap/Bias}$

$$\text{Transfer function} = \frac{V_o}{V_{in}} = \frac{1}{R_o - j\omega X_C}$$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{1}{\sqrt{R_o^2 C^2 + 1}}$$

$$\left| \frac{V_o}{V_{in}} \right|$$

$$\frac{1}{\sqrt{R_o^2 C^2 + 1}}$$

$$X_C = \frac{1}{\omega C}$$

$$\frac{1}{\sqrt{R_o^2 C^2 + 1}}$$

$$\frac{1}{\sqrt{1 + (\frac{\omega}{\omega_c})^2}}$$

$$\frac{1}{RC} = \frac{1}{\omega C}$$

$$\left| \frac{V_o}{V_{in}} \right|$$

$$\frac{1}{\sqrt{1 + \left( \frac{\omega}{\omega_c} \right)^2}}$$

$$\frac{1}{\sqrt{1 + \left( \frac{\omega}{\omega_c} \right)^2}}$$


$$\rightarrow f_c = \frac{1}{2\pi R_C}.$$

$$\rightarrow V_o = \frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}} A_{cl}$$

$$V_o = \frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}} \left( 1 + \frac{R_f}{R_i} \right).$$

$\alpha \rightarrow$  Rate at which gain is rolled off.  
 $\hookrightarrow$  Damping ratio.

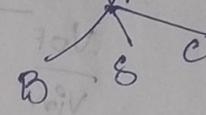Based on  $\alpha$  only we choose effective filter



Butterworth  $\rightarrow \alpha \approx 1.414$ .

$\hookrightarrow$  smooth roll over.

Gibson  $\rightarrow \alpha \approx 2.158$ .

2nd order  $\rightarrow 2 R_C$  networks.

$$f_c = \frac{1}{2\pi R_1 C_1 R_2}$$

$\downarrow$   
 Gain is not stable  $\rightarrow$  bcg of  
 Impedance mismatch.

That's why sallen key we use  
 $\downarrow$   
 1st  $R_C$  is given as feedback

CO-4.

21/10/24

- Oscillators - op-amp.

- Multivibrators - IC 555 times.

Negative feedback - op-amp, <sup>not</sup> shld. be inphase with ip.

### Op amp.


- good stability
- poor gain.

Oscillator = amplifier + positive feedback.

① Generator sinewave or non-sinusoidal wave

is called harmonic oscillators Relaxation oscillators.

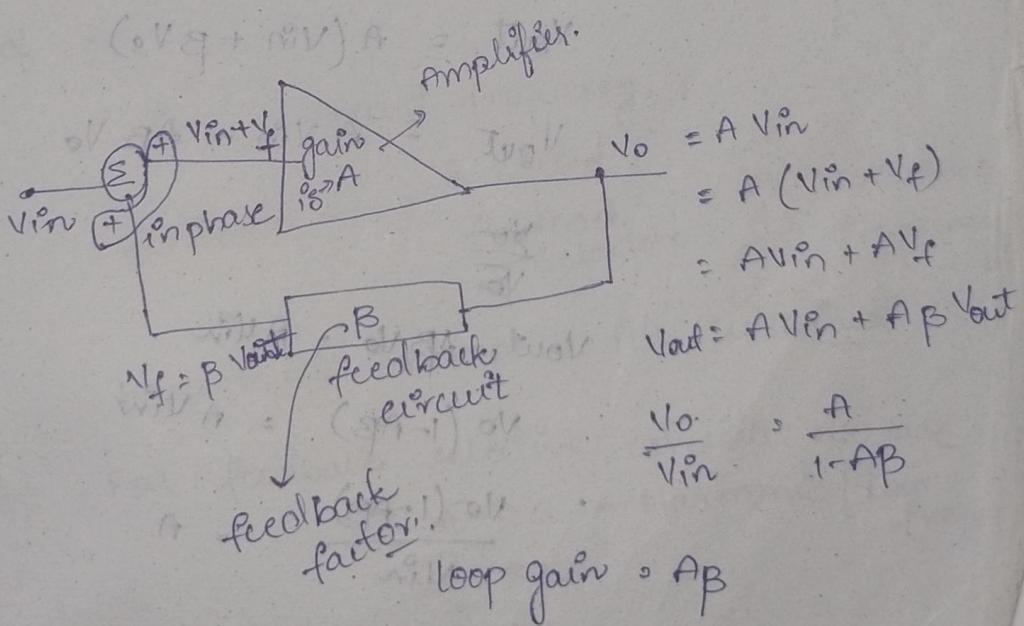which uses or produces time contains an oscillator.



conditions to be an oscillator.

$$|AB| = 1$$

phase  $\angle AB = 0^\circ \text{ or } 360^\circ$

$\hookrightarrow$  Barkhausen criteria.

what if  $|AB| < 1$

assume  $B = 0.9$ ,  $V_{in} = 2$

$$V_o = 2 \times 0.9$$

$\Rightarrow 1.8 \rightarrow$  the thing which  
is ip for next round.

$$V_o = 1.8 \times 0.9$$

which means each time the ~~reducer~~,  
which doesn't produce sin waves.

what if  $|AB| > 1$

$$V_{out} = A(V_{in} + BV_o)$$

$$V_{out} = A V_{in} + AB V_o$$

$$\frac{V_o}{V_o}$$

$$V_{out} - AB V_o = A V_{in}$$

$$V_o(1 - AB) = A V_{in}$$

$$\frac{V_o(1 - AB)}{A V_{in}} = 1$$

$$\frac{V_0}{V_{PN}} \rightarrow \frac{A}{1 - AB}$$

1907-1928.2

2-4

2.4 x 2

4.8

Firstly to produce oscillations  $AB > 1$  then to get sustain ~~at~~ oscillation we  $AB = 1$ .

Oscillator pp is DC signal:

op is ac signal.

(p) Feedback circuit is called thermal noise.

so, this means an oscillator doesn't require any

spec AC.

$f_r$  = resonant frequency.

feedback → is called  
feedback selective or resonance frequency

because at one point it's sustained;

For feedback selective circuits we use  
 $\text{O}_\text{RC}$  - harmonic low freq

② RLC

③ LC

$RC \rightarrow$  used in audio freq range  
 $LC \rightarrow$  low frequency or  $(KHz)$

Harmonic

- sin waves.

RLC - IC 555 timer

- Relaxation oscillators

High frequency,  $(MHz)$ .

Radio frequency range

$RC$  phase shift

Wein bridge

Hartley

Colpitts

Relaxation

Bistable (self learning).  
monostable


Astable

28/10/24
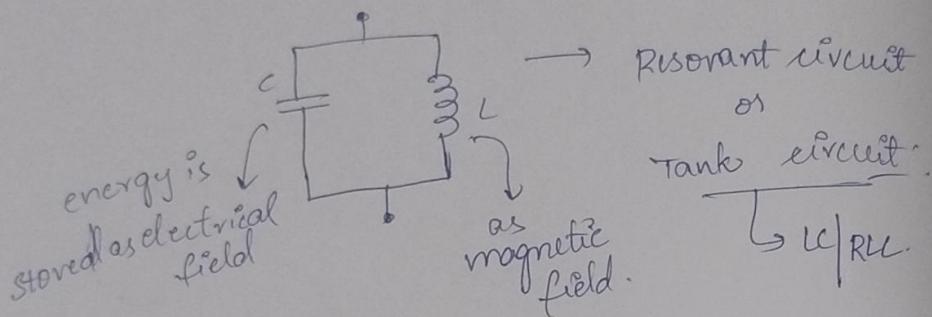
## High Frequency Oscillators

↳ LC oscillators.

RC can't be used in high frequency range bcz  
R,C decreases when freq increases.  
LC oscillators are called as transcavoids.



Positive feedback - op inphase  
with ip

Negative feedback - op out of  
phase.


At high frequencies there is a gain roll off so  
as an amplifier we don't use op-amp we use  
transistors instead.

Impedance of an inductor  
 $Z = j\omega L$


$V = L \frac{di}{dt}$

Instantaneous voltage → Inductance


Instantaneous voltage

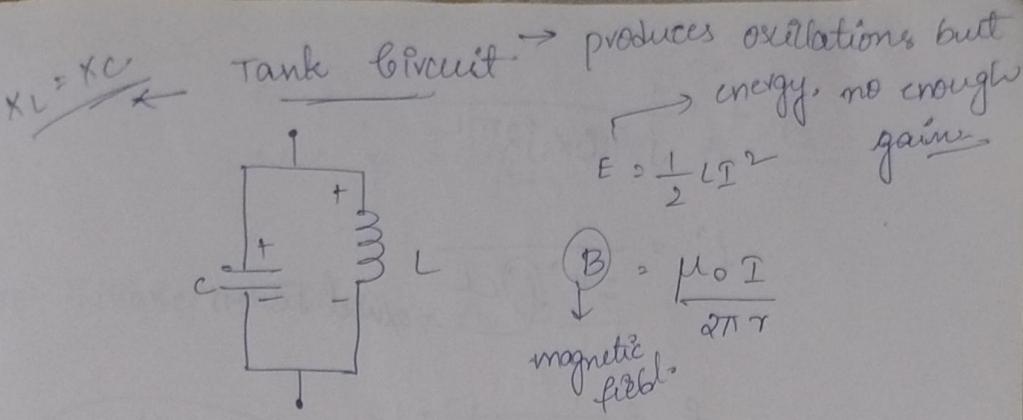

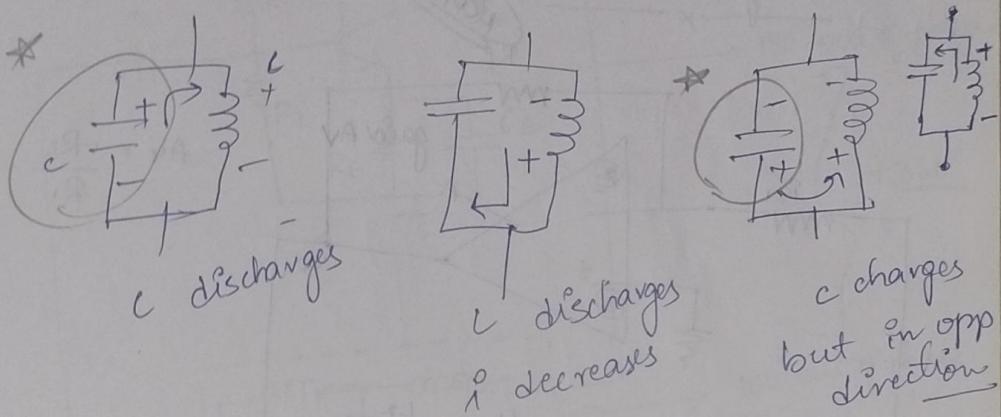when  $C$  is fully charged it starts to discharge.  $\rightarrow i$  increases.  
 $L$  starts discharge means  $i$  ~~increases~~ decreases



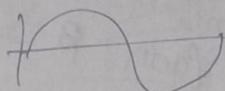capacitors charges in one direction & discharges in another direction.



These produce oscillations which are not sustained so we use oscillator with positive feedback.

$\overbrace{X_L = X_C} \rightarrow$

frequency at which oscillations are setup.

$$j\omega L = j\omega C$$

$$\frac{1}{j2\pi f L} = \frac{1}{j2\pi f C}$$


$$f = \frac{1}{2\pi L C}$$

$$f = \frac{1}{2\pi \sqrt{LC}} \rightarrow \text{actual frequency}$$

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$

$$X_C = \frac{1}{2\pi f_r}$$

Hartley Oscillator. Harmonic Opamp.

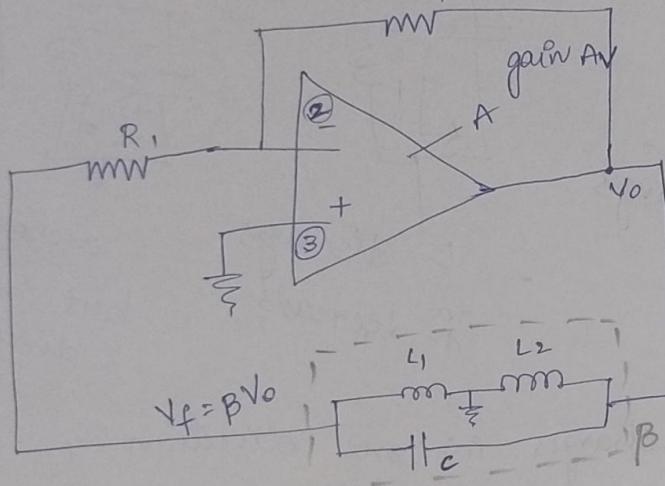

$$A_v = \frac{-R_f}{R_1}$$

$$\text{attenuation} / \text{feedback factor} \quad B = \frac{V_f}{V_o} = \frac{L_1}{L_2}$$

frequency of oscillation  
(or)  
frequency of resonance

$$f_r = \frac{1}{2\pi \sqrt{L_{\text{eq}} C}}$$

$$L_{\text{effective}} = L_1 + L_2 + 2M$$

mutual inductance

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$

NKT


$$AB \approx 1$$

when  $\beta > L_1/L_2$  then  $A > \frac{L_2}{L_1}$ .



To initiate oscillation,  $A_V > \frac{L_2}{L_1}$

$$\Rightarrow \frac{-R_F}{R_1} > \frac{L_2}{L_1}$$

in practical CE

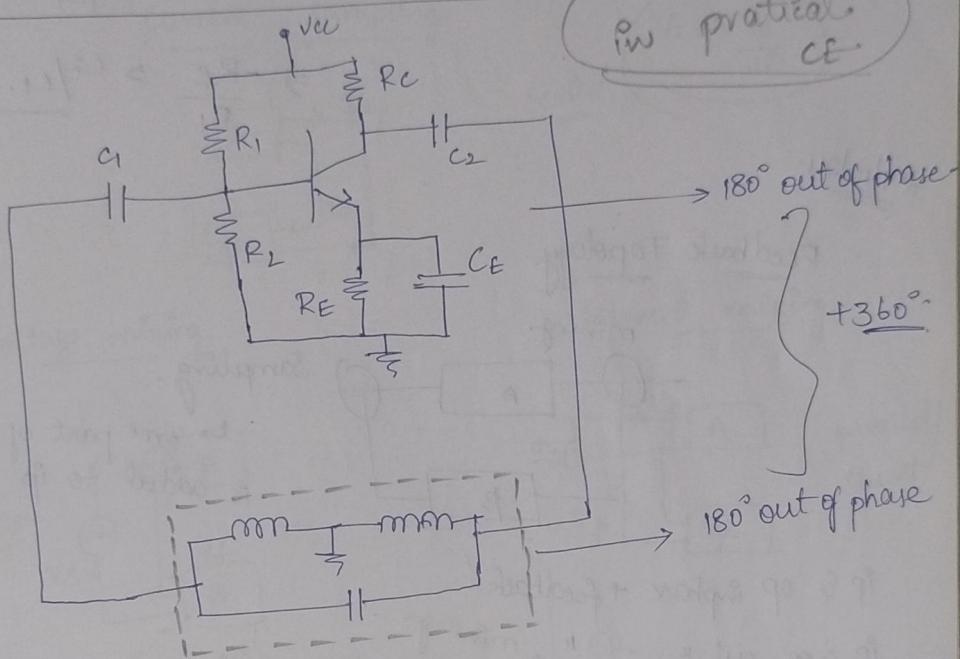

Colpitts Oscillator

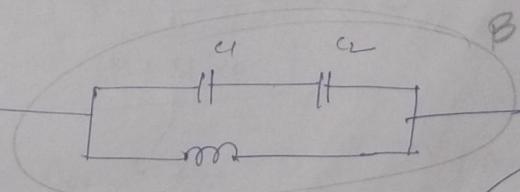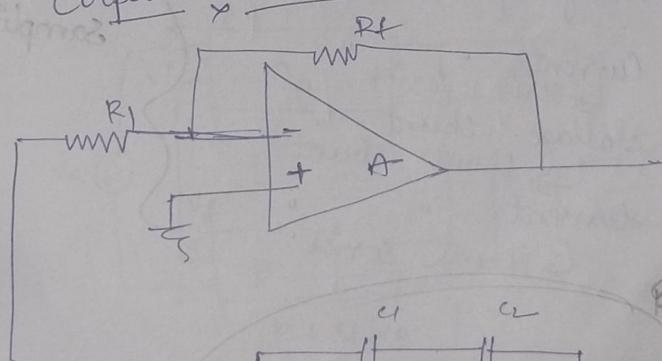

resonant freq

$$f_R = \frac{1}{2\pi\sqrt{LC}}$$

$$\Rightarrow f_R^2 = \frac{1}{2\pi^2 L_{eff} C_{eff}}$$

$$\text{Coff} \rightarrow \frac{C_1 + C_2}{C_1 C_2}$$

$$B \rightarrow \frac{C_1}{C_2}$$

$$A \cdot B = 1$$

$$\Rightarrow A \cdot V = \frac{C_2}{C_1}$$


to initiate oscillation

$$A \cdot V > C_2 / C_1$$

$$\Rightarrow -\frac{R_f}{R_1} > \underline{C_2 / C_1}$$

29/10/24

### Feedback Topology

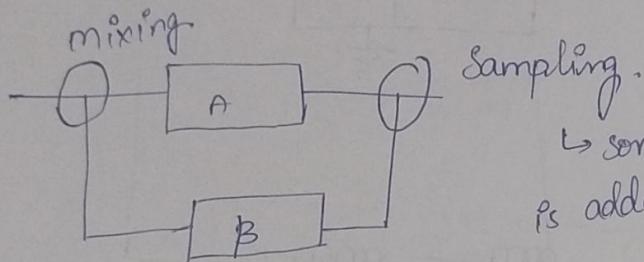

Sampling.

↳ some part of op  
is added to ip

ip & op inphase + feedback.

ip & op out " - " mixing

1) Voltage series shunt  $\rightarrow$  sampling

2) Current series " series "


3) Voltage shunt shunt "

4) Current shunt " series "

Sampling + Mixing

## Voltage Sampling

parallel shunt

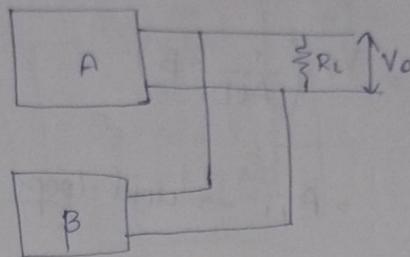

$$\text{sample} - V - \text{shunt}$$


i-series

$$\text{mix} - V - \text{series}$$

i-shunt

## Current Sampling



series

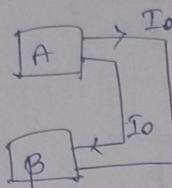

$$A_i V = \frac{V_o}{\sqrt{i}}$$


## Voltage mixing

## Current mixing

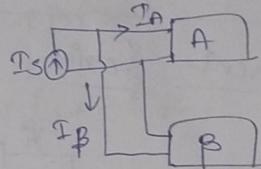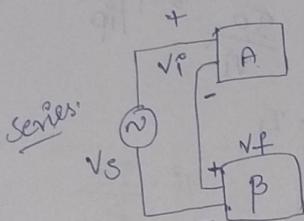

parallel shunt

## Voltage Series feedback topology | shunt series shunt

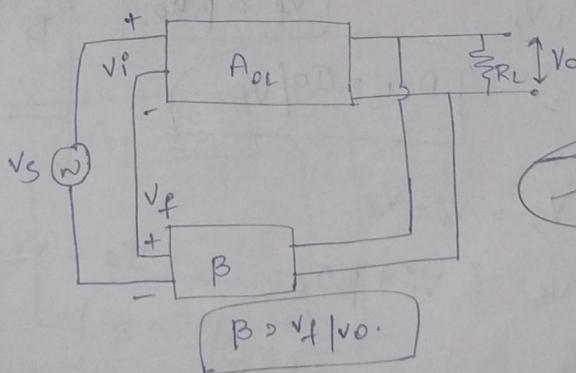

~~$$A_i = \frac{I_o}{\frac{V_o}{A_{OL}}}$$~~

$$A_{OL} = \frac{V_o}{V_i} \Rightarrow V_i = V_o / A_{OL}$$

$$V_s = V_i + V_f$$

$$V_s = V_i + B V_o$$

$$V_S = \frac{V_O}{A_{OL}} + \beta V_O$$

$$V_S = V_O \left( \frac{1}{A_{OL}} + \beta \right)$$

$$\frac{V_O}{V_S} \rightarrow A_{CL} \rightarrow \text{closed loop}$$

$$V_S = V_O \left( \frac{1}{A_{OL}} + \beta \right) \Rightarrow \left( \frac{1 + \beta A_{OL}}{A_{OL}} \right) V_O = V_S$$

$$V_O = V_S \left( \frac{A_{OL}}{1 + \beta A_{OL}} \right)$$


Negative feedback  
adv.

$$\frac{V_O}{V_S} \rightarrow \frac{A_{OL}}{1 + \beta A_{OL}}$$

- ① less interference
- ② less noise.

current series
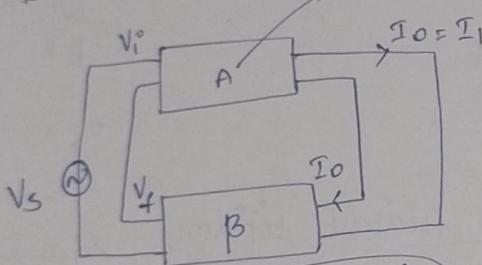
$$A_{OL} = \frac{I_O}{V_i} \rightarrow \frac{I_O}{I_P} = \frac{P_o}{P_i}$$



$$V_i = \frac{I_O}{A_{OL}}$$

$$V_S = V_i + V_f$$

$$A_{CL} = I_O / V_S$$

$$\beta = \frac{V_f}{I_O}$$

$$V_S = V_i + V_f$$

$$V_S = V_i + \beta I_O$$


$$= \frac{I_O}{A_{OL}} + \beta I_O$$

$$I_O = V_S \left( \frac{A_{OL}}{A_{OL}\beta + 1} \right)$$

$$V_S = I_O \left( \beta + \frac{1}{A_{OL}} \right)$$

$$A_{CL} = \frac{V_S}{I_O} = \frac{A_{OL}}{A_{OL}\beta + 1}$$

## Voltage shunt

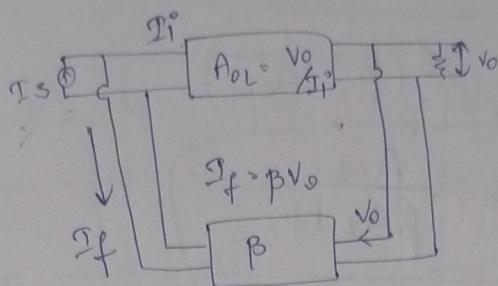

$$P = I_f / V_o$$

$$A_{OL} = \frac{V_o}{I_i}$$

$$A_{CL} = \frac{V_o}{I_S}$$

$$I_S = I_i + I_f$$


$$I_S = I_i + \beta V_o$$

$$I_S = I_i + \beta A_{OL} I_i$$

$$I_S = I_i (1 + \beta A_{OL})$$

$$I_S = I_i (1 + \beta A_{OL}) \left( \frac{V_o}{A_{OL}} \right)$$

## Current shunt

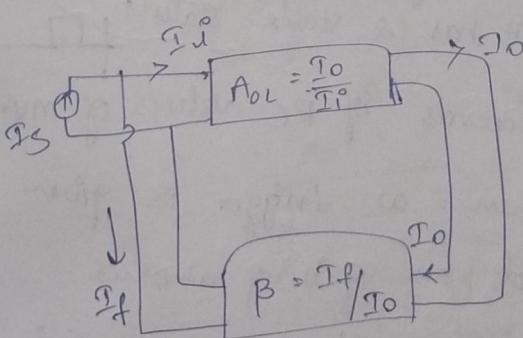

$$A_{OL} = \frac{I_o}{I_i}$$

$$A_{CL} = \frac{I_o}{I_S}$$

$$I_S = I_f + I_i$$

$$= \beta I_o + \frac{I_o}{A_{OL}}$$

$$I_S = I_o \left( \beta + \frac{1}{A_{OL}} \right)$$

$$I_f > \beta I_o$$

$$A_{CL} = \frac{I_0}{R \left( \beta + \frac{1}{A_{OL}} \right)}$$

$$\boxed{A_{CL} = \frac{A_{OL}}{\beta A_{OL} + 1}}$$

4/11/24:

### IC 555 Timers.

555  $\rightarrow$  3, 5K $\Omega$  Resistors


$\hookrightarrow$  Manufactured by

① Signetics  $\rightarrow$  NE 555 timer IC

Tachometers,  
Waveform Generation,

$\hookrightarrow$  Relaxation oscillators.

(Non sinusoidal waveform).


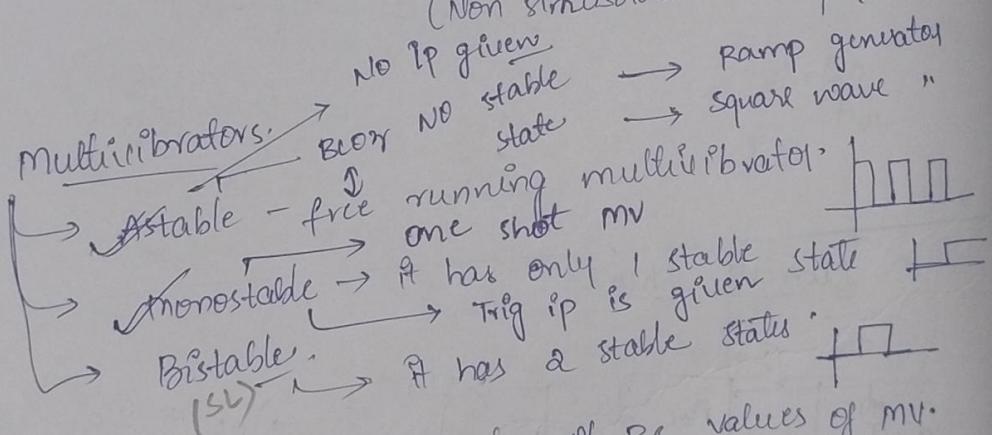


ON & OFF depends of RC values of MV.

Bistable means when a trigger is given goes to high state and on giving another trigger it goes to low.  $\hookrightarrow$  used as flip flop frequency divider.

# IC 555 Timer

→ definite stable timer

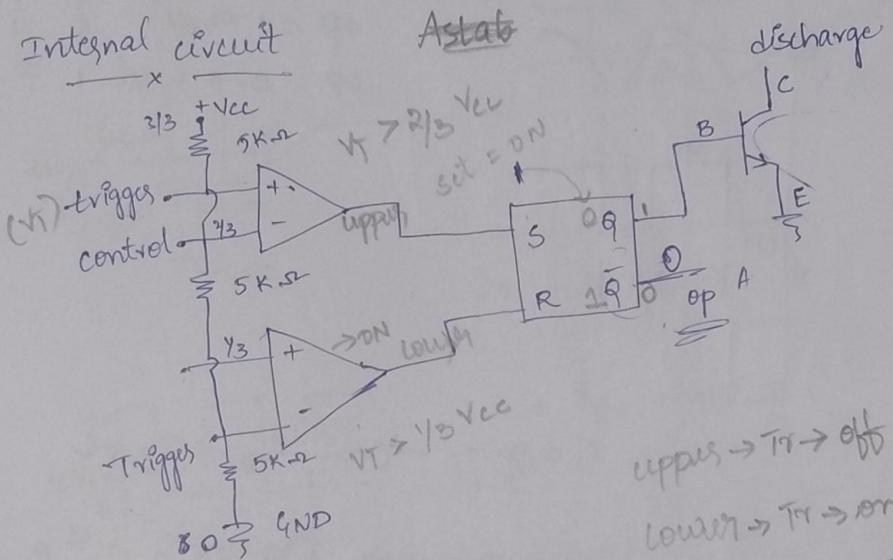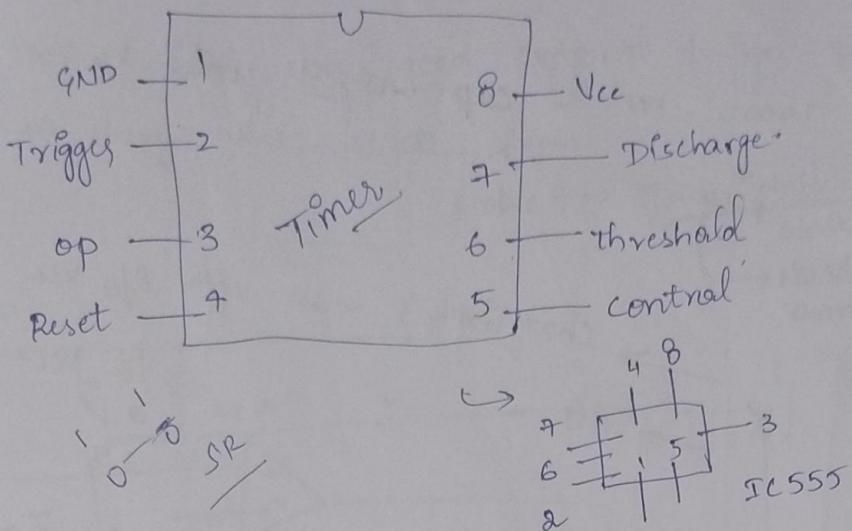


## SR flip flop

S	R	Q	Q̄	invited
0	0	0	1	
0	0	1	0	
0	0	0	1	set
0	1	1	0	
1	0	0	0	reset
1	0	1	0	
1	1	0	1	no change
1	1	1	1	

$$\begin{cases} S = 1 \quad Q = 1 \quad \bar{Q} = 0 \\ R = 1 \quad Q = 0 \quad \bar{Q} = 1 \end{cases}$$

$$\begin{cases} S = 1 \quad V_T > \frac{2}{3}V_{cc} \\ L \frac{1}{3}m \quad R = 1 \end{cases}$$
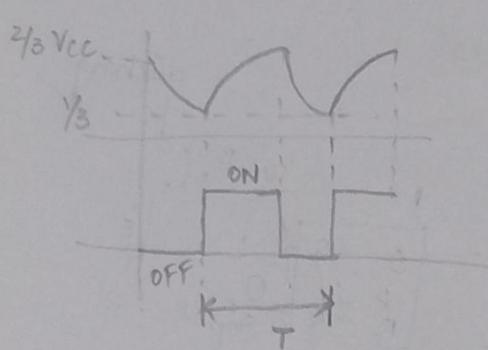
$$\begin{cases} S = 1 \quad Q/P \\ R = 1 \quad Q = 0 \\ a = 1 \end{cases}$$



$$\begin{array}{l} \text{op} = 1 \rightarrow \text{set } 0 \quad 1 \\ \text{op} = 0 \rightarrow \text{reset } 1 \quad 0 \end{array}$$



Here 2555 - astable  $\xrightarrow{\text{Nop}}$  - oscillat<sup>or</sup>.  
- mono - timer.  
- hyst<sup>er</sup> - flip

$$^{10} \text{ Duty cycle} = \frac{T_{on}}{T}$$

- monostable
- bistable - flip
- clock frequency
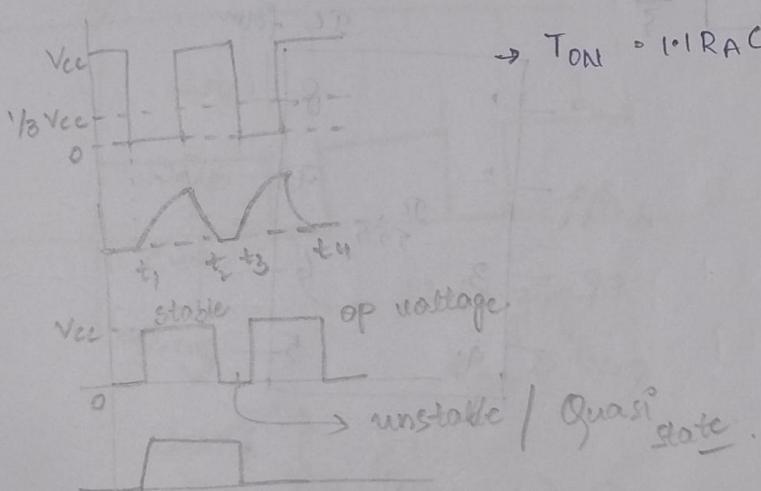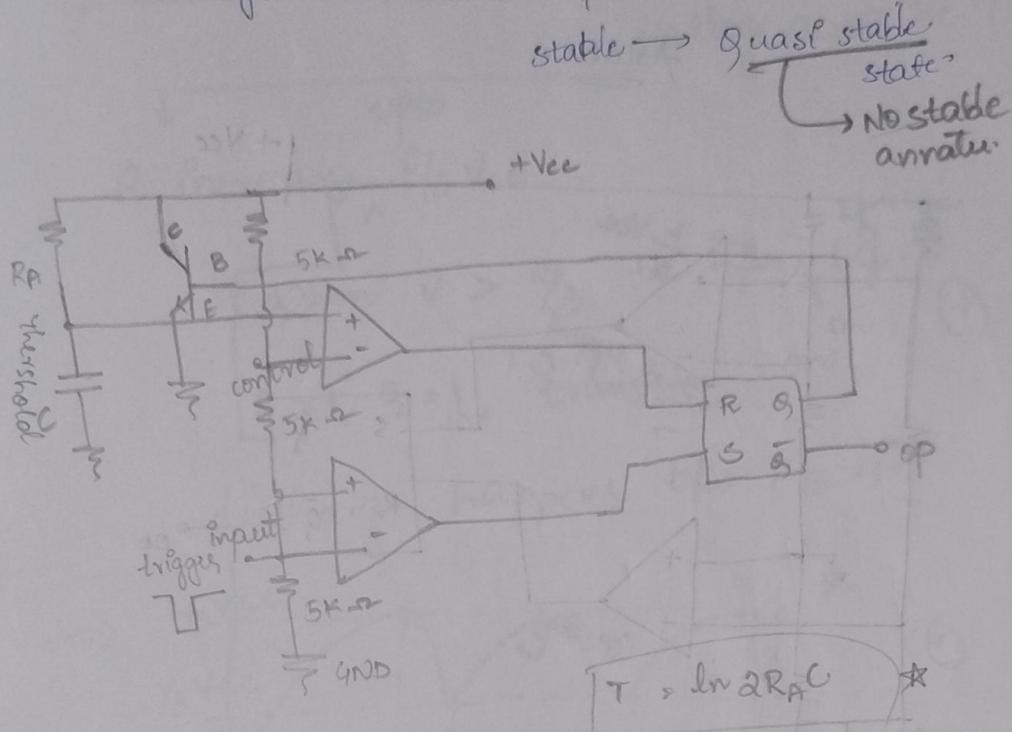
## \* Monostable \*

- It's only have one stable state
- To operate you need external trigger, so this is to change the state from





\* multivibrator circuit, oscillates b/w a high state & a low state producing a continuous op

Astable  $\rightarrow$  multivibrator has even duty cycle:  
ON - 50%  
OFF - 50%  $T = T_{ON} + T_{OFF}$

Monostable is called one shot ms that have one stable state. As external ip is given it returns back to its original state.

Astable

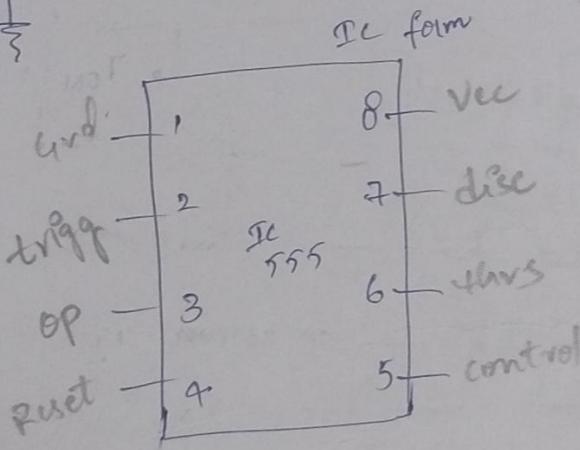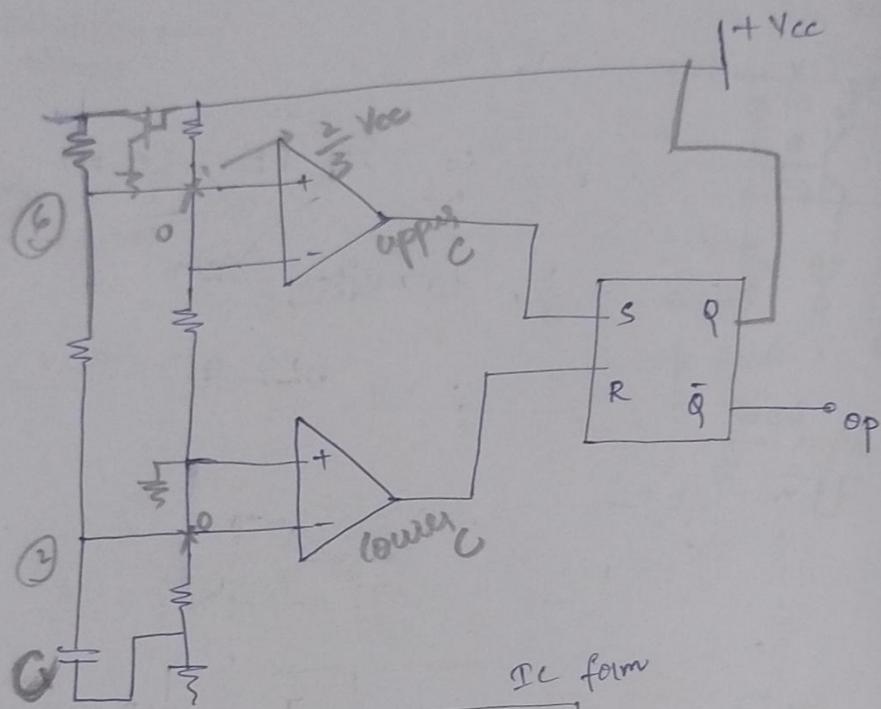

$$\textcircled{6}, \textcircled{2} = 0V$$

$$x < \frac{1}{3} Vcc \quad LC = 1 \rightarrow \text{Reset} = 1$$

$$\text{Initially } x' = 0 < \frac{2}{3} Vcc \rightarrow \text{to turn on}$$

$$x' > \frac{2}{3} Vcc \rightarrow$$

$R = 1$ ,  $Q = 0$ , transistors = off

No  $i$  in Base,  $C_L$  will be charging

-through  $V_{CC}$ ,  $R_A, R_B$ .

voltage across  $V_C \uparrow$


↓ upto

it increases,  $\sqrt{3} V_{CC}$ .

when  $V > \sqrt{3} V_{CC}$ ,  $U_C = 1$ ,  $I_C = 0$

$S = 1$ ,  $Q = 1$ , transistors = on

discharge happens b/w  $R_B, C$ .

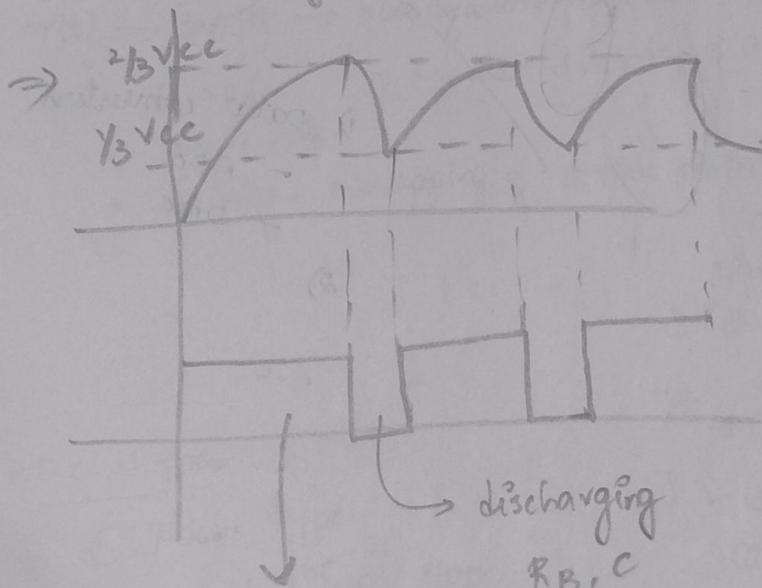


charging  
 $R_A, R_B, C$

discharging  
 $R_B, C$

$$T_{ON} = 0.693 (R_A + R_B)C \quad T_{OFF} = 0.693 R_B C$$

Duty cycle =  $T_{ON} + T_{OFF}$   $T > 0.693 (R_A + 2R_B)C$
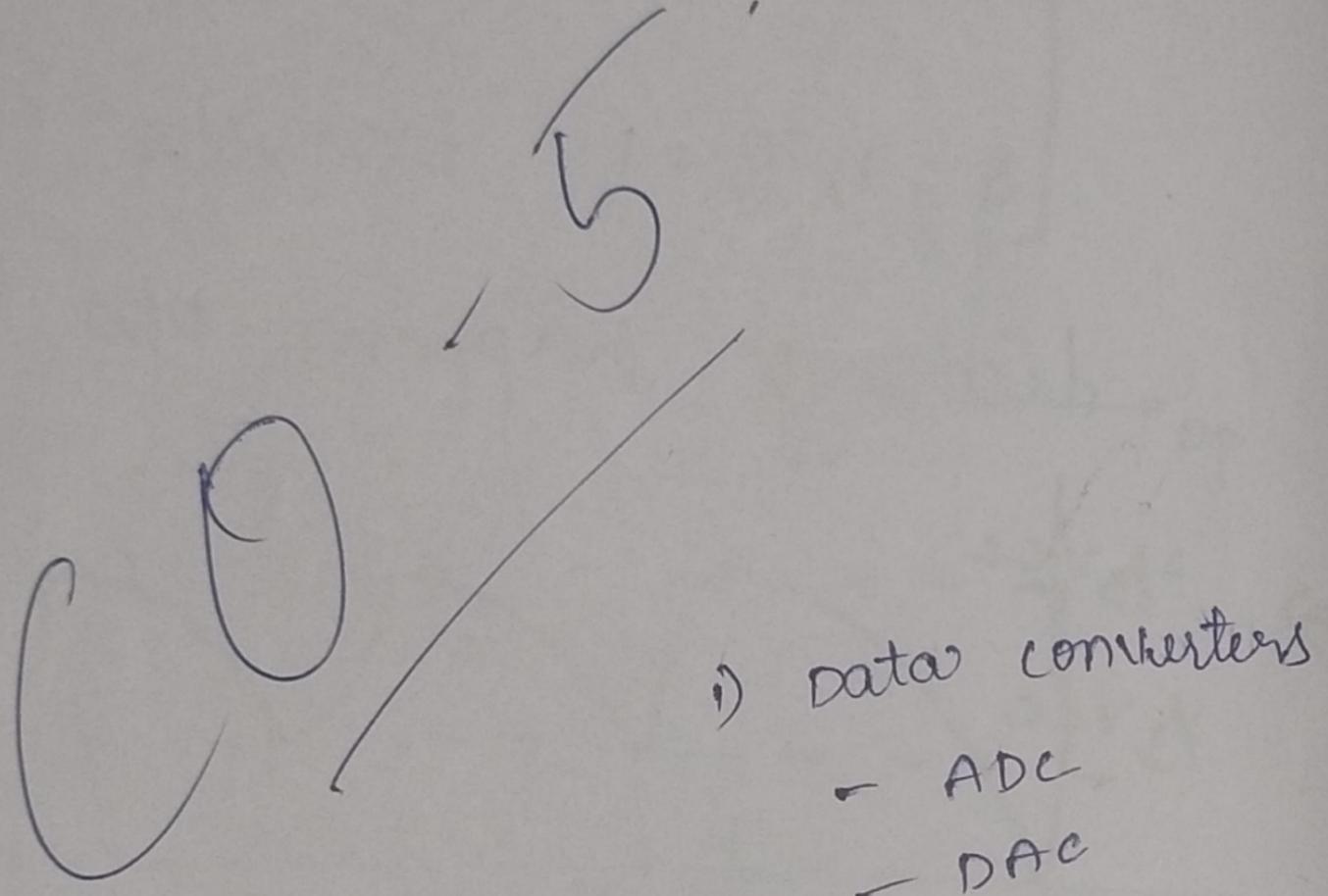
$$\Rightarrow \frac{0.693 (R_A + R_B)C}{0.693 (R_A + 2R_B)C} \text{ duty cycle} = \frac{R_A + R_B}{R_A + 2R_B}$$



11/11/24

## Analog to Digital & converters

Sampling - continuous in amplitude  
discrete in time

Analog - conts in time, amplitude

conditions for sampling

①  $f_s \geq 2f_{msg}$  → sampling theorem  
↳ sampling

②  $T_s \leq \frac{1}{2f_m}$  → Nyquist theorem.

Quantization - discrete in time, amplitude

$m(t) \rightarrow$  sample → quantization → encoder

- $f_s > 2f_m$  → amplitude
- Nyquist rate
- aliasing - overlapping of 2 time periods.

encodes the signal by assigning 0, 1 to amplitude

DAC types

ADC types

- ① Flash type
  - ② single / dual slope
  - ③ successive approximation
  - ④ Delta sigma
- ① Binary weighted resistors
- ② R- $\Delta$  ladder types

Sampling we use sample & hold circuit to get correct time period samples.

ADC

→ 3 bit ADC

→ full scale output voltage

(1)

$$V_{ref}/2$$


Resolution - given in no of bits

$$\frac{V_{max} - V_{min}}{2^n}$$

full scale outputs voltage

$$2^m$$
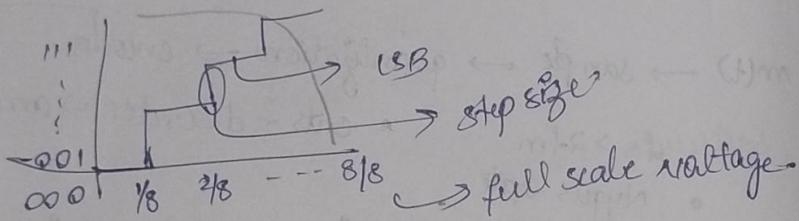
$$\begin{aligned} \text{Min voltage for ADC} &= 1.25 \text{ V.} \rightarrow \frac{10}{2^3} \\ &= 125 \text{ mV.} \end{aligned}$$



001 → 010

Step size = 1.25 because it's min for ADC conver-

at 1/8 = 111

$$\boxed{\text{Resolution} = \frac{(2^n - 1) V_{ref}}{2^n}}$$

Step size

$$\Rightarrow \text{Resolution} = 2^n - 1 \times \text{step size}$$

Rate at which ADC converted at which  
is no of bits converted to digital of

No of bits ↑ Resolution ↑