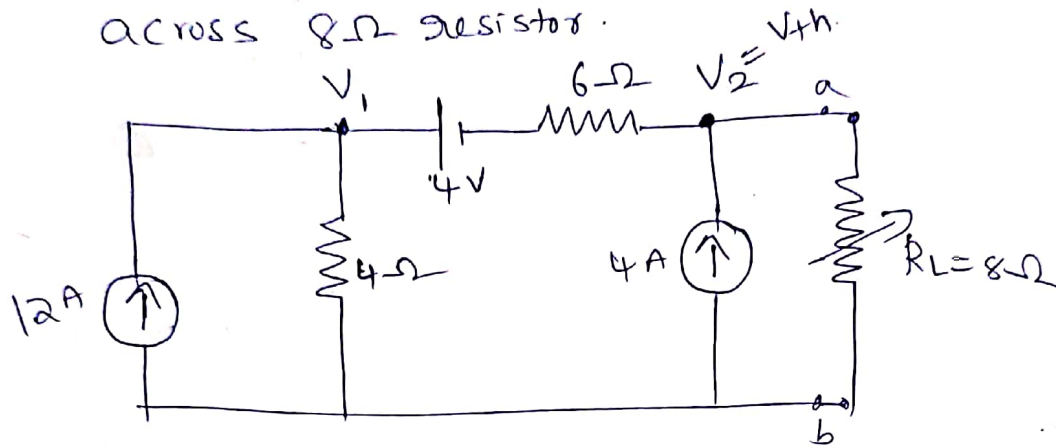


ALM-3 Solutions

① Thevenin's theorem. Calculate current across 8Ω resistor.



To find V_{th} Open circuit R_L Apply nodal analysis

$$\text{At } V_1: \frac{V_1}{4} + \frac{V_1 - 4 - V_{th}}{6} = 12$$

$$3V_1 + 2V_1 - 8 - 2V_{th} = 144$$

$$5V_1 - 2V_{th} = 152 \longrightarrow \textcircled{1}$$

At V_2

$$\frac{V_{th} + 4 - V_1}{6} = 4$$


$$-V_1 + V_{th} = 20 \longrightarrow \textcircled{2}$$

$$V_1 = 64V$$
$$V_{th} = V_2 = 84V$$

to find R_{th}


Voltage source — Short circuit

Current source — open circuit

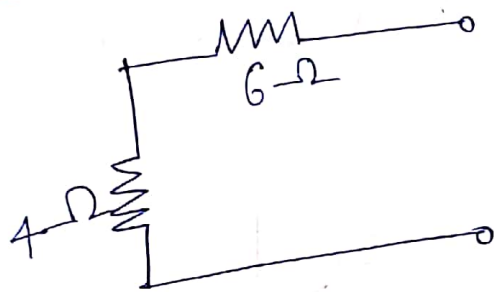

$$R_{th} = 6 + 4 = 10 \Omega$$

Thevenin's equivalent circuit

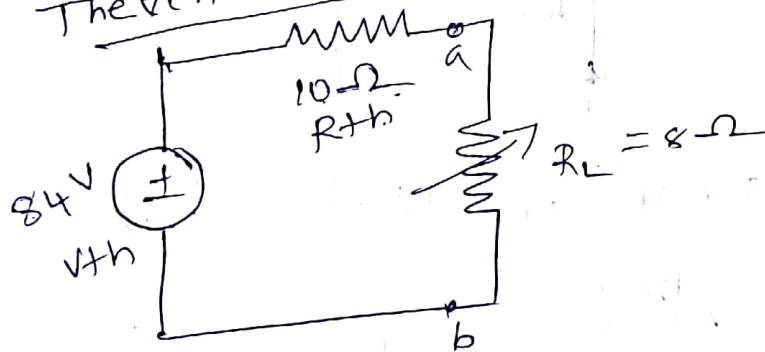


Current across R_L


$$\therefore I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{84}{10 + 8} = 4.67 A$$

$\therefore I_L = 4.67 A$

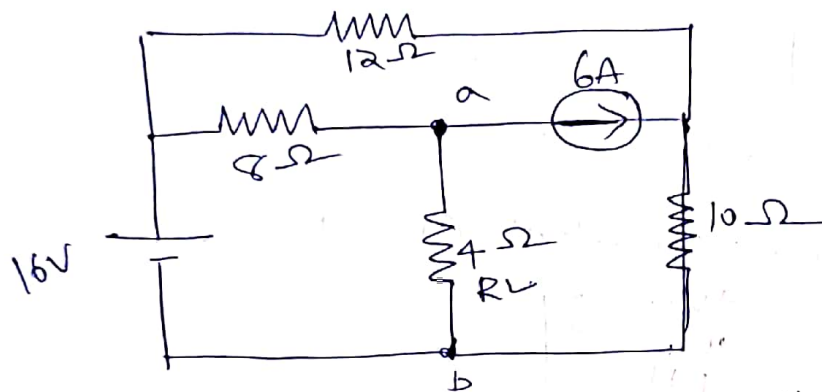② Norton's theorem. find current across 4Ω



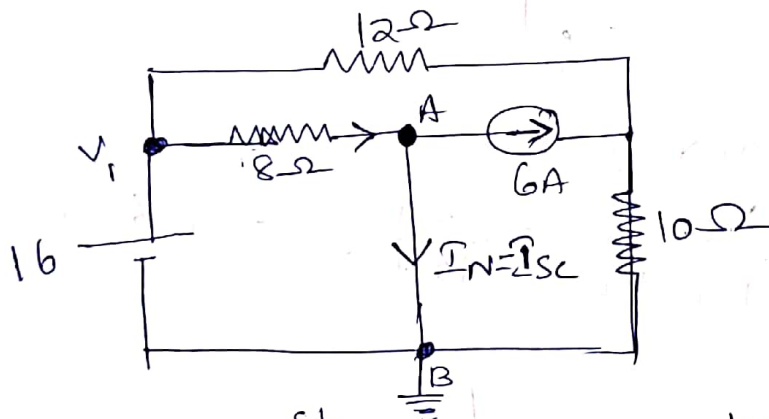Sol: Short circuit " R_L " to find " I_N "



From the 1st mesh we can directly write

$$\boxed{V_1 = 16V}$$

$$\text{Current through } 8\Omega \text{ resistor} = \frac{V_1}{8}$$

$$I_{8\Omega} = \frac{16}{8} = 2A$$

$$\boxed{I_{8\Omega} = 2A}$$

$$\text{Apply KCL at node A} \Rightarrow I_{8\Omega} = I_N + 6$$

Sum of the currents entering a node =
Sum of the currents leaving a node.

$$I_{SC} = I_N = I_{8\Omega} - 6 = 2 - 6 = -4A$$

$$I_{8\Omega} = I_N + 6$$


$$I_N = I_{8\Omega} - 6 = 2 - 6 = -4A$$

$$\boxed{I_N = -4A}$$

To find R_N

open circuit current source.


Short circuit voltage source.

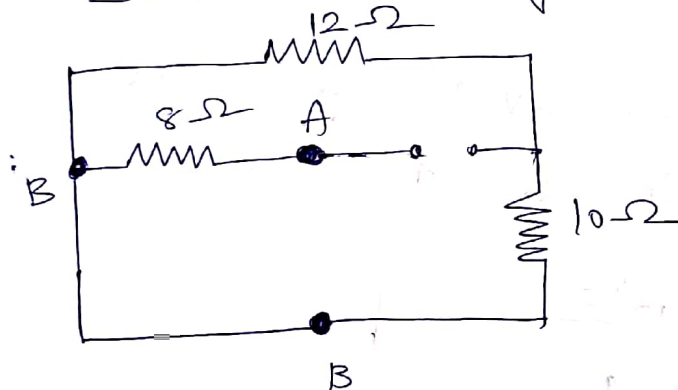

R_N = Resistance between node A and B

$$\boxed{R_N = 8\Omega}$$

Norton's equivalent circuit

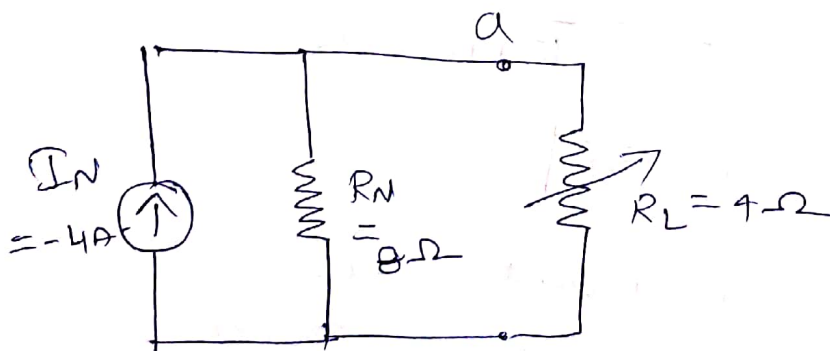


Current across " R_L " \Rightarrow Apply current division rule.

$$I_L = -4 \times \frac{8}{8+4}$$

$$\boxed{I_L = -2.67A}$$


$$= -\frac{8}{3} = -2.67A$$

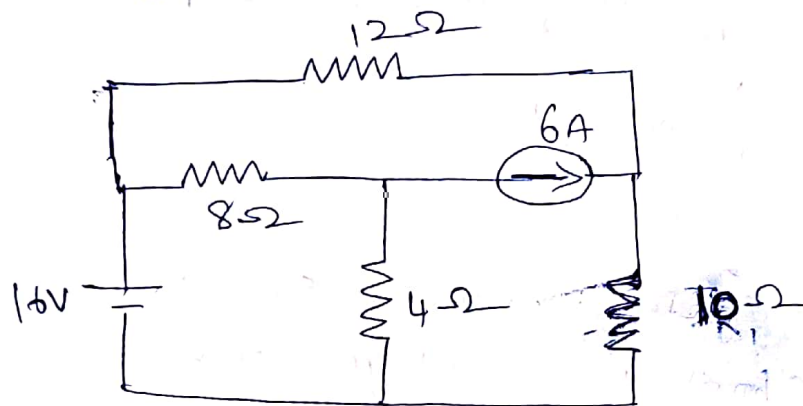③ Superposition theorem find current across 12Ω



Sol:-

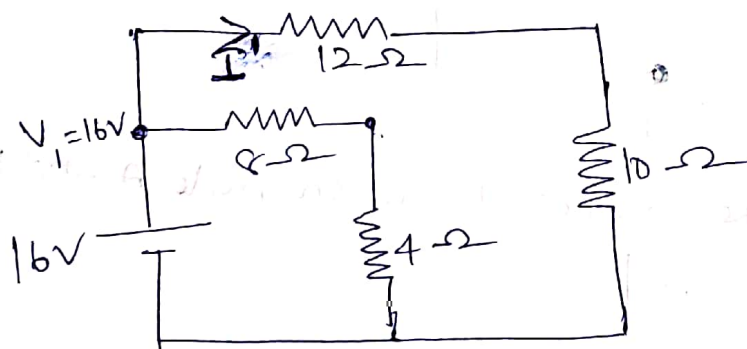Consider 16V Voltage Source.
open circuit current source.





$$I' = \frac{V}{R} = \frac{16}{12+10} = \frac{16}{22}$$

$$I' = 0.73A$$


Consider 6A Current Source.

Short circuit voltage source.

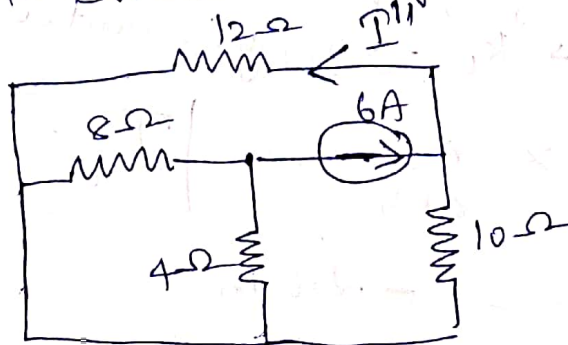

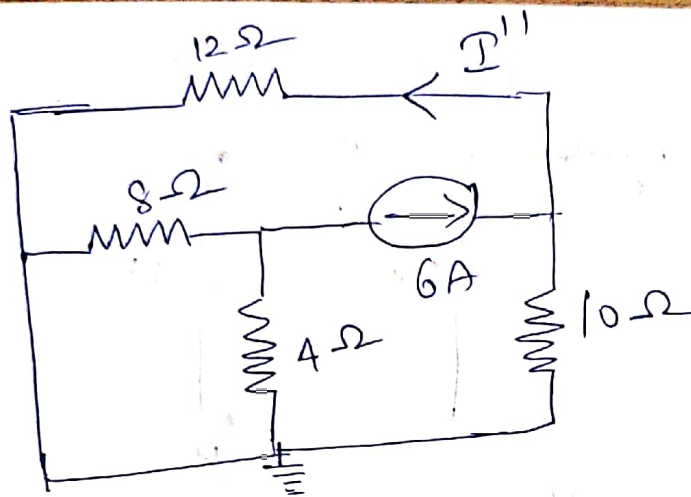

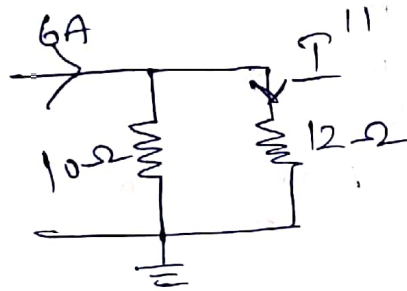Here
 $10\Omega // 12\Omega$
 We can
 re-draw it
 as



Apply
 current
 division rule.

$$I'' = 6 \times \frac{10}{10+12}$$

$$I'' = \frac{60}{22}$$

$$I'' = 2.73 \text{ A}$$


By superposition $I_{12\Omega} = I' - I''$
 $= 0.73 - 2.73$

$$I_{12\Omega} = -2 \text{ A}$$

∴ Current across 12Ω resistor is


$$I_{12\Omega} = -2 \text{ A}$$

④ Maximum power transfer theorem

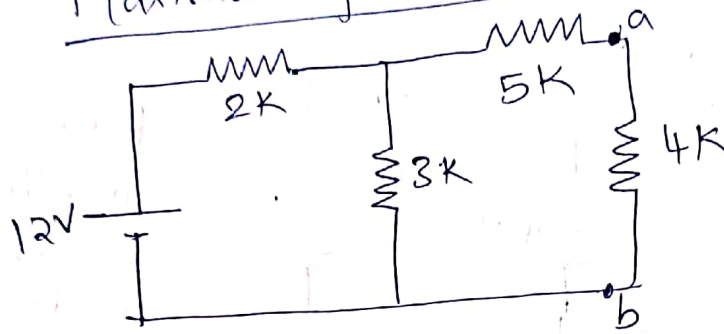

Sol:- To find V_{th}

open circuit " R_L "

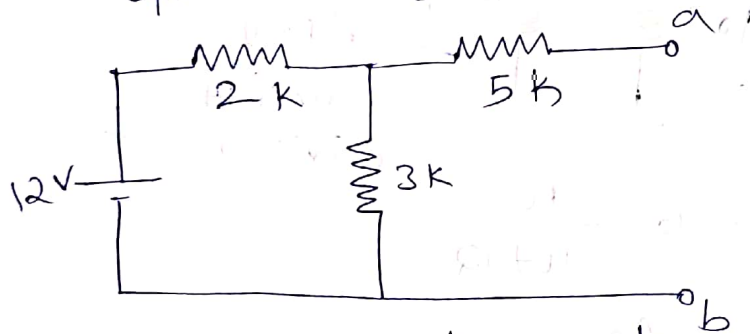

Apply voltage division rule.

$$V_{th} = \text{Total voltage} \times \frac{\text{across that resistor}}{\text{Sum of resistor}}$$


$$= 12 \times \frac{3}{2+3}$$

$$= 36/5 = 7.2V$$

$$\boxed{V_{th} = 7.2V}$$

To find R_{th}

~~open~~ Short circuit Voltage Source

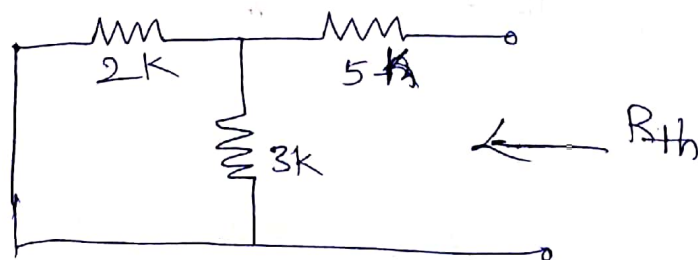


$$R_{th} = \left(\frac{2 \times 3}{2+3} \right) + 5$$

$$= 5 + \frac{6}{5}$$

$$R_{th} = \frac{31}{5} = 6.2 \text{ k}\Omega \quad \therefore \boxed{R_{th} = 6.2 \text{ k}\Omega}$$

← Thevenin's equivalent circuit.

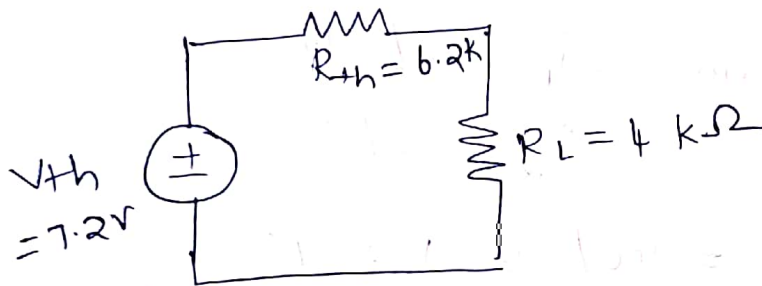

Current across R_L

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{7.2}{(6.2 + 4) \text{ k}} = 0.71 \text{ mA}$$

$$\boxed{I_L = 0.71 \text{ mA}}$$

power across 4Ω resistor.

$$P_{4\Omega} = I_L^2 R_L$$

$$= (0.71 \times 10^{-3})^2 \times 4000$$

$$\boxed{P_{4\Omega} = 2.02 \text{ mW}}$$

(ii) To achieve higher power $\boxed{R_L = R_{th}}$
At $R_L = 6.2 \text{ k}\Omega$ we will get higher power

$$P_{L \max} = \frac{V_{th}^2}{4 \times R_{th}} = \frac{(7.2)^2}{4 \times 6.2 \times 10^3} = 2.1 \text{ mW}$$

$$\boxed{P_{L \max} = 2.1 \text{ mW}}$$