

Experiment 4: FET CHARACTERISTICS

Aim/Objective: To study Drain Characteristics and Transfer Characteristics of a FET.


Description:

The basic circuit diagram for studying drain and transfer characteristics is shown in figure.


Drain characteristics are obtained between the drain to source voltage (V_{DS}) and drain current (I_D) taking gate to source voltage (V_{GS}) as the parameter.

Transfer characteristics are obtained between the gate to source voltage (V_{GS}) and Drain current (I_D) taking drain to source voltage (V_{DS}) as parameter.

Circuit Diagram:

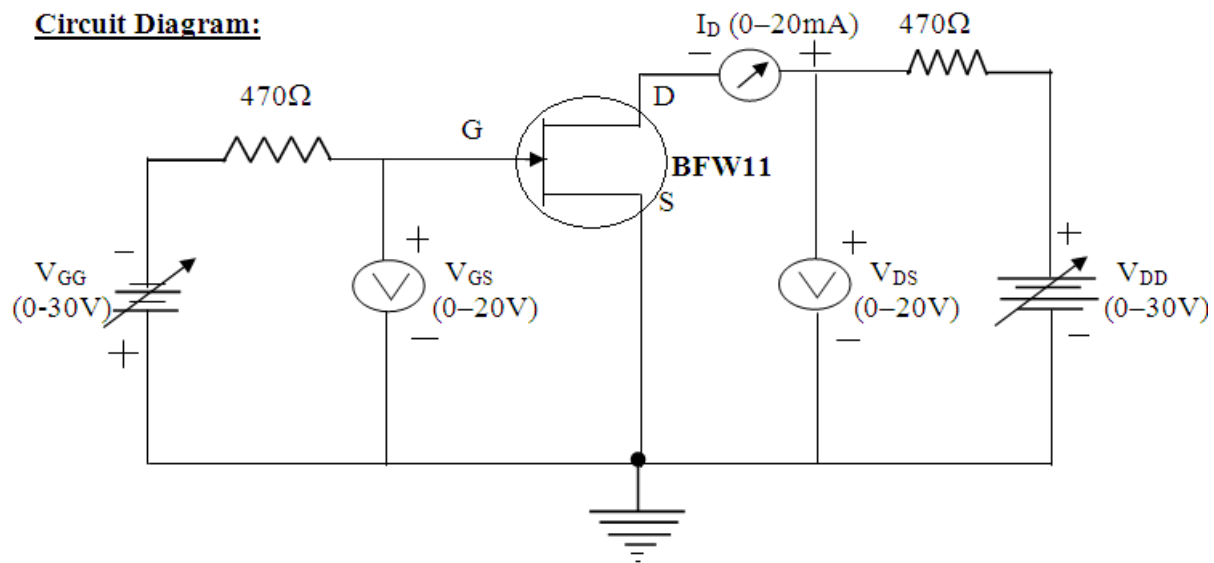

Pin assignment of FET:

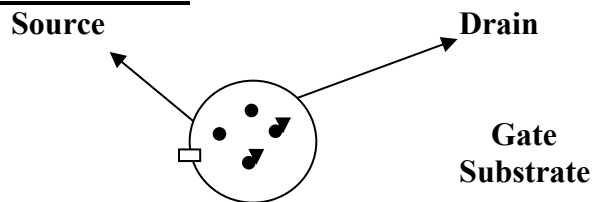

Pre lab session

- 1) What is the basic structure and working principle of a JFET (Junction Field Effect Transistor)? How does it differ from a BJT?**
- 2) Define pinch-off voltage in a JFET. What happens to the drain current beyond this voltage in the output characteristics?**
- 3) How are the input and output characteristics of a JFET measured? Which terminals are involved in each case?**
- 4) What is the significance of the high input impedance of a FET in analog applications?**

In-Lab Session

Procedure:

Drain Characteristics

1. Make the connections as per circuit diagram.
2. Keep $V_{GS} = 0V$ by varying V_{GG} .
 1. Varying V_{DD} gradually, note down both drain current I_D and drain to source voltage (V_{DS}).
2. Step Size is not fixed because of non linear curve and vary the X-axis variable (i.e. if output variation is more, decrease input step size and vice versa).
3. Repeat above procedure (step 3) for $V_{GS} = -1V$.

Transfer characteristics:

1. Keep $V_{DS} = 2V$ by varying V_{DD} .
2. Varying V_{GG} gradually from 0 – 5V, note down both drain current (I_D) and gate to source voltage (V_{GS}).
3. Step Size is not fixed because of non linear curve and vary the X-axis variable (i.e. if output variation is more, decrease input step size and vice versa).
4. Repeat above procedure (step 2) for $V_{DS} = 4V$.


Tabular column:

Drain characteristics:

$V_{GS} = -1V$			$V_{GS} = -2V$	
S.No	V_{DS} (V)	I_D (mA)	V_{DS} (V)	I_D (mA)
1				
2				
3				
4				
5				
6				
7				
8				
9				
10				

Transfer characteristics:

$V_{DS} = 2V$			$V_{DS} = 4V$	
S.No	V_{GS} (V)	I_D (mA)	V_{GS} (V)	I_D (mA)
1				
2				
3				
4				
5				
6				
7				
8				
9				
10				

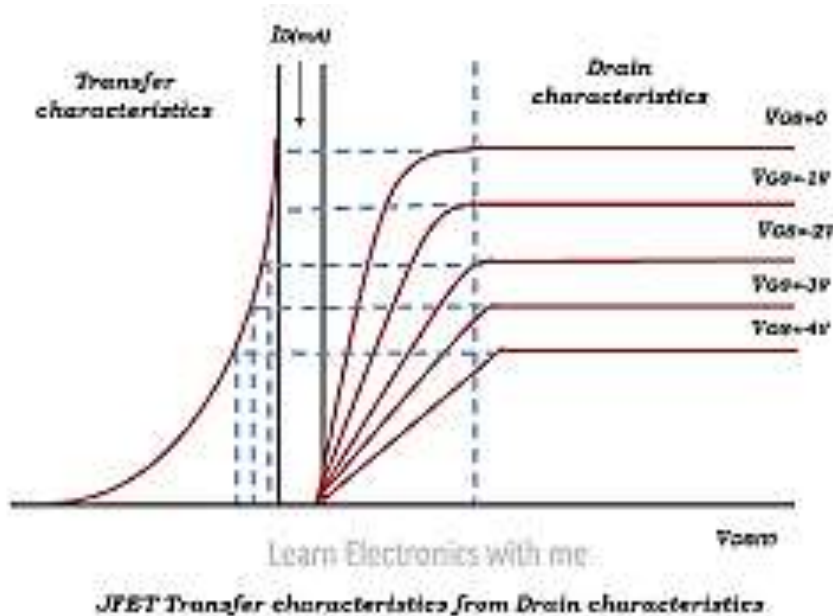

Calculations:

Drain Resistance (r_d): It is given by the ratio of small change in drain to source voltage (ΔV_{DS}) to the corresponding change in Drain current (ΔI_D) for a constant gate to source voltage (V_{GS}), when the JFET is operating in pinch-off or saturation region.

Trans-Conductance (g_m) : Ratio of small change in drain current (ΔI_D) to the corresponding change in gate to source voltage (ΔV_{GS}) for a constant V_{DS} .

$g_m = \Delta I_D / \Delta V_{GS}$ at constant V_{DS} . (from transfer characteristics)

The value of g_m is expressed in mho's or siemens (s).

Amplification Factor (μ) : It is given by the ratio of small change in drain to source voltage (ΔV_{DS}) to the corresponding change in gate to source voltage (ΔV_{GS}) for a constant drain current.

$$\mu = \Delta V_{DS} / \Delta V_{GS}.$$

$$\mu = (\Delta V_{DS} / \Delta I_D) \times (\Delta I_D / \Delta V_{GS})$$

$$\mu = r_d \times g_m.$$

Result:

Viva-Voce

- Which of the following parameters defines the amplification capability of a FET?
 - Transconductance (g_m)
 - Input resistance
 - Drain resistance
 - Cut-off frequency

2. In the output characteristics of an n-channel JFET, the region where drain current becomes constant is called the:
- A. Ohmic region
 - B. Saturation region
 - C. Cut-off region
 - D. Breakdown region
3. The input impedance of a FET is typically:
- A. Very low
 - B. Low
 - C. Moderate
 - D. Very high
4. Pinch-off voltage (V_p) in a JFET is the:
- A. Maximum gate voltage for conduction
 - B. Voltage at which gate current becomes maximum
 - C. Drain-source voltage at which drain current saturates
 - D. Gate-source voltage at which drain current becomes almost zero
5. For a JFET operating in the active (saturation) region, the drain current is primarily controlled by:
- A. V_{DS}
 - B. V_{GS}
 - C. Gate current
 - D. Load resistance

Inference and Analysis:

Evaluator Remark (if Any):	Marks Secured: ____ out of 50
	Signature of the Evaluator with Date