

ALM-4 solutions

$$1) \quad i_1 = 100 \sin(100t)$$

$$i_1 = 100 \cos(100t - 90^\circ)$$

$$i_2 = 200 \cos(100t + 30^\circ)$$

$$\text{Phasor form} \Rightarrow i_1 = 100 \angle -90^\circ$$

$$i_2 = 200 \angle 30^\circ$$

$$a) \quad i_1 + i_2 = 100 \angle -90^\circ + 200 \angle 30^\circ$$

$$= 100 [\cos(-90^\circ) + j \sin(-90^\circ)]$$

$$+ 200 [\cos 30^\circ + j \sin 30^\circ]$$

$$= -j100 + 173.2 + j100$$

$$= 173.2$$

$$i_1 + i_2 = 173.2 \angle 0^\circ$$

$$\boxed{i_1 + i_2 = 173.2 \cos(100t)}$$

$$b) \quad i_1 - i_2 = -173.2 - j200$$

$$|i_1 - i_2| = \sqrt{(-173.2)^2 + (-200)^2} = 264.57$$

$$\theta = \tan^{-1}\left(\frac{-200}{-173.2}\right) = 229.1^\circ$$

$$\boxed{i_1 - i_2 = 264.57 \cos(100t + 229.1^\circ)}$$

$$c) \quad i_1 \cdot i_2 = 100 \angle 90^\circ \cdot 200 \angle 30^\circ$$

$$= 20000 \angle -60^\circ$$

$$\boxed{i_1 \cdot i_2 = 20000 \cos(100t - 60^\circ)}$$

$$d) \quad \frac{i_1}{i_2} = \frac{100 \angle -90^\circ}{200 \angle 30^\circ} = \frac{1}{2} \angle -90^\circ - 30^\circ$$

$$= \frac{1}{2} \angle -120^\circ$$

$$\boxed{\frac{i_1}{i_2} = \frac{1}{2} \cos(100t - 120^\circ)}$$

$$e) \quad \left(\frac{i_1}{i_2} \right)^2 = \left[\frac{100 \angle -90^\circ}{200 \angle 30^\circ} \right]^2$$

$$= \left[\frac{1}{2} \angle -120^\circ \right]^2$$

$$= \frac{1}{4} \angle -240^\circ$$


$$\boxed{\left(\frac{i_1}{i_2} \right)^2 = \frac{1}{4} \cos(100t - 240^\circ)}$$

$$f) \quad (i_1 \cdot i_2)^3 = \left[100 \angle 90^\circ \times 200 \angle 30^\circ \right]^3$$

$$= \left[20000 \angle -60^\circ \right]^3 = 20000^3 \angle -180^\circ$$

$$= 20000^3 \cos(100t - 180^\circ)$$

②

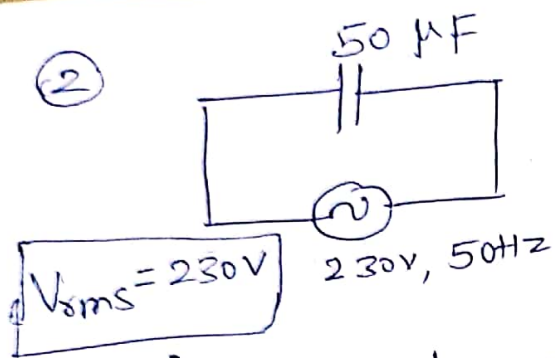

$$\omega = 2\pi f$$

$$a) X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$= \frac{1}{2\pi \times 50 \times 50 \times 10^{-6}}$$

$$X_C = 63.66 \Omega$$

$$b) I_{\max} = \frac{V_{\max}}{X_C}$$

$$V_{\max} = V_{\text{rms}} \times \sqrt{2}$$

$$= 230 \times 1.414$$


$$V_{\max} = 325.22 \text{ V}$$

$$I_{\max} = \frac{325.22}{63.66} = 5.11 \text{ A} \Rightarrow \frac{V_{\max}}{X_C}$$

$$I_{\max} = 5.11 \text{ A}$$

$$c) I_{\text{rms}} = \frac{V_{\text{rms}}}{X_C} = \frac{230}{63.66} = 3.61 \text{ A}$$

3

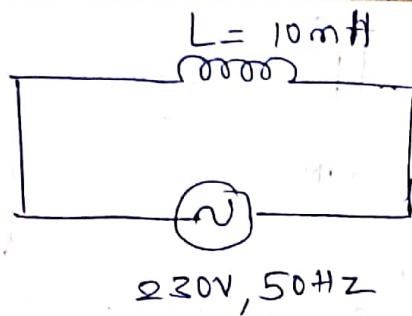

$$V_{\text{rms}} = 230\text{V}$$

$$f = 50\text{Hz}$$

$$L = 10\text{mH}$$

$$\begin{aligned} \text{a) } X_L &= \omega L = 2\pi fL \\ &= 2\pi \times 50 \times 10 \times 10^{-3} \end{aligned}$$

$$X_L = 3.142 \Omega$$

$$\text{b) } I_{\text{max}} = \frac{V_{\text{max}}}{X_L}$$

$$V_{\text{max}} = V_{\text{rms}} \times \sqrt{2} = 230 \times 1.414 = 325.22$$


$$V_{\text{max}} = 325.22 \text{ V}$$

$$I_{\text{max}} = \frac{325.22}{3.142} = 103.5 \text{ A}$$

$$I_{\text{max}} = 103.5 \text{ A}$$

$$\text{c) } I_{\text{rms}} = \frac{V_{\text{rms}}}{X_L} = \frac{230}{3.142} = 73.2 \text{ A}$$

$$I_{\text{rms}} = 73.2 \text{ A}$$

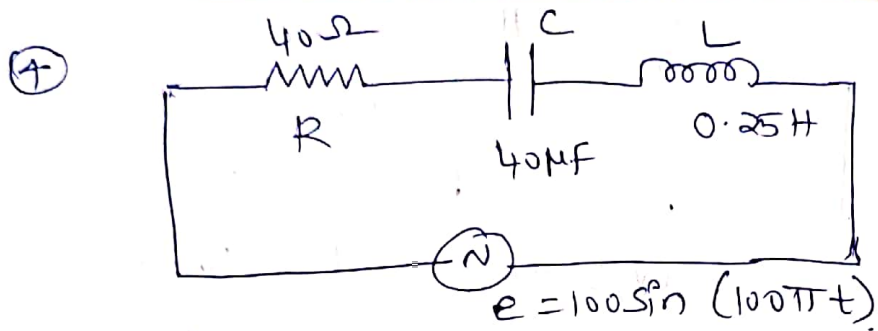

$$V_{\max} = 100$$

$$V_{\text{rms}} = \frac{V_{\max}}{\sqrt{2}} = \frac{100}{\sqrt{2}} = 70.7 \text{ V}$$

$$\boxed{V_{\text{rms}} = 70.7 \text{ V}}$$

$$(i) \quad X_L = \omega L = 2\pi f L = 100\pi \times 0.25 = 78.54\Omega$$

$$\boxed{X_L = 78.54\Omega}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{100\pi \times 40 \times 10^{-6}} = 79.58\Omega$$

$$\boxed{X_C = 79.58\Omega}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{40^2 + (78.54 - 79.58)^2}$$

$$\boxed{Z = 40.01\Omega}$$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} = \frac{70.7}{40.01} = 1.77 \text{ A}$$

$$\boxed{I_{\text{rms}} = 1.77 \text{ A}}$$

(ii) power supplied

(or)

$$I_{rms}^2 R = V_{rms} I_{rms} \cos \phi$$

$$= 70.7 \times 1.77 \times 0.998$$

$$= 125 \text{ W}$$

$$\cos \phi = \frac{R}{Z}$$

$$= \frac{40}{40.01}$$

$$\boxed{\cos \phi = 0.998}$$

(iii) power factor = $\cos \phi = 0.998$

$$\Rightarrow \frac{R}{Z} = 0.998$$

⑤ RLC Series Circuit

$$V(t) = 283 \sin(100\pi t)$$

$$\begin{array}{l|l} V_m = 283 & I_{\max} = 0.314 \\ \omega = 100\pi & V_c = 300V \end{array}$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} = \frac{283}{\sqrt{2}} = 200V$$

$$\begin{array}{l} I_{\max} = \frac{V_{\text{rms}}}{R} \Rightarrow R = \frac{V_{\text{rms}}}{I_{\max}} = \frac{200}{0.314} \\ \text{at resonance.} \end{array}$$
$$= 637\Omega$$

$$V_c = I_{\max} X_c$$

$$\Rightarrow X_c = \frac{V_c}{I_{\max}} = \frac{300}{0.314}$$
$$= 955\Omega$$

$$C = \frac{1}{\omega_0 X_c}$$

$$= \frac{1}{100\pi \times 955}$$

$$\boxed{C = 3.34 \mu F}$$

At resonance $X_L = X_c$; So, $X_L = 955\Omega$

$$L = \frac{X_L}{\omega_0} = \frac{955}{100\pi} = 3.04H$$

$$Q\text{-factor} = \frac{\omega_0 L}{R}$$

$$Q. = \frac{100\pi \times 3.04}{637} = 1.5$$

$$\text{Bandwidth} = \frac{\omega_0}{Q}$$

$$= \frac{100\pi}{1.5}$$

$$B.W = 209.44 \text{ rad/sec.}$$