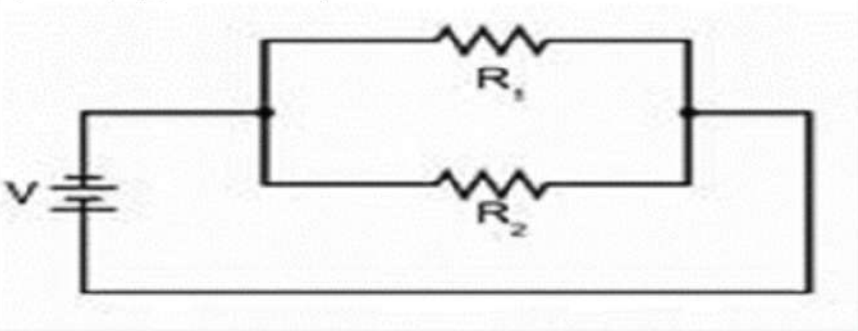
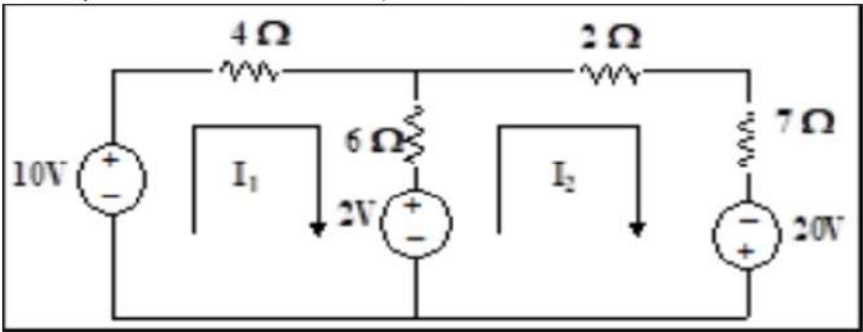
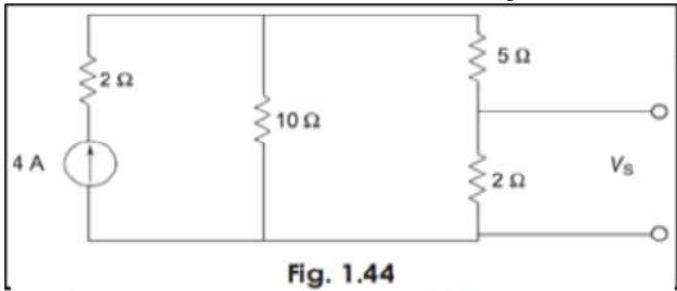


B.Tech - Even Sem : Semester in Exam-I
Academic Year:2023-2024
23EC1203 - BASIC ELECTRICAL AND ELECTRONIC CIRCUITS
Set No: 1

Time:		Max.Marks: 50					
S.NO	Answer All Questions	Choice	Options	Marks	CO	CO BTL	COI BTL
1.	ANSWER ALL QUESTIONS [6 x 2 = 12M]			12Marks	CO2	2	2
1.A.	Define KCL, KVL with formulae ?			2Marks	CO1	2	2
1.B.	How many Branches,loops, nodes exists in the given circuit? 			2Marks	CO1	2	2
1.C.	Distinguish ideal and practical voltage sources in all aspects ?			2Marks	CO1	2	2
1.D.	Mention the role of reactance in any electrical circuit ?			2Marks	CO2	2	2
1.E.	Define form factor, peak factor ?			2Marks	CO2	2	2
1.F.	Represent RMS, average Value in a sinusoidal wave form ?			2Marks	CO2	2	2

2.	ANSWER ALL QUESTIONS [4 x 4 = 16M]			16Marks	CO2	2	2
2.A.	Find the Thevenin's voltage across 40 ohm resistance in the given circuit ? <div data-bbox="327 835 858 1115" data-label="Diagram"> </div>			4Marks	CO1	2	2
2.B.	Calculate the total capacitance in a circuit consists of $C_1=5\mu F$, $C_2=10\mu F$ connected in parallel and series ?			4Marks	CO1	2	2
2.C.	Calculate i) Frequency ii) RMS VALUE III) AVERAGE VALUE IV) FORM FACTOR in a sinusoidal signal of voltage $40 \sin(628)t$			4Marks	CO2	2	2
2.D.	Calculate the average and RMS value of the square wave. <div data-bbox="284 1294 900 1487" data-label="Figure"> </div>			4Marks	CO2	2	2

3.	ANSWER ALL QUESTIONS [5 + 6 = 11M]	choice Q-4	11Marks	CO1	2	2
3.A.	Write the mesh equations and solve for the currents I_1 , and I_2 ? 		5Marks	CO1	2	2
3.B.	Explain about the V-I characteristics for passive elements, How to measure the energy stored across inductor and capacitor elements ?		6Marks	CO1	2	2
4.	ANSWER ALL QUESTIONS [5 + 6 = 11M]		11Marks	CO1	2	2
4.A.	If four resistors $R_1=R_2=20k\Omega$ and $R_3=R_4=10k\Omega$, is connected in series with a power supply of 20V , then calculate circuit current and individual voltages across each resistor ?		5Marks	CO1	2	2
4.B.	Determine the current in the 10Ω resistance and find V_s in the circuit shown in Fig. 1.44 		6Marks	CO1	2	2

5.	ANSWER ALL QUESTIONS [5 + 6 = 11M]	choice Q-6		11Marks	CO2	2	2
5.A.	Explain the concept of impedance in Series RL and RC circuit.			5Marks	CO2	2	2
5.B.	Draw the phasor representation of an alternating quantity represent phase lag and phase lead with waveforms			6Marks	CO2	2	2
6.	ANSWER ALL QUESTIONS [5 + 6 = 11M]			11Marks	CO2	2	2
6.A.	Write the polar form of the voltage given by $V = \sin(100\pi t + \pi/6)$ V and obtain its rectangular form.			5Marks	CO2	2	2
6.B.	Define bandwidth, resonant frequency, Qfactor in a series RLC circuit.			6Marks	CO2	2	2