



AY-2025-2026
ODD SEM

Department of ECE

ANALOG ELECTRONIC CIRCUIT DESIGN
23EC2104

Topic:

SMALL-SIGNAL OPERATION AND MODELS

Session - 07

SESSION CONTENT

- Trans-conductance
 - Input Resistance at the Base
 - Input Resistance at the Emitter
 - Voltage Gain
 - Separating the Signal and the DC Quantities
-
- Hybrid- π Model
 - T Model

AIM OF THE SESSION



To understand and analyze the small-signal behavior of Bipolar Junction Transistors (BJTs) using equivalent models for AC signal analysis.

INSTRUCTIONAL OBJECTIVES



The Session is designed to:

1. Define small-signal operation in BJTs and its purpose.
2. Explain the significance of small-signal models in amplifier analysis.
3. Describe the components of Hybrid- π and T-models.


LEARNING OUTCOMES



At the end of this session, learners will be able to:

1. Apply small-signal models for analyzing BJT amplifier circuits.
2. Derive and use small-signal parameters from DC operating points.
3. Choose the appropriate model (Hybrid- π or T-model) for different applications.

Small-Signal Operation and Models

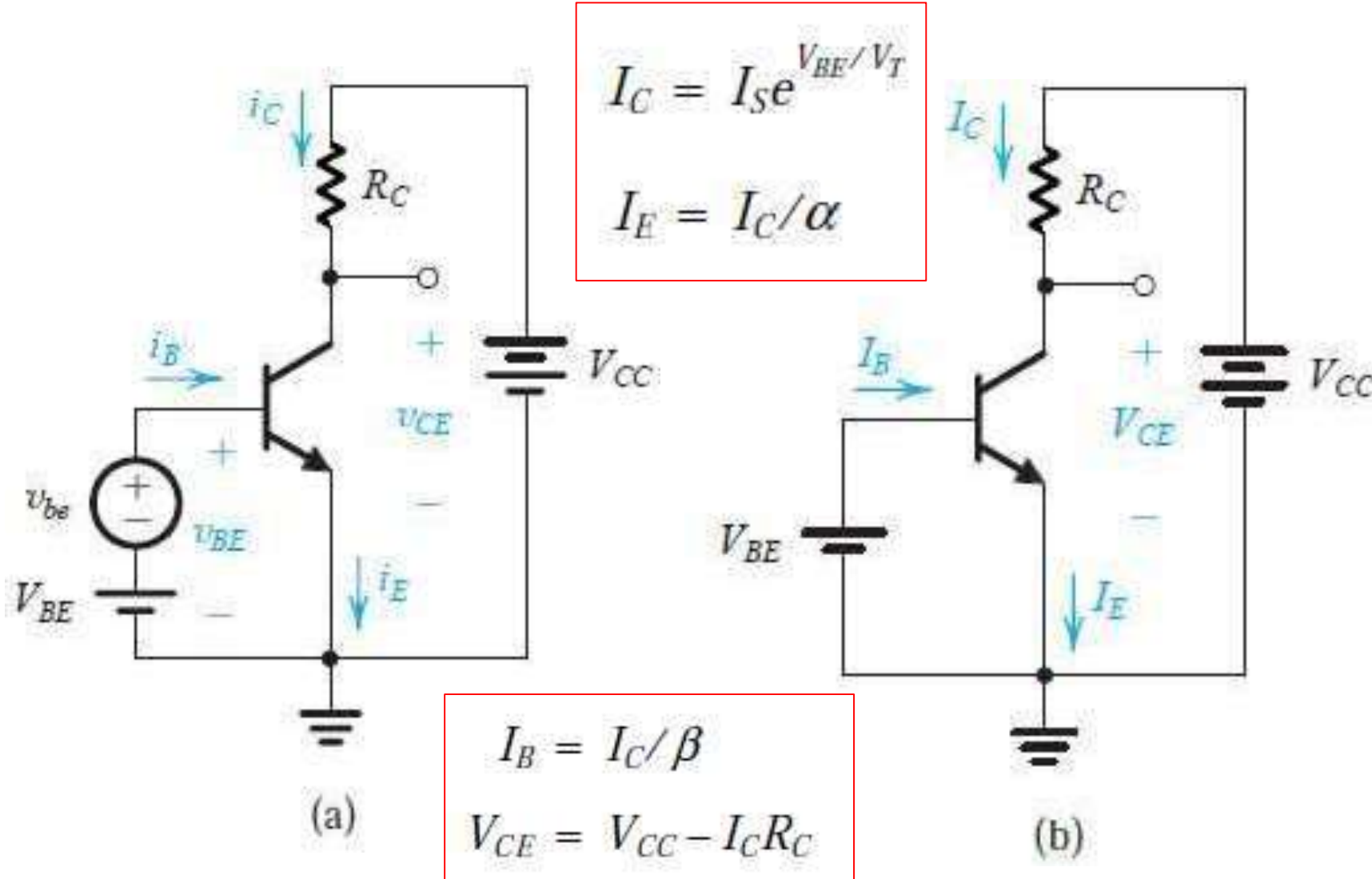

Transconductance

$$v_{BE} = V_{BE} + v_{be} \text{-----(1)}$$

$$i_C = I_S e^{v_{BE}/V_T} = I_S e^{(V_{BE} + v_{be})/V_T} \\ = I_S e^{V_{BE}/V_T} e^{v_{be}/V_T}$$


$$i_C = I_C e^{v_{be}/V_T}$$

----- (2)

If $v_{be} < V_T$,

$$e^{\frac{v_{be}}{V_T}} = 1 + \left(\frac{v_{be}}{V_T}\right) + \frac{\left(\frac{v_{be}}{V_T}\right)^2}{2!} + \frac{\left(\frac{v_{be}}{V_T}\right)^3}{3!} + \dots$$
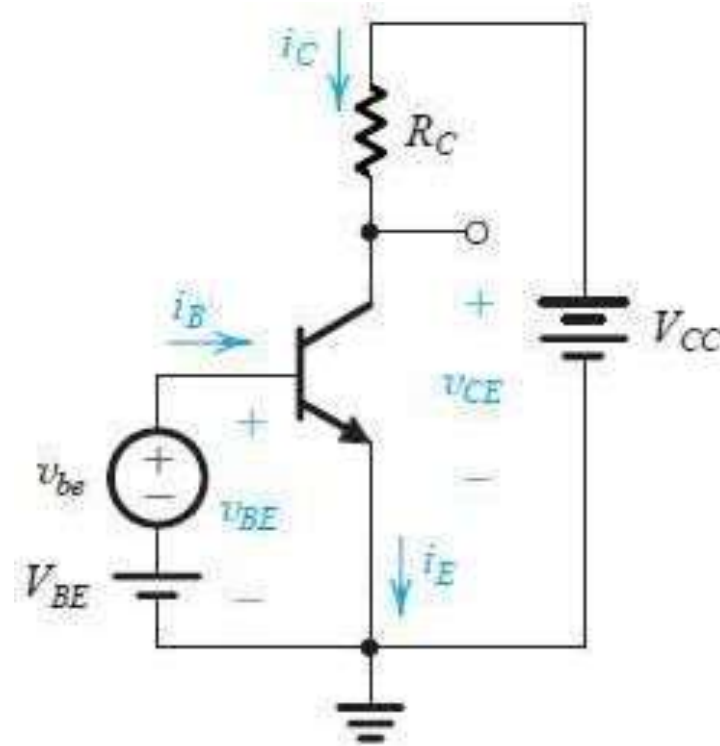
$$e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots + \frac{x^n}{n!} + \dots$$



(a)

$$i_C \approx I_C \left(1 + \frac{v_{be}}{V_T}\right) \text{-----(3)}$$

Transconductance

$$e^{\frac{v_{be}}{V_T}} = 1 + \left(\frac{v_{be}}{V_T}\right) + \frac{\left(\frac{v_{be}}{V_T}\right)^2}{2!} + \frac{\left(\frac{v_{be}}{V_T}\right)^3}{3!} + \dots \quad \text{-----(3)}$$

This approximation, which is valid only for v_{be} less than approximately 10 mV, is referred to as the **small-signal approximation**.

$$i_C \approx I_C \left(1 + \frac{v_{be}}{V_T}\right) \quad \longrightarrow \quad i_C = I_C + \frac{I_C}{V_T} v_{be} \quad \text{-----(4)}$$

Thus the collector current is composed of the dc bias value I_C and a signal component i_c ,

$$i_c = \frac{I_C}{V_T} v_{be}$$

Transconductance

$$i_c = \frac{I_C}{V_T} v_{be}$$


This equation relates the signal current in the collector to the corresponding base-emitter signal voltage. It can be rewritten as

$$i_c = g_m v_{be}$$

$$g_m = \frac{I_C}{V_T}$$

$$g_m = \left. \frac{\partial i_C}{\partial v_{BE}} \right|_{I_C=I_C}$$

Transconductance

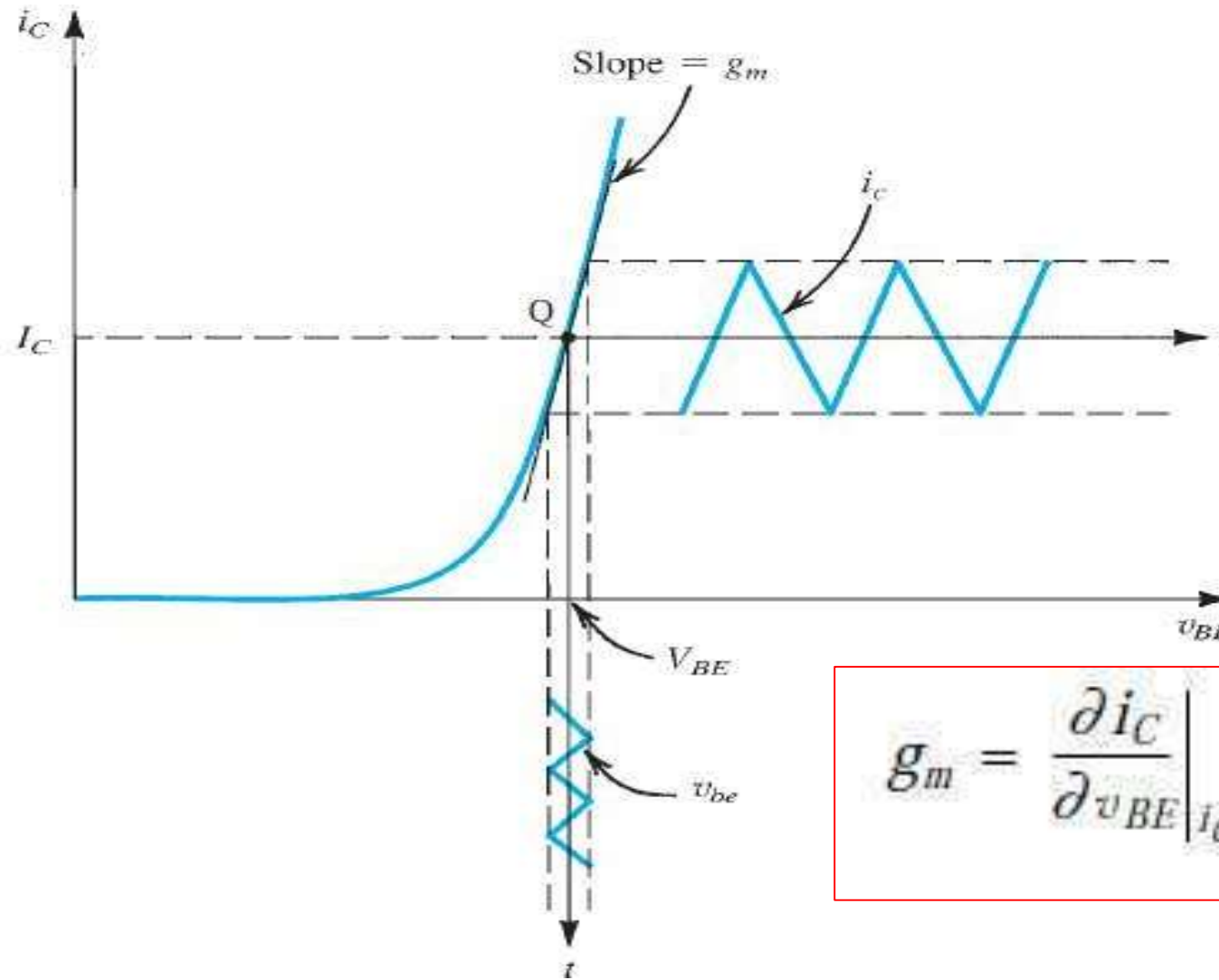

$$g_m = \left. \frac{\partial i_C}{\partial v_{BE}} \right|_{I_C = I_C}$$

Input Resistance at the Base

$$i_B = \frac{i_C}{\beta} = \frac{I_C}{\beta} + \frac{1}{\beta} \frac{I_C}{V_T} v_{be}$$

Thus,

$$i_B = I_B + i_b$$

where I_B is equal I_C/β to and the signal component i_b is given by

$$i_b = \frac{1}{\beta} \frac{I_C}{V_T} v_{be}$$

Substituting for I_C/V_T by g_m gives

$$i_b = \frac{g_m}{\beta} v_{be}$$

The small-signal input resistance between base and emitter, *looking into the base*, is denoted by r_π and is defined as

$$r_\pi \equiv \frac{v_{be}}{i_b}$$

$$r_\pi = \frac{\beta}{g_m}$$

Substitute g_m and Replace I_C/β by I_B

$$r_\pi = \frac{V_T}{I_B}$$

Input Resistance at the Emitter

$$i_E = \frac{i_C}{\alpha} = \frac{I_C}{\alpha} + \frac{i_c}{\alpha}$$

Thus,

$$i_E = I_E + i_e$$

where I_E is equal to I_C / α and the signal current i_e is given by

$$i_e = \frac{i_c}{\alpha} = \frac{I_C}{\alpha V_T} v_{be} = \frac{I_E}{V_T} v_{be}$$

If we denote the **small-signal resistance** between **base** and **emitter** looking into the emitter by **r_e** , it can be defined as

$$r_e \equiv \frac{v_{be}}{i_e}$$

$$r_e = \frac{V_T}{I_E}$$

$$r_e = \frac{\alpha}{g_m} \simeq \frac{1}{g_m}$$

Input Resistance at the Emitter

The relationship between r_π and r_e can be found by combining their respective definitions


$$v_{be} = i_b r_\pi = i_e r_e$$

Thus,

$$r_\pi = (i_e / i_b) r_e$$

which yields

$$r_\pi = (\beta + 1) r_e$$

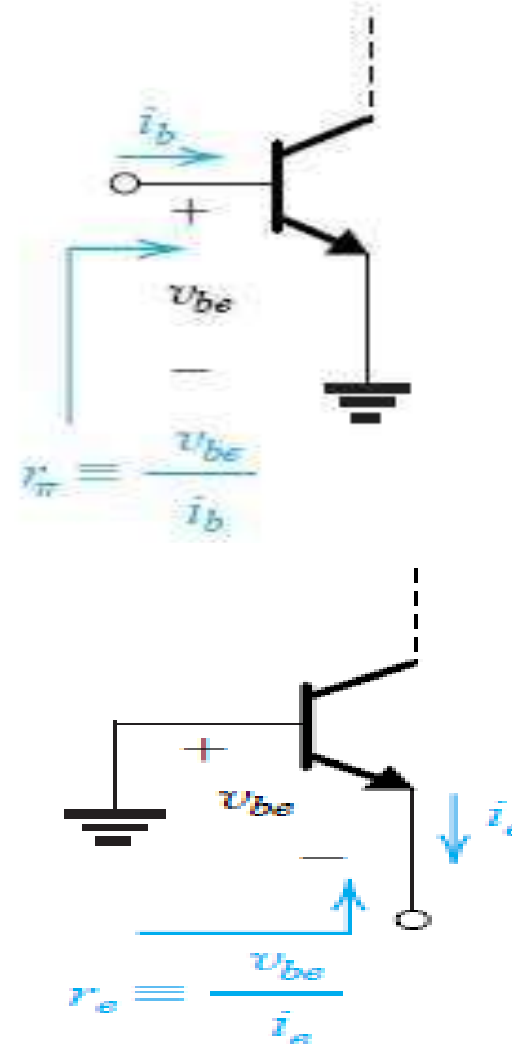

Voltage Gain

$$\begin{aligned}v_{CE} &= V_{CC} - i_c R_C \\&= V_{CC} - (I_C + i_c) R_C \\&= (V_{CC} - I_C R_C) - i_c R_C \\&= V_{CE} - i_c R_C\end{aligned}$$

Here the quantity V_{CE} is the dc bias voltage at the collector, and the signal voltage is given by

$$v_{ce} = -i_c R_C = -g_m v_{be} R_C$$

$$= (-g_m R_C) v_{be}$$

Thus the voltage gain of this amplifier A_v is

$$A_v \equiv \frac{v_{ce}}{v_{be}} = -g_m R_C$$

$$A_v = -\frac{I_C R_C}{V_T}$$

Small Signal Operation

Transconductance

$$g_m = \frac{I_C}{V_T}$$

$$g_m = \frac{i_c}{V_{be}}$$

$$g_m = \left. \frac{\partial i_C}{\partial v_{BE}} \right|_{I_C=I_C}$$

Input Resistance
at the Base

$$i_B = I_B + i_b$$

$$r_\pi = \frac{V_T}{I_B}$$

$$r_\pi = \frac{\beta}{g_m}$$

Input Resistance
at the Emitter

$$i_E = I_E + i_e$$

$$r_e = \frac{V_T}{I_E}$$

$$r_e = \frac{\alpha}{g_m} \simeq \frac{1}{g_m}$$


Voltage Gain

$$A_v \equiv \frac{v_{ce}}{v_{be}} = -g_m R_C$$

$$A_v = -\frac{I_C R_C}{V_T}$$

$$r_\pi = (\beta + 1)r_e$$

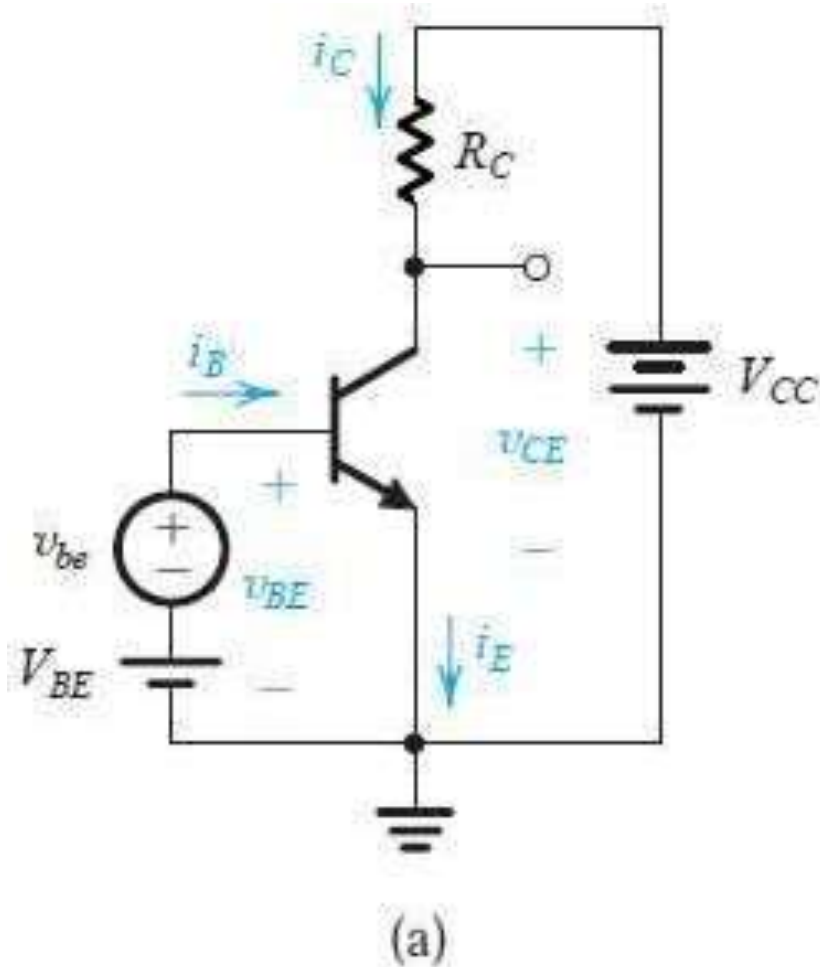
Separating the Signal and the DC Quantities



❖ Every current and voltage in the amplifier circuit of Fig.(a) is composed of two components: a dc component and a signal component

❖ For instance, $v_{BE} = V_{BE} + v_{be}$, $i_C = I_C + i_c$, and so on

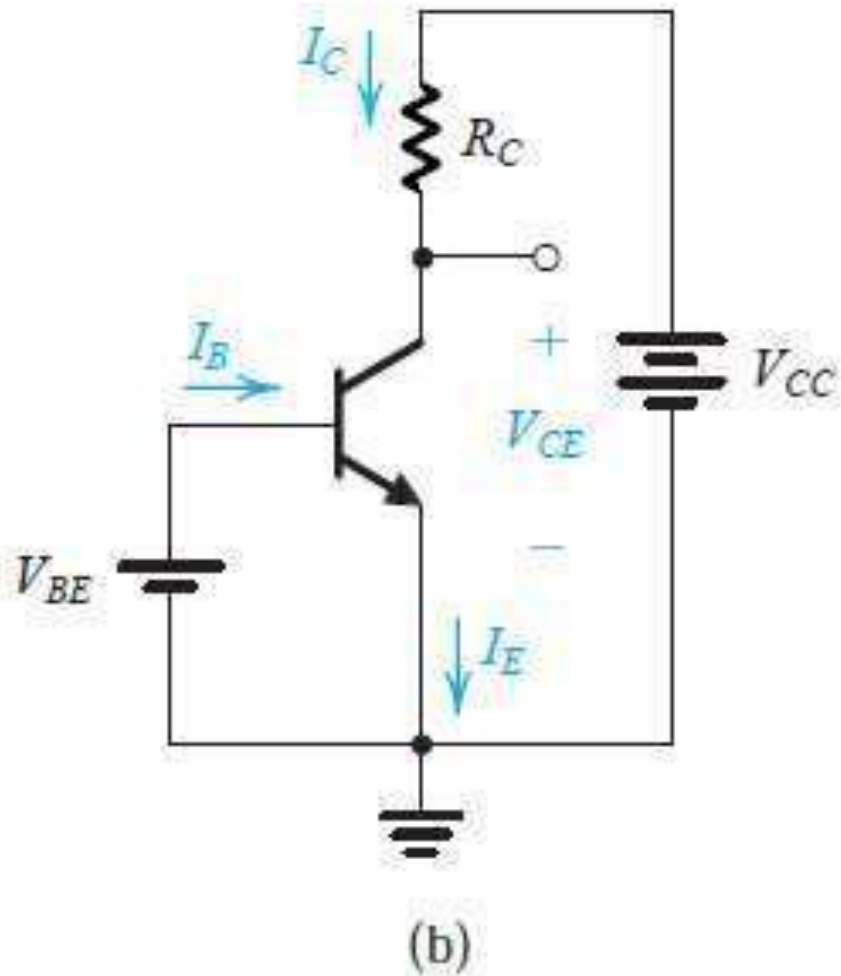Separating the Signal and the DC Quantities



The dc components are determined from the dc circuit given in Fig. 6.36(b) and from the relationships imposed by the transistor.


$$I_C = I_S e^{V_{BE}/V_T}$$

$$I_E = I_C / \alpha$$

$$I_B = I_C / \beta$$

$$V_{CE} = V_{CC} - I_C R_C$$

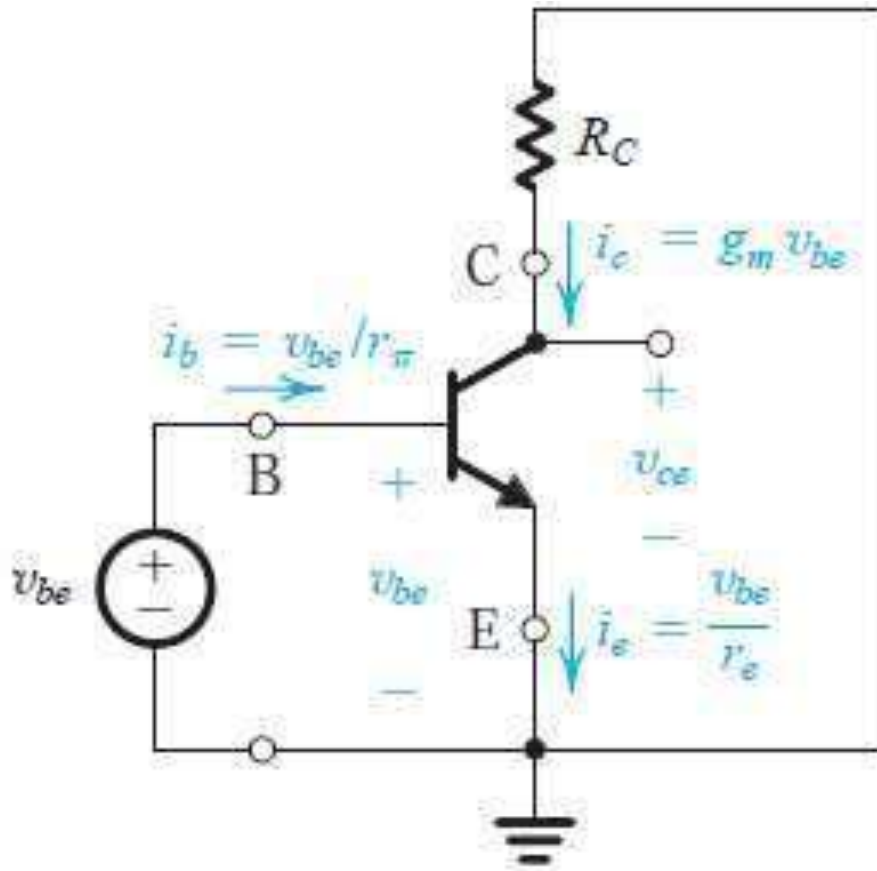Separating the Signal and the DC Quantities




❖ On the other hand, a representation of the signal operation of the BJT can be obtained by eliminating the dc sources, as shown in Fig.

❖ Expressions for the current elements (*ic, ib, and ie*) obtained when a **small signal vbe** is applied.


❖ Small-Signal Circuit Model.

HYBRID π MODEL

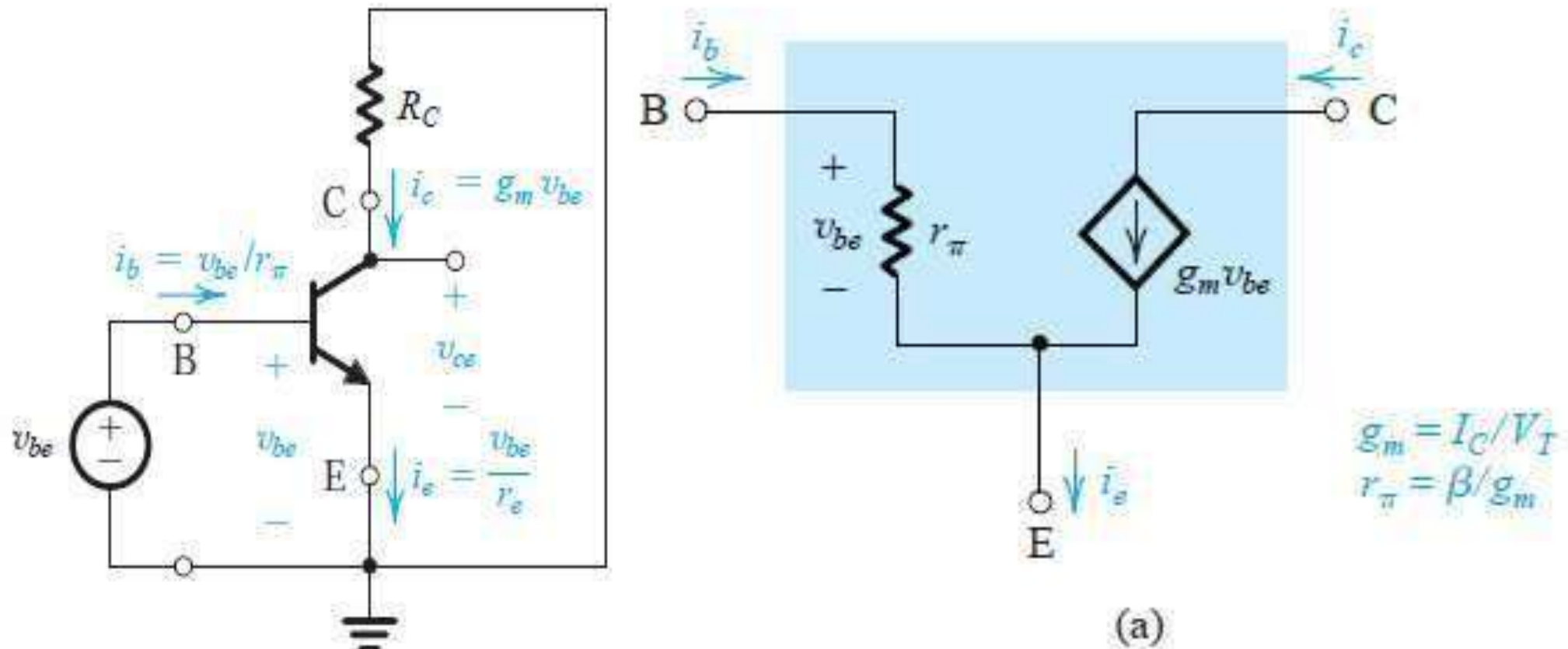

This model represents the BJT as a **voltage controlled current source** and explicitly includes the input resistance looking into the base, r_π

HYBRID π MODEL

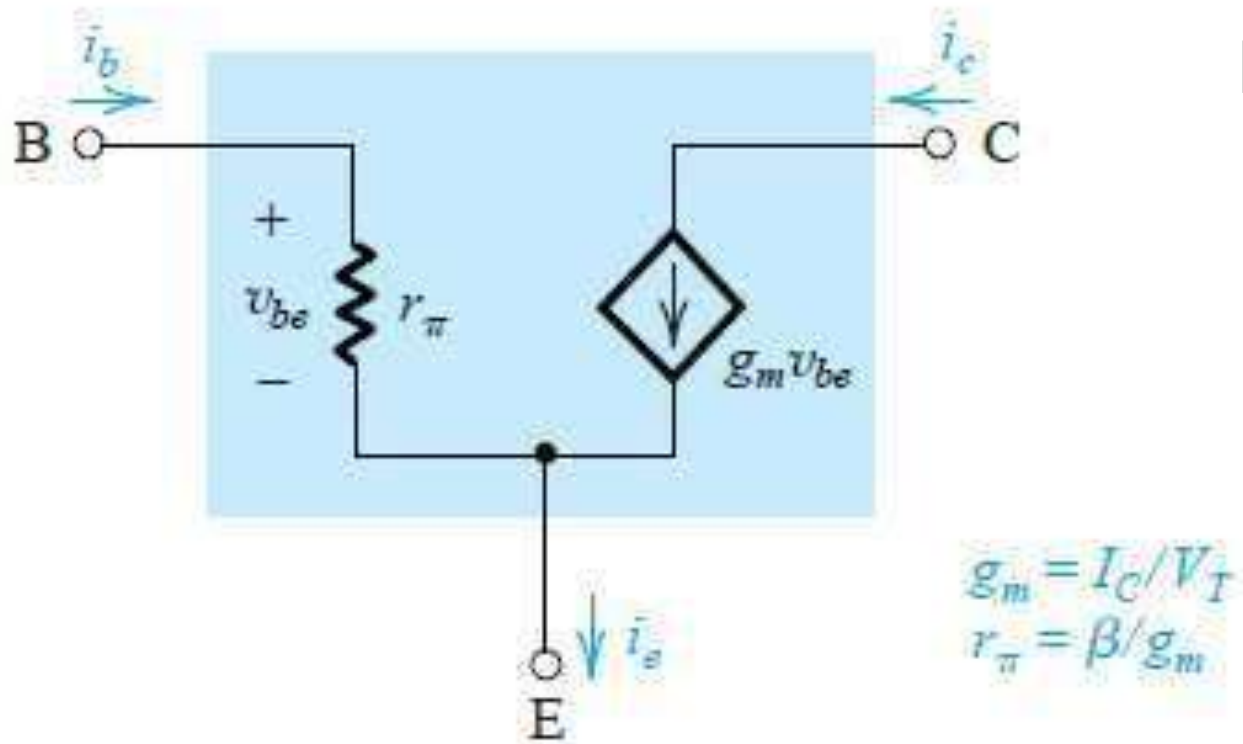

(a)

In this model


$$i_c = g_m v_{be}$$
$$i_b = \frac{v_{be}}{r_{\pi}}$$

$$g_m = I_C / V_T$$
$$r_{\pi} = \beta / g_m$$

HYBRID π MODEL

In this model

$$i_e = i_c + i_b$$

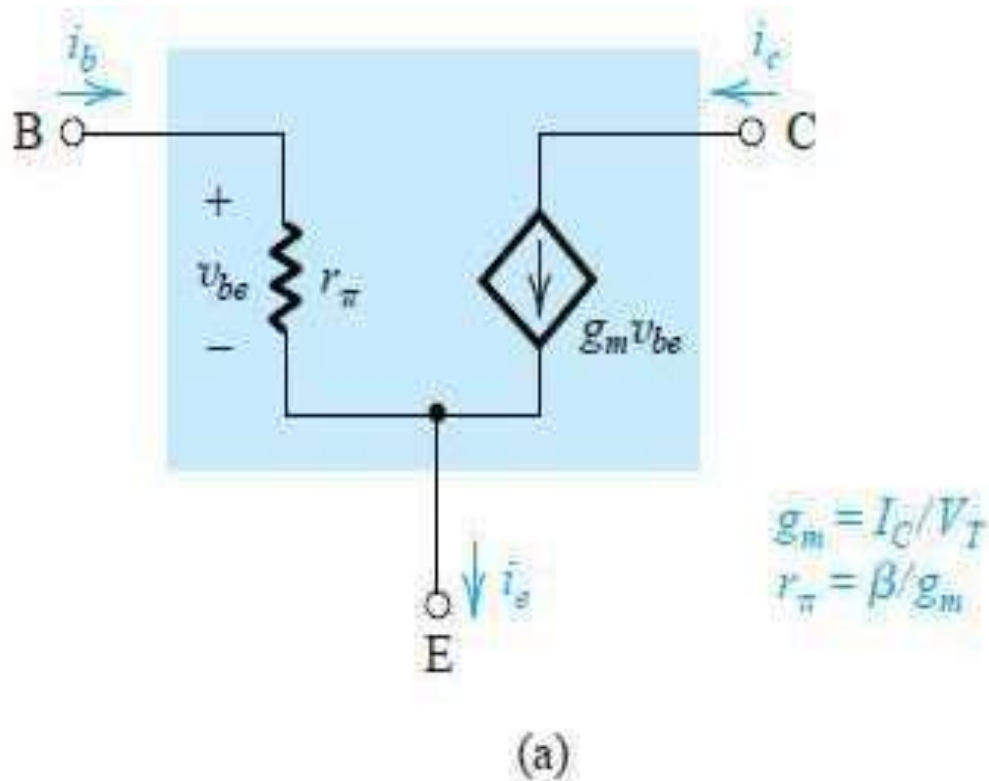

$$i_e = \frac{v_{be}}{r_\pi} + g_m v_{be} = \frac{v_{be}}{r_\pi} (1 + g_m r_\pi)$$

But $g_m r_\pi = \beta$,

$$= \frac{v_{be}}{r_\pi} (1 + \beta) = v_{be} / \left(\frac{r_\pi}{1 + \beta} \right)$$


$$= v_{be} / r_e$$

HYBRID π MODEL

Slightly different model can be obtained by expressing the **current of the controlled source** ($g_m v_{be}$) *in terms of base current i_b*


$$\begin{aligned} g_m v_{be} &= g_m (i_b r_\pi) \\ &= (g_m r_\pi) i_b = \beta i_b \end{aligned}$$

Equivalent circuit model is

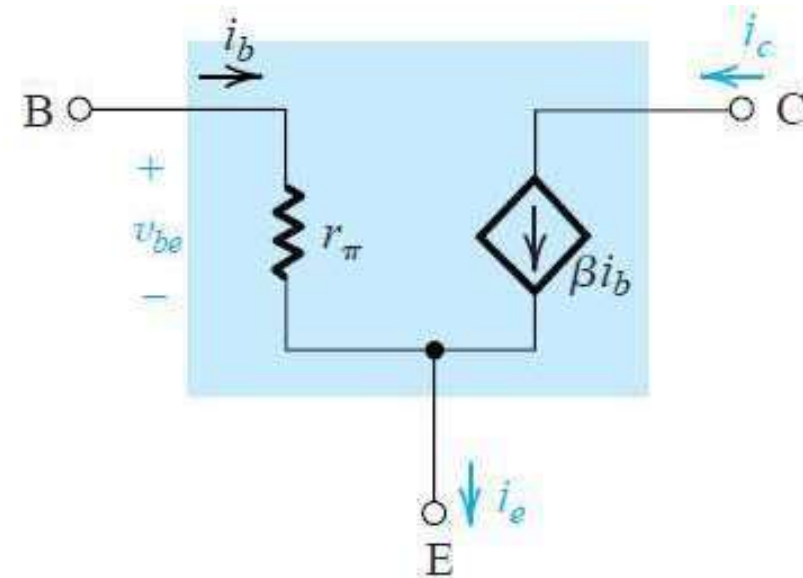

Here the transistor is represented as a **current-controlled current source**, with the control current being **i_b** .

HYBRID π MODEL

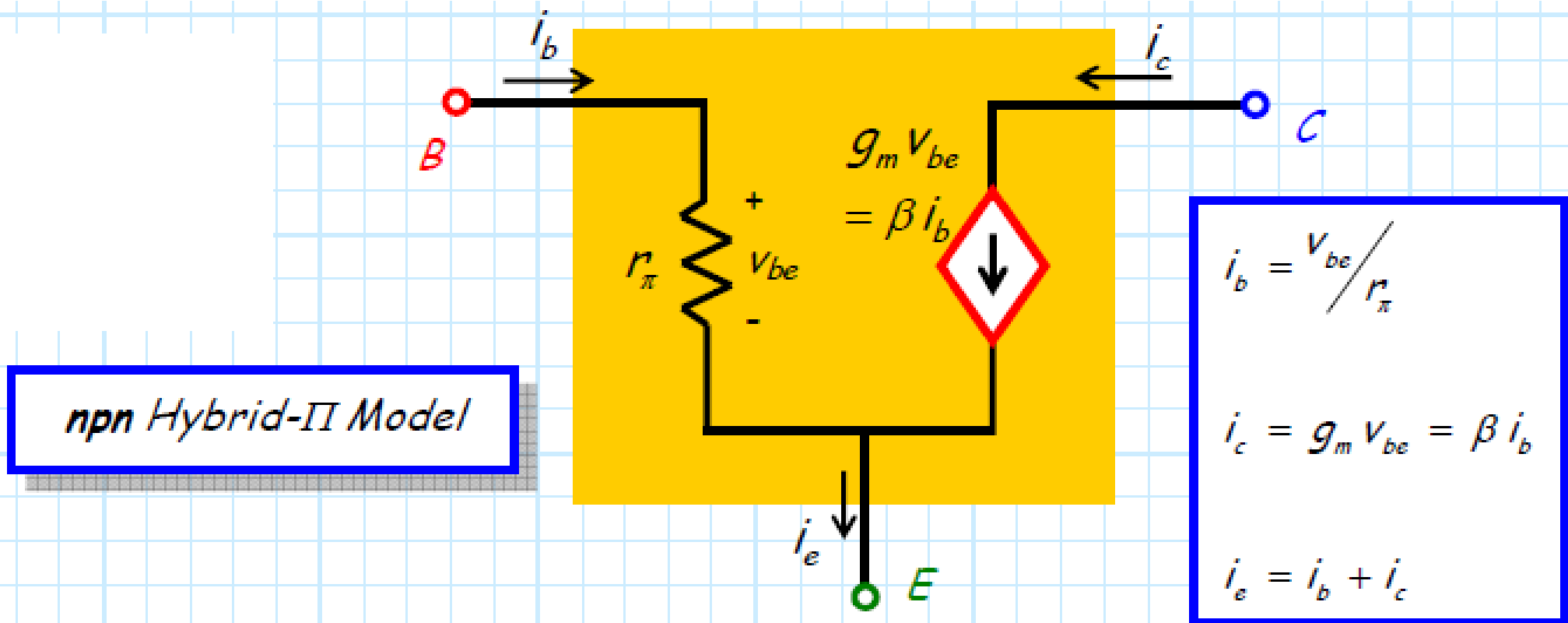


HYBRID π MODEL

$$i_b = v_{eb} / r_\pi$$


$$i_c = g_m v_{eb} = \beta i_b$$

$$i_e = i_b + i_c$$

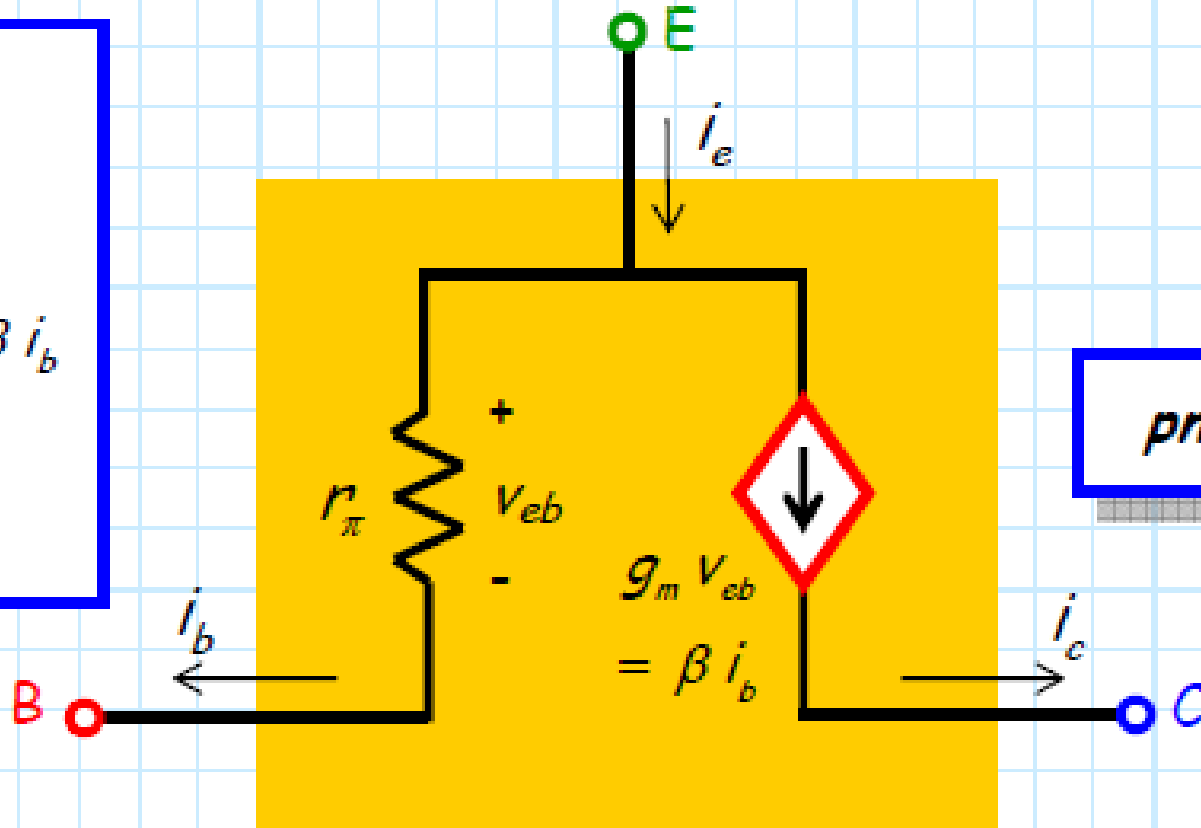

pnp Hybrid- Π Model

npn T-Model

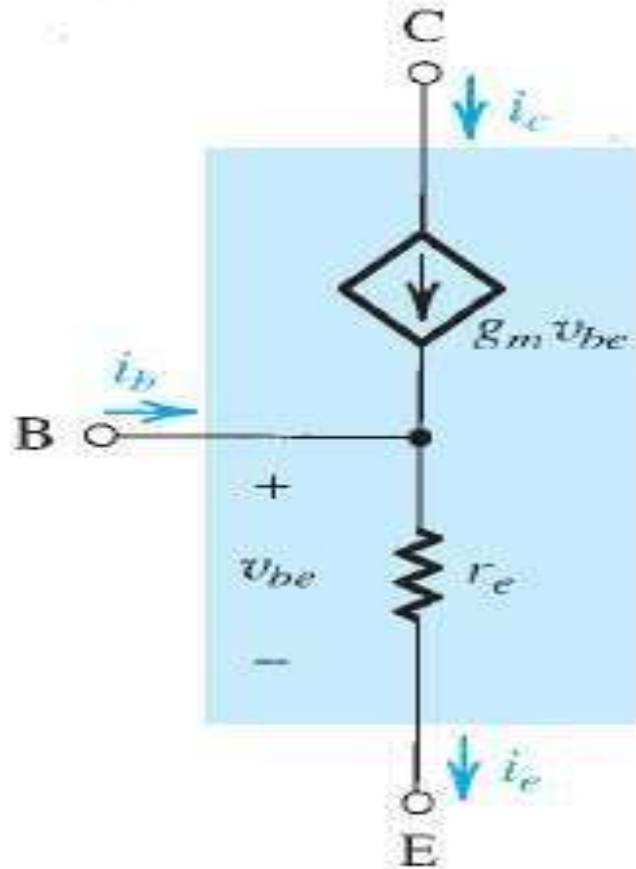

(a)

T Model

$$i_e = i_c + i_b$$


$$i_b = i_e - i_c$$

$$\begin{aligned} i_b &= \frac{v_{be}}{r_e} - g_m v_{be} = \frac{v_{be}}{r_e} (1 - g_m r_e) \\ &= \frac{v_{be}}{r_e} (1 - \alpha) = \frac{v_{be}}{r_e} \left(1 - \frac{\beta}{\beta + 1}\right) \\ &= \frac{v_{be}}{(\beta + 1)r_e} = \frac{v_{be}}{r_\pi} \end{aligned}$$

The current of the controlled source can be expressed in terms of the emitter current.

$$\begin{aligned} g_m v_{be} &= g_m (i_e r_e) \\ &= (g_m r_e) i_e = \alpha i_e \end{aligned}$$

npn T-Model

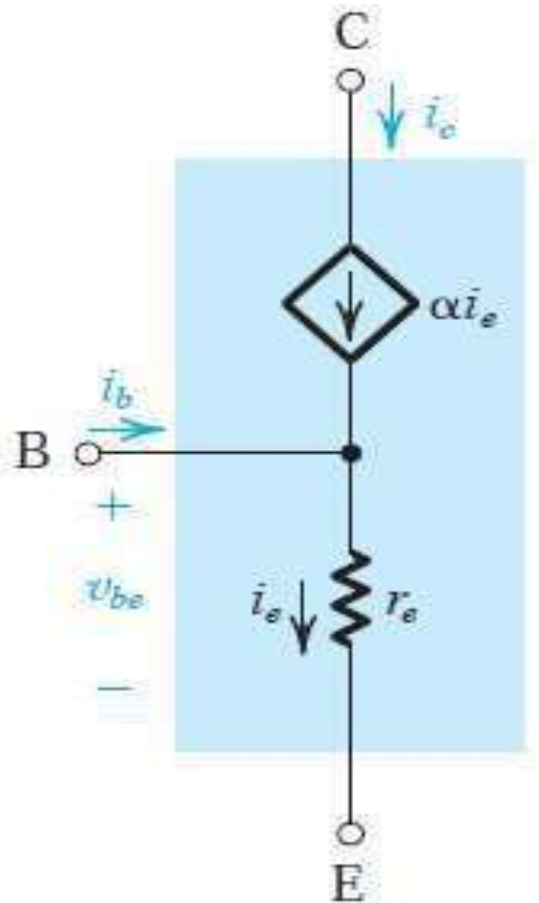

T Model



$$\begin{aligned} i_b &= \frac{v_{be}}{r_e} - g_m v_{be} = \frac{v_{be}}{r_e} (1 - g_m r_e) \\ &= \frac{v_{be}}{r_e} (1 - \alpha) = \frac{v_{be}}{r_e} \left(1 - \frac{\beta}{\beta + 1}\right) \\ &= \frac{v_{be}}{(\beta + 1)r_e} = \frac{v_{be}}{r_\pi} \end{aligned}$$

The current of the controlled source can be expressed in terms of the emitter current.

$$\begin{aligned} g_m v_{be} &= g_m (i_e r_e) \\ &= (g_m r_e) i_e = \alpha i_e \end{aligned}$$

npn T-Model

T Model

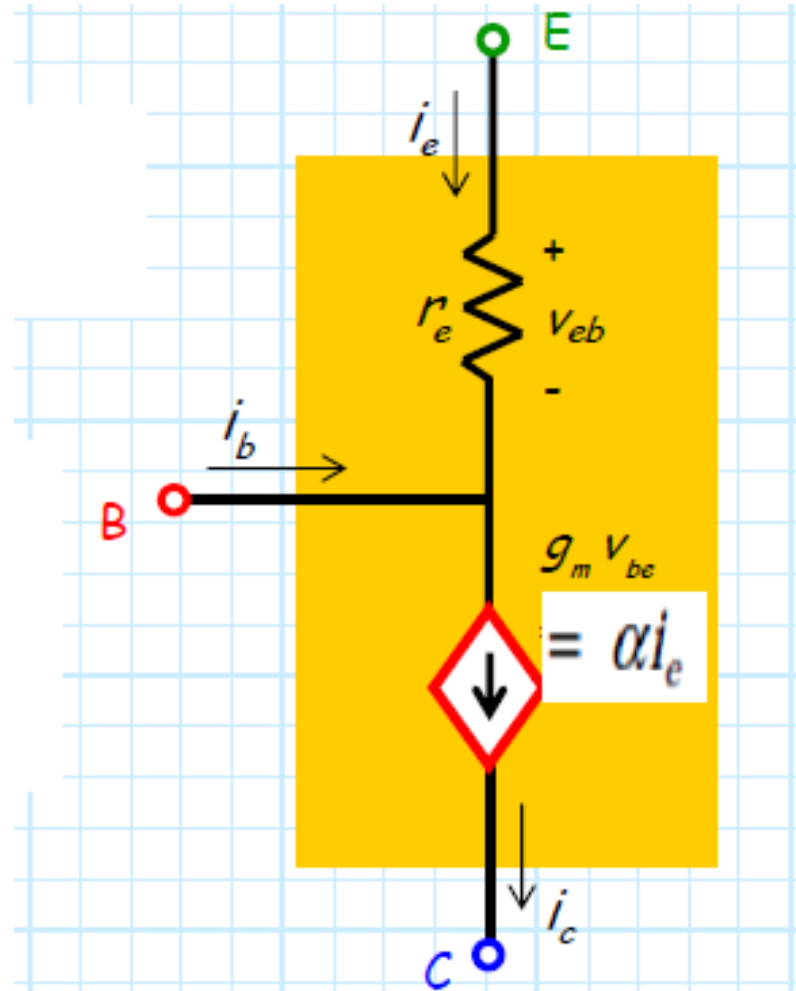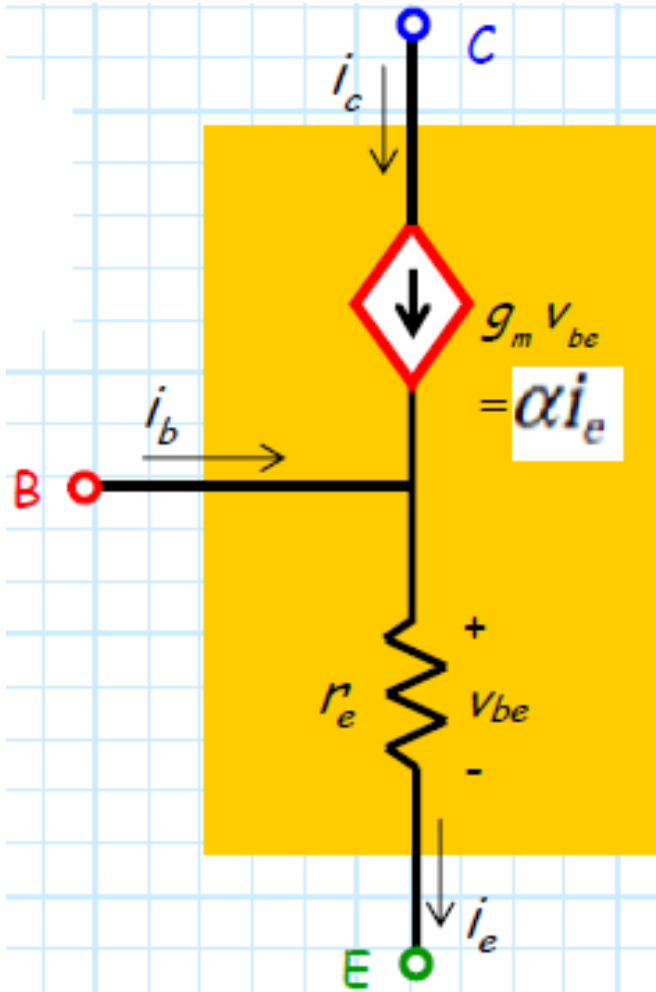

APPLICATION OF THE SMALL SIGNAL EQUIVALENT CIRCUIT

1. Eliminate the signal source and determine the dc operating point of the BJT and in particular the dc collector current I_C .

$$I_C, I_B, I_E \text{ and } V_C$$

2. Calculate the values of the small-signal model parameters:

$$g_m = \frac{I_C}{V_T} \quad r_\pi = \frac{V_T}{I_B} \quad r_\pi = \frac{\beta}{g_m} \quad r_e = \frac{\alpha}{g_m} \simeq \frac{1}{g_m} \quad r_e = \frac{V_T}{I_E}$$

3. Eliminate the dc sources by replacing each dc voltage source with a short circuit and each dc current source with an open circuit.

APPLICATION OF THE SMALL SIGNAL EQUIVALENT CIRCUIT

4. Replace the BJT with one of its small-signal equivalent circuit models. Although any one of the models can be used, one might be more convenient than the others for the particular circuit being analyzed.

➤ Hybrid- π Model

➤ T Model

➤ Hybrid Model

5. Analyze the resulting circuit to determine the required quantities (e.g., voltage gain, input and output resistance).

$$A_v = \frac{v_o}{v_i}$$

$$R_o \text{ and } R_i$$