

**AY-2025-2026**  
**ODD SEM**

**Department of ECE**

**ANALOG ELECTRONIC CIRCUIT DESIGN**  
**23EC2104**

Topic:

**STABILITY FACTOR OF BJT BIAS**

**Session - 06**

# SESSION CONTENT

---

- Stability Factor
- Stability Factor for Fixed Bias
- Stability Factor for Collector Feedback Bias
- Stability Factor for Voltage Divider Bias

## AIM OF THE SESSION



To compare stability of various biasing circuits for BJT

## INSTRUCTIONAL OBJECTIVES

This Session is designed to:

1. Demonstrate stability factor
2. Compare stability of various biasing circuits



## LEARNING OUTCOMES

At the end of this session, you should be able to:

1. Derive stability factor for BJT
2. Select biasing circuit based on stability factor



# REVISIT BIASING OF BJT

---

- Biasing refers to the application of D.C. voltages to setup the operating point in such a way that output signal is undistorted throughout the whole operation.
- Also once selected properly, the Q point should not shift because of change of  $I_C$  due to
  - (i)  $\beta$  variation due to replacement of the transistor of same type
  - (ii) Temperature variation

## Stabilization

- The process of making operating point independent of temperature changes or variation in transistor parameters is known as stabilization.
- Stabilization of operating point is necessary due to
  - ❖ Temperature dependence of  $I_C$
  - ❖ Individual variations
  - ❖ Thermal runaway

# STABILIZATION

## Temperature dependence of $I_C$ & Thermal runaway

$$I_C = \beta I_B + (\beta + 1) I_{CBO}$$

- $I_{CBO}$  is strong function of temperature. A rise of  $10^\circ\text{C}$  doubles the  $I_{CBO}$  and  $I_C$  will increase  $(\beta + 1)$  times of  $I_{CBO}$
- The flow of  $I_C$  produce heat within the transistor and raises the transistor temperature further and therefore, further increase in  $I_{CBO}$
- This effect is cumulative and in few seconds, the  $I_C$  may become large enough to burn out the transistor.
- The self destruction of an unstablized transistor is known as thermal runaway.

## Stability Factor

- The rate of change collector current  $I_C$  with respect to the collector leakage current  $I_{CBO}$  is called stability factor, denoted by  $S$ .

$$S = \left( \frac{dI_C}{dI_{CBO}} \right) \quad \text{Lower the value of } S, \text{ better is the stability of the transistor.}$$

# STABILITY FACTOR

$$I_C = \beta I_B + (\beta + 1)I_{CBO} \quad (1)$$

Differentiating equation (1) w.r.t  $I_C$

$$1 = \left( \frac{dI_B}{dI_C} \right) + (\beta + 1) \frac{dI_{CBO}}{dI_C}$$

$$1 = \left( \frac{dI_B}{dI_C} \right) + \frac{(\beta + 1)}{S}$$

$$S = \frac{(\beta + 1)}{1 - \left( \frac{dI_B}{dI_C} \right)}$$

➤ The rate of change collector current  $I_C$  with respect to the collector leakage current  $I_{CBO}$  at constant  $\beta$  and  $I_B$  is called stability factor, denoted by  $S$ .

## Different biasing schemes

- (i) Fixed bias (base resistor biasing)
- (ii) Collector Feedback bias
- (iii) Voltage divider bias

# STABILITY FACTOR FOR FIXED BIAS

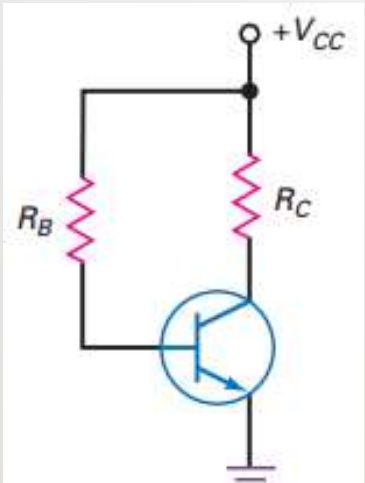


Fig. 6.1. Fixed Bias

Using KVL in the base-emitter loop

$$V_{CC} - I_B R_B - V_{BE} = 0 ; I_B = (V_{CC} - V_{BE}) / R_B$$

$$I_C = \beta I_B = \beta (V_{CC} - V_{BE}) / R_B$$

Using KVL in the collector-emitter loop

$$V_{CC} - I_C R_C - V_{CE} = 0 ; V_{CE} = V_{CC} - I_C R_C$$

$Q(V_{CE}, I_C)$  is set

# STABILITY FACTOR FOR FIXED BIAS

---

## Advantages:

- Operating point can be shifted easily anywhere in the active region by merely changing the base resistor ( $R_B$ ).
- A very small number of components are required.

## Disadvantages:

- Poor stabilization
- High stability factor ( $S = \beta + 1$  because  $I_B$  is constant so  $dI_B/dI_C = 0$ ), hence prone to thermal runaway

## Usage:

- Due to the above inherent drawbacks, fixed bias is rarely used in linear circuits (i.e., those circuits which use the transistor as a current source). Instead, it is often used in circuits where transistor is used as a switch.

How the Q point is affected by changes in  $V_{BE}$  and  $I_{CBO}$  in fixed bias?

$$I_B = (V_{CC} - V_{BE})/R_B \quad I_C = \beta I_B$$



# STABILITY FACTOR FOR COLLECTOR FEEDBACK BIAS

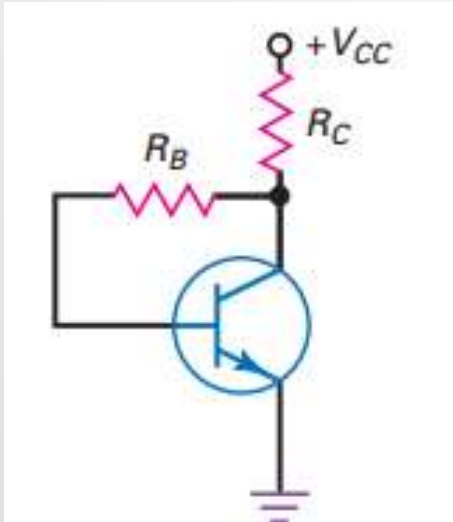


Fig. 5.2. Collector Feedback Bias

$$V_{CC} = (I_C + I_B)R_C + V_{CE} \quad (1)$$

$$V_{CE} = I_B R_B + V_{BE} \quad (2)$$

Since,  $I_C = \beta I_B$  so from equation (1) & (2)

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta) R_C}$$

**$Q(V_{CE}, I_C)$  is set**

# STABILITY FACTOR FOR COLLECTOR FEEDBACK BIAS

## Advantages:

- Better stabilization compared to fixed bias

## Disadvantages:

- This circuit provides negative feedback which reduces the gain of the amplifier.

## Usage:

- The feedback also decreases the input impedance of the amplifier as seen from the base, which can be advantageous. Due to the gain reduction from feedback, this biasing form is used only when the trade-off for stability is warranted.

## How the bias stability is improved in collector base bias?

If  $I_C$  becomes larger than design value, it causes an increase voltage drop across  $R_C$  hence smaller value of  $V_{CE}$  which in turn causes  $I_B$  to be smaller than its design value. Since  $I_C = \beta I_B$  thus  $I_C$  will also tend to be reduced towards its original value.

For bias Stabilization :  $R_B \ll \beta R_C$

$$I_C = \beta \left[ \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta) R_C} \right]$$

If  $R_B \ll \beta R_C$

$$I_C = \frac{V_{CC} - V_{BE}}{R_C}$$

# STABILITY FACTOR FOR VOLTAGE DIVIDER BIAS

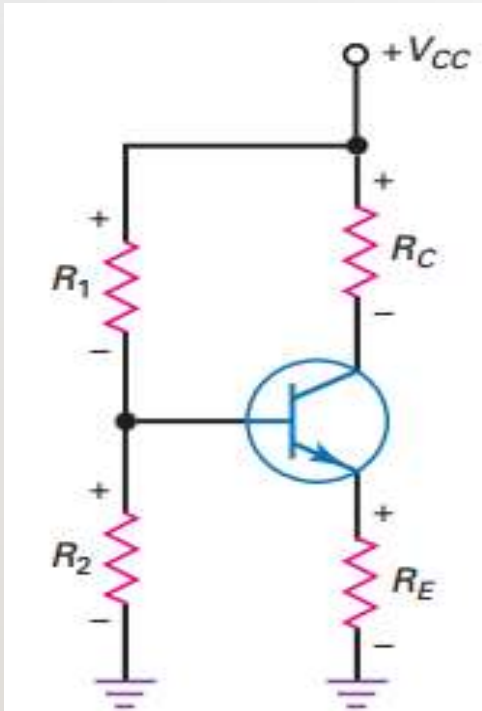


Fig. 6.3. Voltage divider bias for BJT

$$V_{Th} = I_B R_{Th} - V_{BE} - (I_B + I_C) R_E$$

$$0 = R_{Th} \left( \frac{dI_B}{dI_C} \right) + (1 + \frac{dI_B}{dI_C}) R_E$$

$$\frac{dI_B}{dI_C} = - \frac{R_E}{R_{Th} + R_E}$$


$$S = (\beta + 1) \frac{(R_{Th} + R_E)}{R_E (\beta + 1) + R_{Th}}$$

$$S = (\beta + 1) \frac{(1 + \frac{R_{Th}}{R_E})}{(\beta + 1) + \frac{R_{Th}}{R_E}}$$

➤ For stability, S should be small which can be achieved by making  $R_{Th}/R_E$  small. For very small  $R_{Th}/R_E$ ;  $S = 1$  (ideal case)


➤ For very small  $R_{Th}/R_E$ :  $R_2 \downarrow \longrightarrow R_{Th}$  current drawn by  $R_2$  will be large.  
 $R_E \uparrow \longrightarrow$  Large  $V_{CC}$  required. Hence compromise is made in selection.
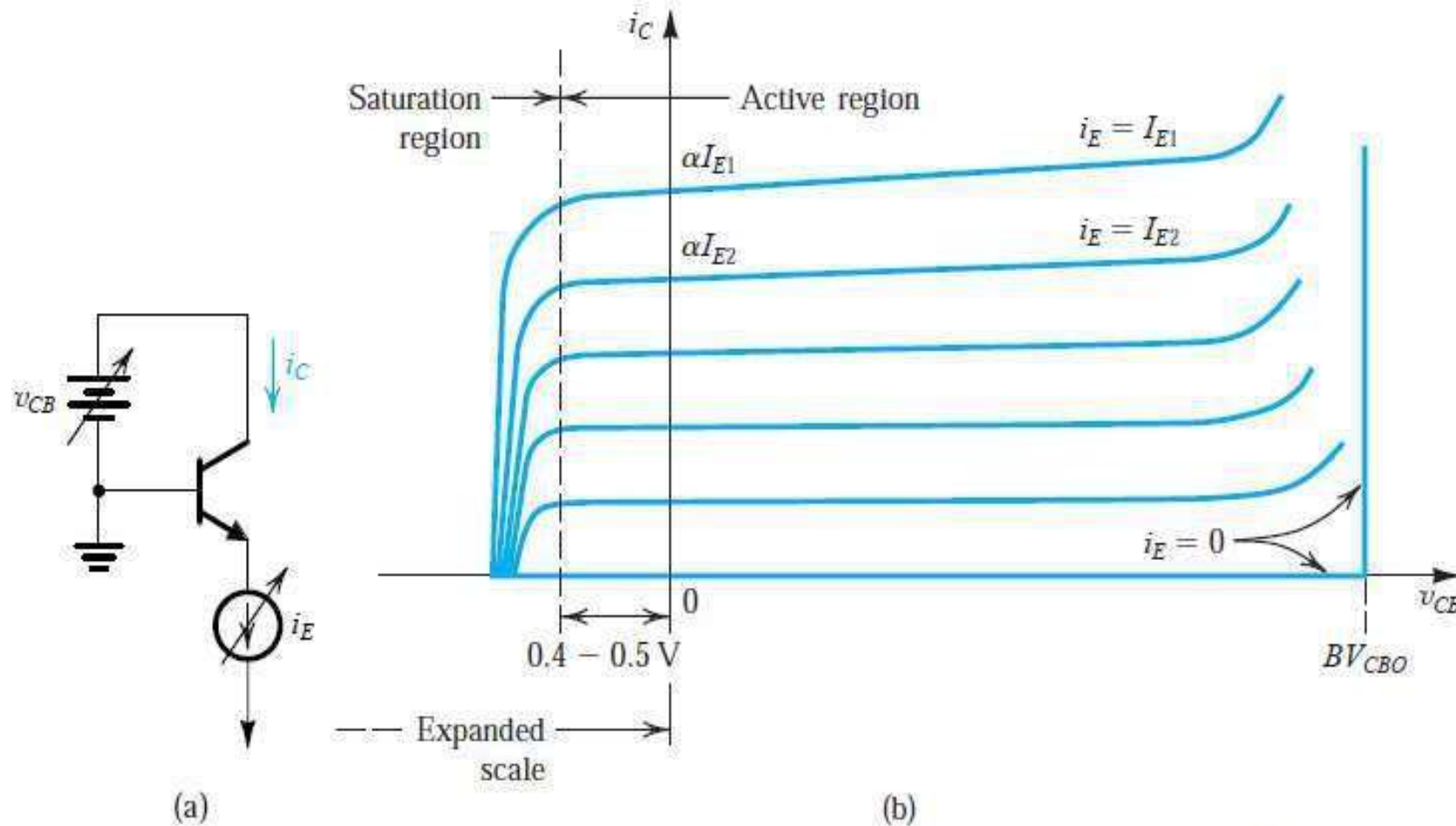
# Transistor Breakdown and Temperature Effects




The BJT common-base characteristics including the transistor breakdown region.
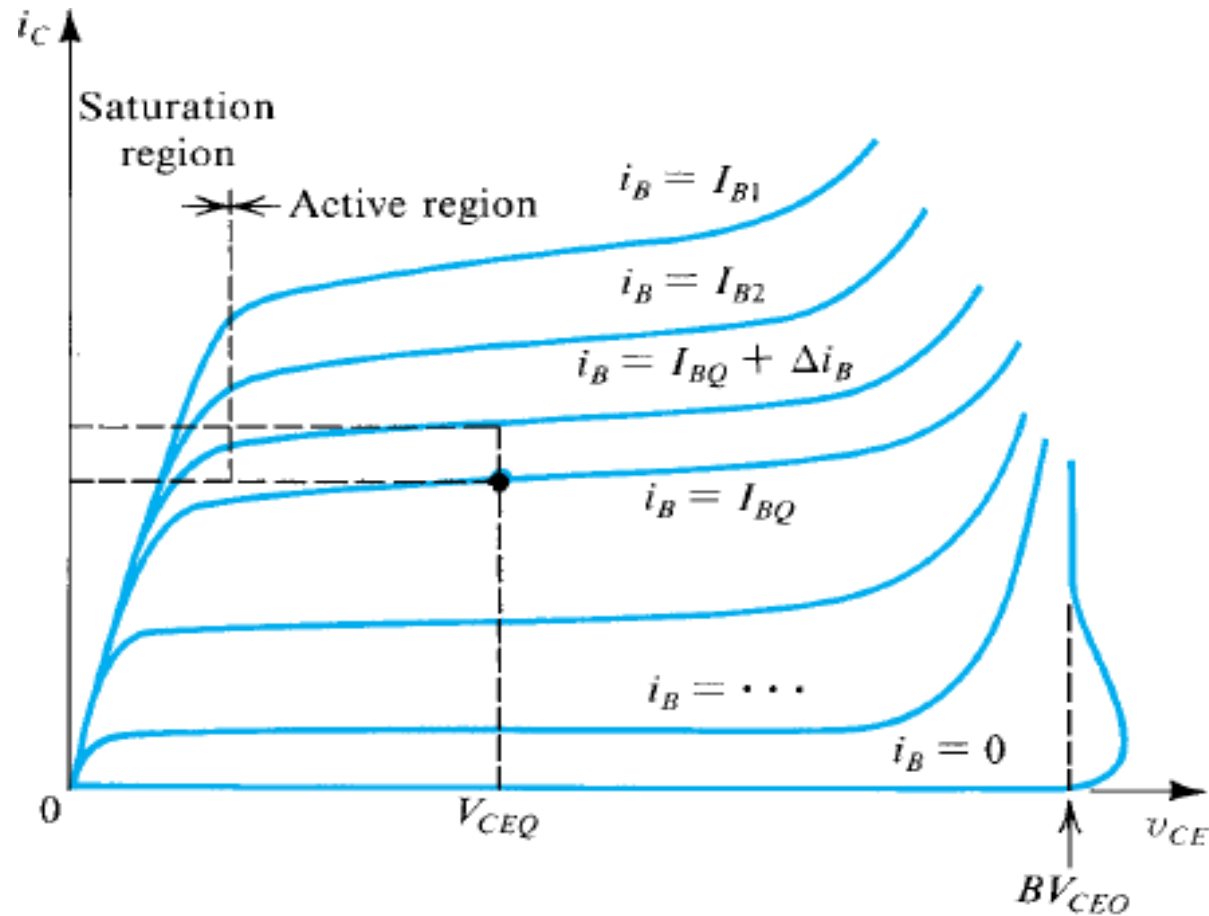
# Transistor Breakdown and Temperature Effects



The BJT common-emitter characteristics including the breakdown region.
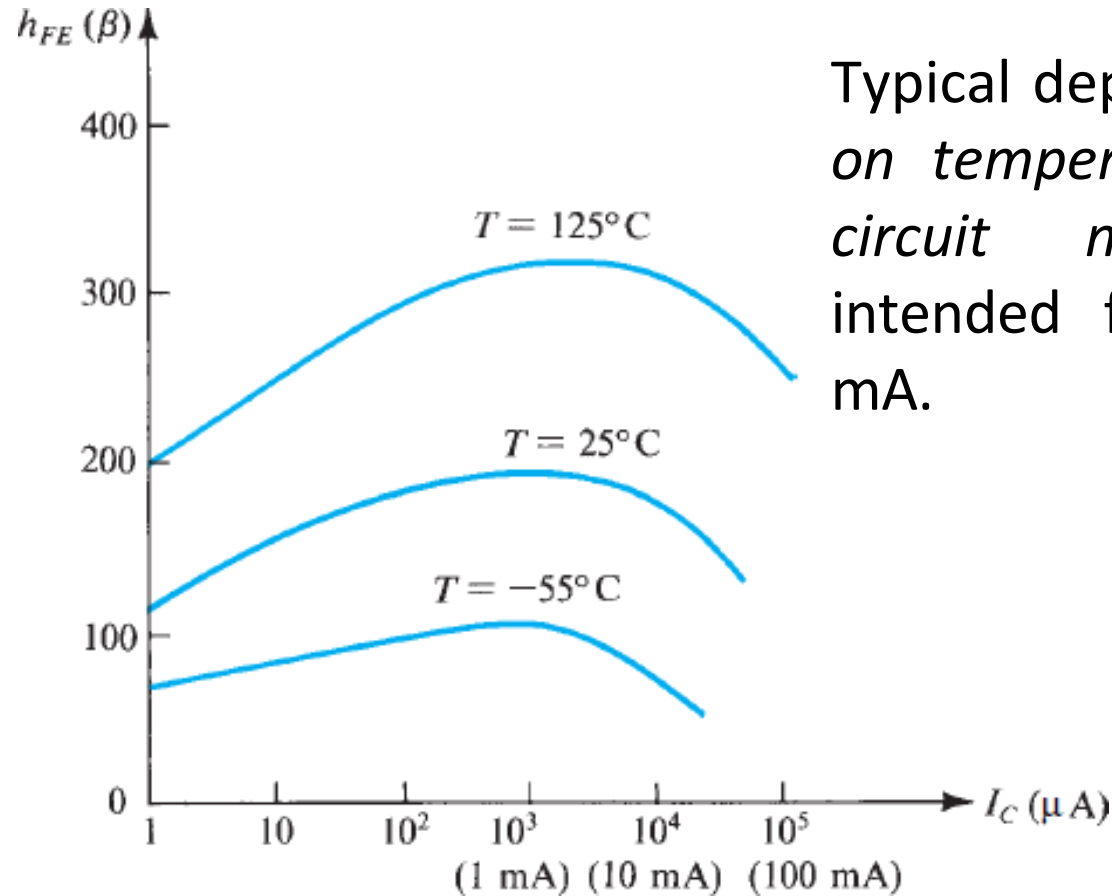
# Transistor Breakdown and Temperature Effects



Typical dependence of  $\beta$  on  $I_C$  and on temperature in an integrated-circuit npn silicon transistor intended for operation around 1 mA.

6.1. Compare the stability factors for fixed bias, collector feedback bias and voltage divider bias for BJT

Solution:

$S = 1 + \beta$  for fixed bias.

$S = 1$  could be achieved with collector feed back bias at the cost of reducing  $R_B$  which draw more base current which causes less battery life for  $V_{CC}$

$S=1$  could be achieved with voltage divide bias at increase input current or increase supply voltage.

## SELF-ASSESSMENT QUESTIONS

1. Which Bias more thermally stable?

- (a) Emitter Bias
- (b) Base Bias
- (c) Collector feedback Bias
- (d) Voltage divider bias

2. Which of the following bias is less effected by temperature variation?

- (a) Voltage divider bias
- (b) Collector feedback bias



## SELF-ASSESSMENT QUESTIONS

3. Which of the following is ideal stability factor for BJT?

- (a) 1
- (b)  $1 + \beta$
- (c) zero
- (d)  $\beta$

4. Which of the following is the smallest realizable stability factor?

- (a) 1
- (b)  $1 + \beta$
- (c) zero
- (d)  $\beta$

## ANSWERS

1. D
2. A
3. C
4. A

## TERMINAL QUESTIONS

1. Obtain the expression for stability factor of BJT with respect to reverse saturation current.
2. Obtain the stability factor for Fixed bias of BJT.
3. Obtain the stability factor for Collector feedback bias of BJT.
4. Obtain the stability factor for voltage divider bias of BJT.
5. Compare stability of fixed bias and voltage divider bias.

## REFERENCES FOR FURTHER LEARNING OF THE SESSION

---

### Reference Book:

- I. Robert L. Boylestad and Louis Nashelsky - “Electronic Devices and Circuit Theory”

# THANK YOU



## Team – ANALOG ELECTRONIC CIRCUIT DESIGN

Prepared by – Dr. M. Siva Kumar