

Question bank – BEEC – END SEM REFERENCES


1. Define KCL, KVL with formulae ?
2. Define Voltage division rule ?
3. Define form factor, peak factor ?
4. Calculate the total inductance in a circuit in which $L_1=5H$, $L_2=10H$, $L_3=25H$ are connected in series
5. Draw the VI characteristics of PN junction Diode
6. Draw the symbols for PNP and NPN transistor
7. Classify three terminal voltage regulators
8. Mention few applications of OP AMP
9. Define Branches, loops, nodes ?
10. Calculate the total inductance in a circuit in which $L_1=5H$, $L_2=10H$, $L_3=25H$ are connected in series
11. Draw the series RLC circuit and mention total impedance in the network .
12. Define RMS, average Value in a sinusoidal wave form ?
13. Draw the VI characteristics of zener Diode
14. Explain how diode acts as switch with its equivalent circuit ?
15. Draw the pin diagrams of 7805 and 7905 Ics
16. Mention the applications of LM723
17. Mention the total equivalence inductance in the circuit If two inductors are connected in case i) Series case ii) Parallel
18. Calculate the branch currents in the shunt network if $R_1=R_2= 10K\Omega$, $R_3=R_4=40K\Omega$ powered with a supply of 20V.
19. Define form factor, peak factor ?
20. Define RMS, average Value in a sinusoidal wave form ?
21. Define Rectification and ripple factor
22. Illustrate the PNP & NPN Transistors with terminal voltages and currents
23. Draw the symbol of OP- AMP IC 741 with input and out put pins
24. Describe the IC 555 with its pin configuration
25. State maximum power transfer theorem?
26. Define power factor ?

Question bank – BEEC – END SEM REFERENCES

27. Draw the series RLC circuit and mention total impedance in the network .
28. Define reactive power, real power
29. Draw the circuit symbol for PNP & NPN Transistor
30. Mention different types of clippers and clamper circuits
31. Define slew rate, CMRR
32. Draw the op-amp symbol with input , output pins.

Important Long Questions

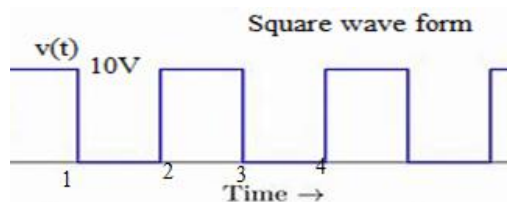
1. Enumerate the steps involved in mesh analysis
2. Calculate the average and RMS value of the square wave.




3. Explain the operation of full wave bridge rectifier with neat circuit and output wave form
4. Describe the features of op-amp with its pin configuration
5. Describe the steps involved to do nodal analysis
6. State and explain Thevenin's theorem with its equivalent circuit ?
7. If 2 capacitors are connected in i) series ii) in parallel If $C_1=10\mu\text{F}$ & $C_2= 50 \mu\text{F}$ Find the maximum energy stored when a 220V DC supply is across the combination?
8. State and explain maximum power transfer theorem with its equivalent circuit ?
9. The current drawn by a pure capacitance of $20\mu\text{F}$ is 1.382 A from 220V ac supply, find the supply frequency ?
10. If two sinusoidal currents are given by $I_1= 10 \sin(\omega t+\pi/3)$ and $I_2=(15\sin(\omega t-\pi/4)$, Calculate and plot the phase difference between them in degrees
11. Explain the concept of impedance in Series RL and RC circuit.
12. Calculate i) Frequency ii) RMS VALUE III) AVERAGE VALUE IV) FORM FACTOR in a sinusoidal signal of voltage $40 \sin(628)t$

Question bank – BEEC – END SEM REFERENCES

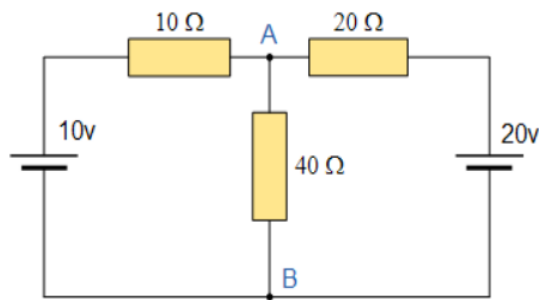13. A 4.2 V zener is used with the load current is to vary from 10 to 100 mA. Find the value of series resistance R to maintain a voltage of 4.2 V across the load. The input voltage is constant at 12V and the minimum zener current is 5 mA.
14. Explain the operation of center tapped full wave rectifier with neat circuit and output wave form
15. Explain about positive clamper with input and output waveforms
16. Explain how transistor can be used as a switch with an equivalent circuit
17. Describe the following i) OFFSET VOLTAGE ii) CMRR iii) SLEW RATE iv) input impedance v) output impedance v) openloop gain of OP-AMP.
18. Explain about IC 555 TIMER pin configuration, mention the applications of IC 555
19. List out the features of Analog and Digital ICS.
20. Explain about the comparator circuit using OPAMP
21. Find the Thevenin's voltage across 40 ohm resistance in the given circuit ?



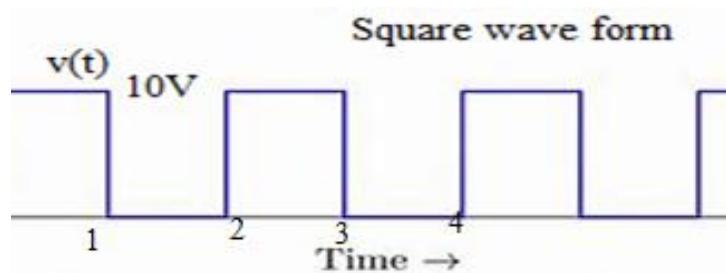-
22. Calculate the average and RMS value of the square wave




23. Explain the operation of full wave center tapped rectifier with neat circuit and output wave form
24. Classify IC voltage regulators and mention the applications of regulators

Question bank – BEEC – END SEM REFERENCES

25. IF four Inductors are connected in case i) parallel each of 60 Henry each ii) in series with $L_1=L_2=10H$, $L_3=L_4=20H$, then calculate the total equivalence inductance in both cases?

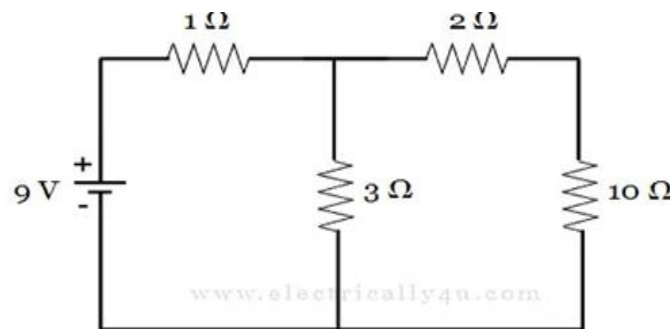26. For the given circuit, determine the current flowing through $10\ \Omega$ resistor using Norton's theorem.



27. State and explain Thevenin's theorem with its equivalent circuit ?

28. Calculate i) Frequency ii) RMS VALUE III) AVERAGE VALUE IV) FORM FACTOR in a sinusoidal signal of voltage $20 \sin(628)t$

29. Explain the concept of impedance in Series RL and RC circuit.

30. Draw the phasor representation of an alternating quantity represent phase lag and phase lead with waveforms


31. A $300\ \mu F$ capacitor is connected across is 240V, 50Hz system Determine i) the capacitance reactance ii) R.M.S value of current iii) Equations for voltages and currents

32. Explain the operation of half wave rectifier with neat circuit and output wave forms

33. A 6.2 V zener is used with the load current is to vary from 12 to 100 mA. Find the value of series resistance R to maintain a voltage of 6.2 V across the load of $1k\Omega$. The input voltage is constant at 12V and the minimum zener current is 10 mA.


Question bank – BEEC – END SEM REFERENCES

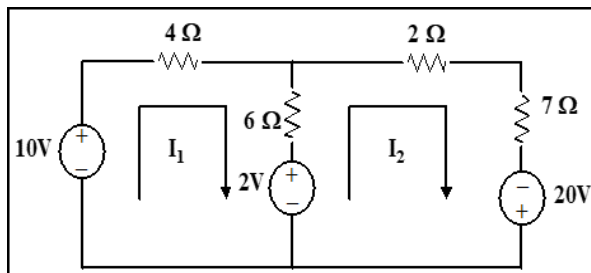34. Compare all rectifiers with respect to ripple factor, efficiency, TUF, PIV values.
35. Explain how transistor can be used as a switch with its equivalent circuits?
36. Classify IC voltage regulators explain about 3 terminal IC voltage regulators
37. Explain modes of IC 555 with its PIN configuration
38. Mention the applications of OP AMP AND TIMERS
39. Describe the characteristics of operational amplifier with pin configuration and symbol
40. Write the mesh equations and solve for the currents I_1 , and I_2 ?



41. The current drawn by a pure capacitance of $20\mu\text{F}$ is 1.382 A from 220V ac supply, calculate the supply frequency ?
42. Explain the operation of full wave bridge rectifier with neat circuit and output wave form
43. Classify the Analog and Digital ICs with few examples
44. State and explain Thevenin's theorem with its equivalent circuit ?

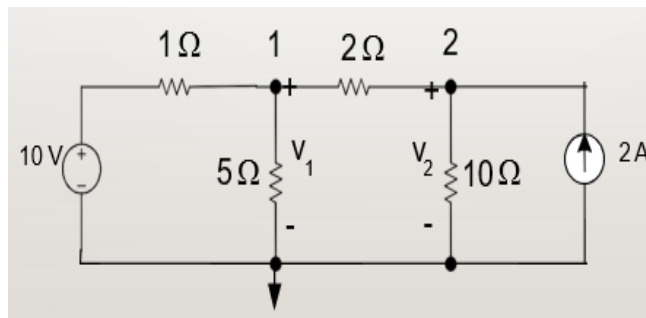45. Determine the Voltages (v_1) and (v_2) using node analysis



Question bank – BEEC – END SEM REFERENCES

- 46 State and explain about Nortans Theorem With equivalent circuit
- 47 Calculate i) Frequency ii) RMS VALUE III) AVERAGE VALUE IV) FORM FACTOR in a sinusoidal signal of voltage $40 \sin(628)t$
- 48 Define power factor , reactive power and real power , apparent power with formulae.
- 49 Write the polar form of the voltage given by $V = \sin [10 \pi t + \pi/3]$ V obtain its rectangular form ?
- 50 A $200 \mu\text{F}$ capacitor is connected across is 240V, 50Hz system Determine i) capacitance reactance ii) R.M.S value of current iii) Equations for voltages and currents
- 51 Explain about positive and negative clampers with input and output waveforms
- 52 A 4.2 V zener is used with the load current is to vary from 10 to 100 mA. Find the value of series resistance R to maintain a voltage of 4.2 V across the load. The input voltage is constant at 12V and the minimum zener current is 10 mA.
- 53 Compare PN junction and ZENER diodes in all aspects
- 54 Explain how diode acts as switch with its equivalent circuit ?
- 55 Describe about the LM 339 IC with PIN configuration
- 56 describe the applications of 555 IC timer with its pin configuration
- 57 Explain the operation of comparators with respect to op-amp
- 58 Distinguish three terminal IC voltage regulators .
- 59 Calculate the total capacitance in a circuit consists of $C_1 = 5 \mu\text{F}$, $C_2 = 10 \mu\text{F}$ connected in parallel and in series form?


Question bank – BEEC – END SEM REFERENCES

60 Draw the phasor representation of an alternating quantity represent phase lag and phase lead with waveforms

61 Explain about positive clamper circuits with neat output wave form

62 Draw the opamp characteristics with negative feed back and mention the practical characteristics of op-amp

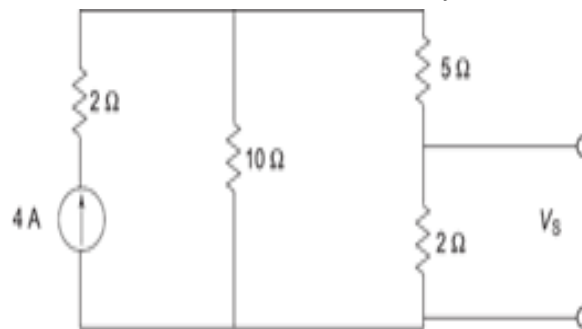63 Determine the current in the 10Ω resistance and find V_s in the circuit shown




64 If 2 capacitors are connected in i) series ii) in parallel If $C_1=10\mu F$ & $C_2= 50 \mu F$ Find the maximum energy stored when a 220V DC supply is across the combination?

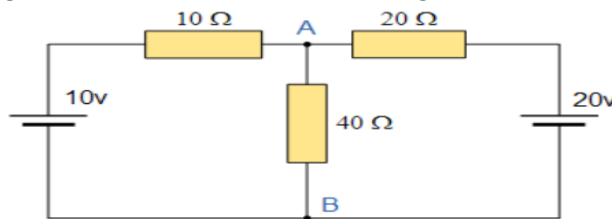Question bank – BEEC – END SEM REFERENCES

65 State and explain Maximum power transfer theorem with its equivalent circuit ?

66 Find the Thevenin's voltage across 40 ohm resistance in the given circuit ?



67 Calculate i) Frequency ii) RMS VALUE III) AVERAGE VALUE IV) FORM FACTOR in a sinusoidal signal of voltage $100 \sin(628)t$

68 Explain about apparent power, reactive power, real power, power factor with formulae?

69 Write the polar form of the voltage given by $V = \sin [10\pi t + \pi/4]$ V obtain its rectangular form ?

70 A Series RL circuit connected with $R=4\Omega$ and inductive reactance $X_L=3\Omega$ is connected to 100 V, 50 Hz. Find the amount of current, power drawn by the circuit and power factor?

71 Explain the operation of positive series clippers with and without reference voltage

72 A 6.2 V zener is used with the load current is to vary from 12 to 100 mA. Find the value of series resistance R to maintain a voltage of 6.2 V across the load. The input voltage is constant at 12V and the minimum zener current is 10 Ma

73 Describe how transistor acts as a switch with equivalent circuits ?

74 Explain the operation of PN junction diode with V-I characteristics ?

75 Enumerate about 7805, 7905 Voltage regulators with its pin configuration


76 What are the features of op-amp IC-741, explain with its pin configuration

77 Classify IC voltage regulators and mention the applications of regulators

78 Explain about IC 555 TIMER pin configuration, mention the features of IC 555

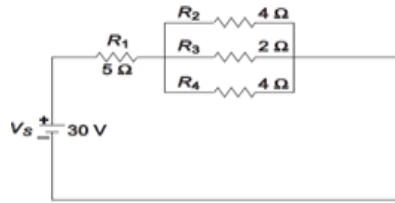Question bank – BEEC – END SEM REFERENCES

79 Calculate the total circuit current in the given circuit



80. Explain the operation of HALF WAVE rectifier with its operation and Output waveform?